JOINT AVIATION AUTHORITIES AIRLINE TRANSPORT PILOT'S LICENCE


Theoretical Knowledge Manual

Akademická krdžnica Vojenská letecká akadémia KOŠICE Ev. AK C'- 2026

AIRCRAFT GENERAL KNOWLEDGE 2

021 02 ELECTRICS AND ELECTRONICS

Second Edition, First Impression.

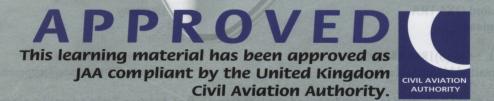





This text book is to be used only for the purpose of private study by individuals and may not be reproduced in any form or medium, copied, stored in a retrieval system, lent, hired, rented, transmitted or adapted in whole or in part without the prior written consent of Oxford Aviation Services Limited.

Copyright in all documents and materials bound within these covers or attached hereto, excluding that material which is reproduced by the kind permission of third parties and acknowledged as such, belongs exclusively to Oxford Aviation Services Limited.

Certain copyright material is reproduced with the permission of the International Civil Aviation Organisation, the United Kingdom Civil Aviation Authority and the Joint Aviation Authorities (JAA).

This text book has been written and published as a reference work to assist students enrolled on an approved JAA Air Transport Pilot Licence (ATPL) course to prepare themselves for the JAA ATPL theoretical knowledge examinations. Nothing in the content of this book is to be interpreted as constituting instruction or advice relating to practical flying.

Whilst every effort has been made to ensure the accuracy of the information contained within this book, neither Oxford Aviation Services Limited nor the publisher gives any warranty as to its accuracy or otherwise. Students preparing for the JAA ATPL theoretical knowledge examinations should not regard this book as a substitute for the JAA ATPL theoretical knowledge training syllabus published in the current edition of 'JAR-FCL 1 Flight Crew Licensing (Aeroplanes)' (the Syllabus). The Syllabus constitutes the sole authoritative definition of the subject matter to be studied in a JAA ATPL theoretical knowledge training programme. If you elect to subscribe to the amendment service offered with this book please note that there will be a delay between the introduction of changes to the Syllabus and your receipt of the relevant updates. No student should prepare for, or is currently entitled to enter himself/herself for, the JAA ATPL theoretical knowledge examinations without first being enrolled in a training school which has been granted approval by a JAA-authorised national aviation authority to deliver JAA ATPL training.

Oxford Aviation Services Limited excludes all liability for any loss or damage incurred or suffered as a result of any reliance on all or part of this book except for any liability for death or personal injury resulting from Oxford Aviation Services Limited's negligence or any other liability which may not legally be excluded.

Cover picture by courtesy of the Boeing Company

Published by: Jeppesen GmbH, Frankfurt, Germany

Contact Details:

Pilot Ground Training Department Oxford Aviation Training Oxford Airport Kidlington Oxford OX5 1RA England

Tel: ++44 (0)1865 844290 E-mail: ddd@oxfordaviation.net Sales and Service Department Jeppesen GmbH Frankfurter Strasse 233 63263 Neu-Isenburg Germany

Tel: ++49 (0)6102 508240

E-mail: fra-services@jeppesen.com

For further information on products and services from Oxford Aviation Training and Jeppesen visit our web sites at: www.oxfordaviation.net and www.jeppesen.com

ISBN: 0-88487-285-8

FOREWORD

Joint Aviation Authorities (JAA) pilot licences were first introduced in 1999. By the end of 2002, all 33 JAA member states will have adopted the new, pan-European licensing system. Many other countries world-wide have already expressed interest in aligning their training with the syllabi for the various JAA licences. These syllabi and the regulations governing the award and the renewal of licences are defined by the JAA's licensing agency, known as "Joint Aviation Requirements-Flight Crew Licensing", or JAR-FCL.

The introduction of JAA licences is, naturally, accompanied by associated JAR-FCL practical skill tests (tests of flying ability) and theoretical knowledge examinations corresponding to each level of licence: Private Pilot Licence (PPL), Commercial Pilot Licence (CPL), CPL with Instrument Rating and Air Transport Pilot Licence (ATPL). The JAR-FCL skill tests and the ground examinations, though similar in content and scope to those conducted by many national authorities, are inevitably different in detail from the tests and examinations set by any individual JAA member state under its own national scheme. Consequently, students who wish to train for JAA licences need access to study material which has been specifically designed to meet the requirements of the new licensing system.

As far as the JAA ATPL ground examinations are concerned, the subject matter to be tested is set out in the ATPL training syllabus contained in the JAA publication, 'JAR-FCL 1 (Aeroplanes)'. Inevitably, this syllabus represents a compromise between the differing academic contents of the national ATPL training syllabi it replaces. Thus, it follows that the advent of the new examinations has created a need for completely new reference texts to cover the requirements of the new syllabus. This series of manuals, prepared by Oxford Aviation Training and published by Jeppesen, aims to cover those requirements and to help student pilots prepare for the JAA ATPL theoretical knowledge examinations.

Oxford Aviation Training (OAT) is one of the world's leading professional pilot schools. It has been in operation for over thirty years and has trained more than 12,000 professional pilots for over 80 airlines, world-wide. OAT was the first pilot school in the United Kingdom to be granted approval to train for the JAA ATPL. As one of the most active members of the European Association of Airline Pilot Schools, OAT has been a leading player in the pan-European project to define, in objective terms, the depth and scope of the academic content of JAA ATPL ground training as outlined in 'JAR-FCL 1 (Aeroplanes)'. OAT led and coordinated this joint-European effort to produce the JAA ATPL Learning Objectives which are now published by the JAA itself as a guide to the theoretical knowledge requirements of ATPL training.

In less than two years since beginning JAA ATPL training, and despite the inevitable teething problems that national aviation authorities have experienced in introducing the new examination system, OAT has achieved an unsurpassed success rate in terms of the passes its students have gained in the JAA ATPL examinations. This achievement is the result of OAT's whole-hearted commitment to the introduction of the new JAA licensing system and of its willingness to invest heavily in the research and development required to make the new system work for its students. OAT has not only been at the forefront of the effort made to document JAA ATPL theoretical knowledge requirements, but it has also produced associated academic notes of the highest quality and created computer-generated and web-based ATPL lessons which ensure that its students are as well-prepared as possible to succeed in the ground examinations. OAT's experience and expertise in the production of JAA ATPL training material make this series of manuals the best learning material available to students who aspire to hold a JAA ATPL.

continued....

Jeppesen, established in 1934, is acknowledged as the world's leading supplier of flight information services, and provides a full range of print and electronic flight information services, including navigation data, computerised flight planning, aviation software products, aviation weather services, maintenance information, and pilot training systems and supplies. Jeppesen counts among its customer base all US airlines and the majority of international airlines world-wide. It also serves the large general and business aviation markets.

The combination of Jeppesen and OAT expertise embodied in these manuals means that students aiming to gain a JAA ATPL now have access to top-quality, up-to-date study material at an affordable cost.

Manuals are not, of course, the complete answer to becoming an airline pilot. For instance, they cannot teach you to fly. Neither may you enter for the new JAA ATPL theoretical knowledge examinations as a "self-improver" student. The new regulations specify that all those who wish to obtain a JAA ATPL must be enrolled with a flying training organisation (FTO) which has been granted approval by a JAA-authorised national aviation authority to deliver JAA ATPL training. The formal responsibility to prepare you for both the flying tests (now known as "skill tests") and the ground examinations lies with your FTO. However, these OAT/Jeppesen manuals represent a solid foundation on which your formal training can rest.

For those aspirant airline pilots who are not yet able to begin formal training with an FTO, but intend to do so in the future, this series of manuals will provide high-quality study material to help them prepare themselves thoroughly for their formal training. The manuals also make excellent reading for general aviation pilots or for aviation enthusiasts who wish to further their knowledge of aeronautical subjects to the standard required of airline pilots.

At present, the JAA ATPL theoretical knowledge examinations are in their infancy. The examinations will inevitably evolve over the coming years. The manuals are supported by a free on-line amendment service which aims to correct any errors and/or omissions, and to provide guidance to readers on any changes to the published JAA ATPL Learning Objectives. The amendment service is accessible at http://www.oxfordaviation.net/shop/notes.htm

OAT's knowledge of and involvement in JAR-FCL developments are second to none. You will benefit from OAT's expertise both in your initial purchase of this text book series and from the free amendment service. OAT and Jeppesen have published what they believe to be the highest quality JAA ATPL theoretical knowledge manuals currently available. The content of these manuals enables you to draw on the vast experience of two world-class organisations, each of which is an acknowledged expert in its field of the provision of pilot training and the publication of pilot training material, respectively.

We trust that your study of these manuals will not only be enjoyable but, for those of you undergoing training as airline pilots, will also lead to success in the JAA ATPL ground examinations.

Whatever your aviation ambitions, we wish you every success and, above all, happy landings.

Oxford, England. January 2002

PREFACE TO EDITION TWO, FIRST IMPRESSION

Edition Two of this work has been recompiled to give a higher quality of print and diagram. The opportunity has also been taken to update the contents in line with Oxford Aviation Training's experience of the developing JAA ATPL Theoretical Knowledge Examinations.

Oxford, England. September 2002

Textbook Series

Book	Title	JAR Ref. No.	Subject
1	010 Air Law		•
		004.04	
2	020 Aircraft General Knowledge 1	<u>021 01</u>	Airframes & Systems
		021 01 01/04 021 01 07 021 01 05 021 01 06 021 01 08/09 021 01 09/10 021 04 00 021 01 11	Fuselage, Wings & Stabilising Surfaces Hydraulics Landing Gear Flight Controls Air Systems & Air Conditioning Anti-icing & De-icing Emergency Equipment Fuel Systems
3	020 Aircraft General Knowledge 2	021 02	Electrics – Electronics
		021 02 01 021 02 02 021 02 05	Direct Current Alternating Current Basic Radio Propagation.
4	020 Aircraft General Knowledge 3	021 00	<u>Powerplant</u>
		021 03 01 021 03 02	Piston Engines Gas Turbines
5	020 Aircraft General Knowledge 4	<u>22</u>	<u>Instrumentation</u>
		022 01 022 03 022 02 022 04	Flight Instruments Warning & Recording Automatic Flight Control Power Plant & System Monitoring Instruments
6	030 Flight Performance & Planning 1	031 032	Mass & Balance Performance
7	030 Flight Performance & Planning 2	033	Flight Planning & Monitoring
8	040 Human Performance & Limitations		
9	050 Meteorology		
10	060 Navigation 1	061	General Navigation
11	060 Navigation 2	062	Radio Navigation
12	070 Operational Procedures		
13	080 Principles of Flight		
14	090 Communications		
15	Reference Material		

AIRCRAFT GENERAL KNOWLEDGE 2

TABLE OF CONTENTS

Subject Number		Title	
1	DIRECT CURRENT ELECTRICS		
	Chapter 1	Basic Principles	
	Chapter 2	Switches	
	Chapter 3	Circuit Protection and Capacitors	
	Chapter 4	Batteries	
	Chapter 5	Magnetism	
	Chapter 6	Generators, Alternators and Motors	
	Chapter 7	Aircraft Electrical Power Systems	
	Chapter 8	Bonding and Screening	
	Chapter 9	Specimen Questions	
2	ALTERNATING CURRENT ELECTRICS		
	Chapter 1	Introduction	
	Chapter 2	Alternators	
	Chapter 3	Practical Aircraft Systems	
	Chapter 4	Transformers	
	Chapter 5	A C Motors	
	Chapter 6	Basic Computers	
	Chapter 7	Semi Conductors	
3	BASIC RADIO PROPAGATION		
	Chapter 1	Basic Principles	
	Chapter 2	Oscillators	
	Chapter 3	Antennae	

JOINT AVIATION AUTHORITIES AIRLINE TRANSPORT PILOT'S LICENCE Theoretical Knowledge Manual

AIRCRAFT GENERAL KNOWLEDGE 2

021 02 01 DIRECT CURRENT

Second Edition, First Impression.

APPROVED This learning material has been approved as JAA compliant by the United Kingdom Civil Aviation Authority.





SUBJECT 1 - DIRECT CURRENT ELECTRICS

CHAPTER ONE - BASIC PRINCIPLES

Contents

		Page
1.1	INTRODUCTION	1.1 - 1
1.2	ELECTRO MOTIVE FORCE (EMF)	1.1 - 3
1.3	CURRENT	1.1 - 4
1.4	RESISTANCE	1.1 - 4
1.5	FACTORS AFFECTING THE RESISTANCE	1.1 - 5
1.6	UNITS OF RESISTANCE	1.1 - 5
1.7	RESISTORS	1.1 - 5
1.8	OHMS LAW	1.1 - 6
1.9	POWER	1.1 - 6
1.10	SERIES AND PARALLEL CIRCUITS	1.1 - 7
1.11	KIRCHOFF'S LAWS 1	.1 - 10
1.12	WHEATSTONE BRIDGE 1	.1 - 12
	SELF ASSESSMENT QUESTIONS	.1 - 15

1.1 INTRODUCTION

An electric current is created when electrons are caused to move through a conductor. Moving electrons can explain most electrical effects.

All materials consist of tiny particles called atoms. Atoms are made up of a nucleus and electrons. Atoms of different materials have different numbers of electrons. The electrons orbit the nucleus like the sun with planets spinning around it.

The electrons have a negative charge and the nucleus has an equal number of positive charges making the atom electrically neutral. The negative electron is held in its orbit by its attraction to the positive nucleus. Electrons in outer orbits are not so strongly attracted to the positive nucleus and may easily fly off and attach themselves to a neighbouring atom in the material. These are called free electrons.

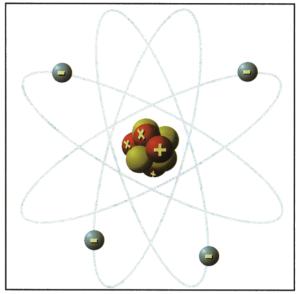


Figure 1.1.

An atom that has lost an electron becomes more positive and is called a positive ion, an atom that has gained an electron becomes more negative and is called a negative ion. If the free electrons can be made to move in a particular direction through the material an electric current has been created.

Materials which have free electrons are called conductors, e.g. copper, silver and aluminium. Materials which have very few free electrons are called insulators, e.g. wood, rubber, glass and plastics.

Electrons are caused to move along a piece of wire by applying a positive charge from some source at one end and a negative charge at the other. The positive charge attracts the free electrons and the negative charge repels them so there is a flow of electrons in one direction through the wire from the negative terminal to the positive terminal.

To maintain the current flow, the force which caused the electrons to flow in the first place must be maintained otherwise the electrons will all collect at the positive terminal and the current flow will cease. To keep the current flowing the source of the force which caused the electrons to move must be capable of absorbing the electrons from the positive terminal and transferring them through itself back to the negative terminal.

In this way the current can be maintained as long as there is a complete circuit.

Electricity had been in use before electrons had been discovered and it had been assumed that electricity had been the flow of something from positive to negative and all the laws of electricity were based on this idea. This is known as conventional flow. Flow from negative to positive is known as electron flow.

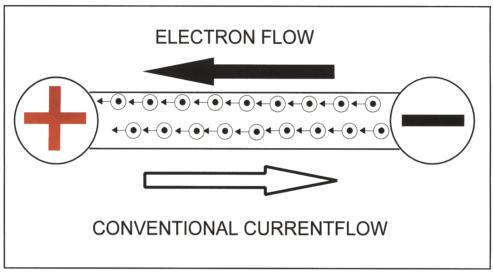


Figure 1.2

There are six basic means to provide the force which causes electrons to flow:-

- a) Friction static electricity
- b) Chemical Action cells and batteries (primary and secondary cells)
- c) Magnetism generators and alternators
- d) Heat thermocouples (junction of two dissimilar metals)
- e) Light photo electric cell
- f) Pressure piezo electric crystals

Of these only Chemical Action (batteries) and Magnetism (generators) produce electrical power in sufficient quantities for normal daily needs.

1.2 ELECTRO MOTIVE FORCE (EMF)

For electric current to flow there must be a force behind it. In the same way that water needs a force (pressure) to make it flow, electricity needs pressure, Electro Motive Force (EMF), to make it flow.

In a water tank if pressure decreases, flow decreases. In electrics if the EMF decreases the flow of electrons decreases.

EMF is measured in units of **Voltage**. The number of volts is a measure of the EMF or **Potential Difference** (the difference in electrical potential between the positive and negative terminal). Voltage is given the symbol **V** or **E**

By increasing the Voltage the flow of electrons increases past any point in a circuit, and decreasing the voltage decreases the flow. To maintain the correct flow it is normal to keep a constant Voltage in a circuit.

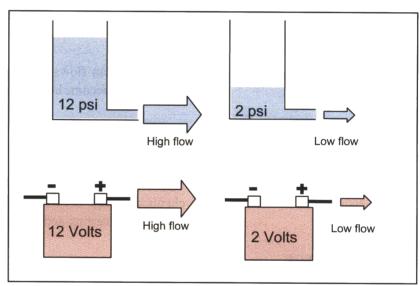


Figure 1.3 Comparison between voltage and water pressure

The source of the voltage can be a battery or a generator. Batteries become discharged as their voltage is used so are limited in their use. Generators are used to maintain a constant Voltage.

For high and low Voltages the following prefixes are used:-

One Microvolt - one millionth of a volt $(1\mu V)$

One Millivolt - one thousandth of a volt (1mV)

One Kilovolt - one thousand volts (1kV)

To measure voltage a **voltmeter** is used. It is connected across the two points between which the voltage is to be measured without disconnecting the circuit.

1.3 CURRENT

The current (symbol I) in a conductor is the number of electrons passing any point in the conductor in one second and is measured in amperes or amps (symbol A).

Current can be measured by an instrument called an **ammeter** which is connected into the circuit so that the current in the circuit passes through the ammeter.

Small values of current are given the following prefixes:

One Microamp - one millionth of an ampere $(1\mu A)$ One Milliamp - one thousandth of an ampere (1mA)

Effects of an electric current:

a)	Heating Effect.	When a current flows through a conductor it always causes the
		conductor to become hot - electric fires, irons, light bulbs and fuses

b) **Magnetic Effect**. A magnetic field is always produced around the conductor when a current flows through it - motors, generators and transformers.

c) Chemical Effect. When a current flows through certain liquids (electrolytes) a chemical change occurs in the liquid and any metals immersed in it - battery charging and electroplating.

1.4 RESISTANCE.

For a current to flow there must be a complete path or circuit. The fewer obstructions in the circuit the greater will be the current flow. The higher the Voltage the greater will be the current flow.

The obstruction in the circuit which opposes the current flow is called resistance. Different materials have different numbers of free electrons, those with more free electrons will have a lower resistance than those with few free electrons, so those with more free electrons are better conductors of electricity.

For a fixed voltage the smaller the resistance the larger will be the current flow and the larger the resistance the smaller will be the current flow. The current in the circuit can therefore be adjusted by altering the resistance.

1.5 FACTORS AFFECTING THE RESISTANCE

- a) Type of material. Eg. Silver is a better conductor than Copper
- b) Length. The longer the wire the greater the resistance
- c) Cross sectional area. The thicker the wire the smaller the resistance
- d) Temperature. The symbol for temperature coefficient is α (alpha). If resistance increases with an increase of temperature, the resistor is said to have a Positive Temperature Coefficient (PTC). If resistance decreases with an increase of temperature, the resistor is said to have a Negative Temperature Coefficient (NTC). Resistors having these characteristics are used in aircraft systems for temperature measurement.

1.6 UNITS OF RESISTANCE

The unit of resistance is the **Ohm** (symbol Ω) A material has a resistance of one ohm if an applied voltage of one volt produces a current flow of one ampere.

For larger and smaller values :-

One millionth of an ohm = one microhm (1 $\mu\Omega$)


One thousandth of an ohm = one milliohm $(1 \text{m}\Omega)$

One thousand ohms = one kilohm $(1 \text{ k}\Omega)$

One million ohms = one megohm (1 M Ω)

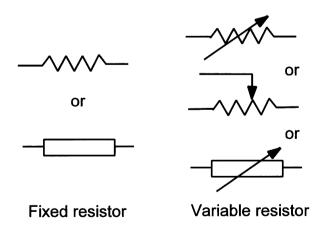1.7 RESISTORS

Sometimes resistance is used to adjust the current flow in a circuit by fitting resistors of known value. These can be either fixed or variable and can be symbolised like this:-



1.8 OHMS LAW

In a closed circuit there is a relationship between Voltage Current and Resistance. If the Voltage remains constant any increase in resistance will cause a decrease in current and vice-versa (Current inversely proportional to resistance).

If the resistance remains the same any increase in voltage will cause an increase in current and viceversa (Current directly proportional to voltage).

This is expressed as OHMS law:

$$V = IR$$

And by transposition

$$I = \underline{V}$$
 or $R = \underline{V}$
 R

1.9 POWER

When a Force produces a movement then Work is said to have been done, the rate at which work is done is called Power.

In an electric circuit Work is done by the Voltage causing the **current** to flow through a **resistance**, creating heat, magnetism or chemical action

The rate at which work is done is called **Power** and is measured in **Watts**

Three formulae for calculating power can be derived from the two basic formulae V=IR and W=VxI

a) Voltage unknown $W = I^2 R$

b) Resistance unknown $\dot{\mathbf{W}} = \mathbf{V} \mathbf{x} \mathbf{I}$

c) Current unknown $\mathbf{W} = \underline{\mathbf{V}}^2$ \mathbf{R}

When a current passes through a resistor it becomes hot and will eventually melt if the current becomes excessive.

The amount of heat developed by a current I in a resistor R is I² R Watts, therefore it can be seen that the heating effect is proportional to the square of the current. So a small increase in current can cause a significant increase in heating effect.


Each electrical component will be given a Power Rating (maximum wattage) which, if exceeded will cause the component to overheat. Eg. 60 Watt light bulb.

Each electrical circuit in an aircraft will be protected by a fuse or circuit breaker which will prevent the maximum power rating of a component to be exceeded by breaking the circuit if the current increases.

1.10 SERIES AND PARALLEL CIRCUITS

More than one resistance can be connected in any one circuit and the may be connected in Series - one after the other, or in Parallel - alongside each other.

a) Series

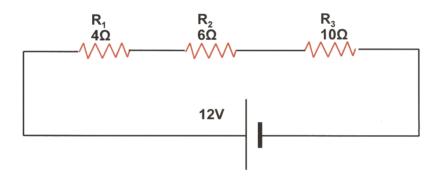

Series connection reduces current flow and therefore power consumption, but can be impractical because individual loads (resistances) cannot be individually controlled. Also the failure of one resistance would mean failure of the rest of the circuit.

The total circuit resistance can be calculated by summing the individual resistances.

$$R_{T} = R_{1} + R_{2} + R_{3}$$
ie. $R_{T} = 4 + 6 + 10$


$$R_{T} = 20 \text{ ohms}$$

$$V = IR \text{ so current} = \frac{12}{20} = 0.6 \text{ amps}$$

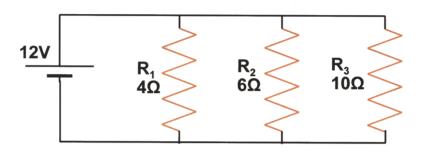b) Parallel

Parallel connection ensures each resistor is individually controllable and receives the same voltage. Failure of one resistor will not affect the others .Most aircraft loads are connected in parallel.

The total circuit resistance can be found by the following method.



$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{4} + \frac{1}{10}$$

$$\frac{1}{R_T} \qquad \qquad = \qquad \frac{15+10+6}{60}$$


$$\frac{1}{R_T} = \frac{31}{60}$$

$$R_{T} = \underline{\underline{60}}$$

$$R_T = 1.94 \text{ ohms}$$

$$V = IR$$
 so current = $\underline{12} = 6$ amps approx 1.94

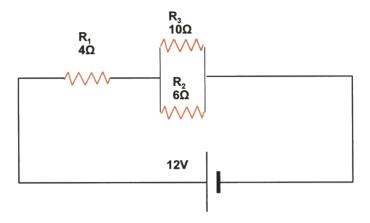c) Combination of series and parallel resistors



First evaluate the parallel resistors then add the result to the series resistor

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{6}$$

Find the lowest common denominator

$$\frac{1}{R_T} = \frac{3+5}{30}$$

$$\frac{1}{R_T} = \frac{8}{30}$$

 $R_T = 30 \over 8$ Therefore the total resistance for the two parallel resistors is:

$$R_T = 3.75 \text{ ohms}$$

An alternative method of calculating the resistance of 2 resistors in parallel is:

$$R_T = \underbrace{R_1 \times R_2}_{R_1 + R_2}$$

Using the above example

$$R_T = \underbrace{10 \times 6}_{10+6}$$

$$R_{T} = \frac{60}{16}$$

$$R_{\rm T} = 3.75 \text{ ohms}$$


Note: The total resistance of resistors in parallel is always less than the value of the lowest resistor e.g. 3.75 ohms is less than 6 ohms.

Total circuit resistance is 3.75 ohms plus 4 ohms = $\frac{7.75 \text{ ohms}}{1.00 \text{ ohms}}$

1.11 KIRCHOFF'S LAWS

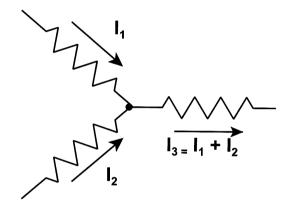
a) First law

The total current flow into a point on a circuit is equal to the current flow out of that point e.g.



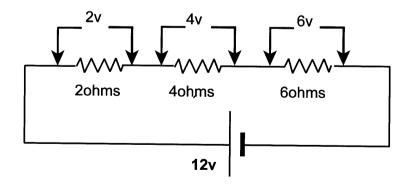b) Second law

If all the voltage drops in a closed circuit are added together, their sum always equals the voltage applied to that closed circuit.



To prove Kirchoff's 2nd Law, first we must calculate the current and therefore the total resistance

$$\begin{array}{lll} R_T & = & R_1 + R_2 + R_3 \\ R_T & = & 2 + 4 + 6 \\ R_T & = & 12 \text{ ohms} \end{array}$$

From Ohm's Law

$$V = IR \qquad \qquad \therefore \qquad I = \frac{V}{R}$$

$$I = \frac{12}{12}$$

I = 1 amp

We can now calculate the voltage drops throughout the circuit. At present all we know is there is 12 volts before the 2 ohm resistor and zero volts after the 6 ohm resistor.

Using Ohm's Law V= IR. To calculate the voltage drop across the 2 ohm resistor:

$$V = 1$$
 amp x 2 ohms = 2 volts

Therefore, the voltage drop is 2 volts i.e. 12 volts enters the 2 ohm resistor 10 volts exits. Using the same approach for the 4 ohm resistor:

V = 1 amp x 4 ohms = 4 volts i.e. 10 volts enters the 4 ohm resistor and 6 volts exits.


Finally, calculating the voltage drop across the 6 ohm resistor:

V = 1 amp x 6 ohms = 6 volts i.e. 6 volts enters the 6 ohm resistor and zero volts exit.

Therefore, the voltage drop in the closed circuit is 2 volts + 4 volts + 6 volts = 12 volts which equals the voltage applied.

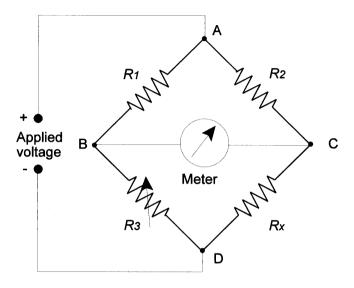1.12 WHEATSTONE BRIDGE

The two statements in Kirchoff's laws concerning the sums of currents and voltages in a circuit are useful for solving complicated problems. The arrangement of resistors below is called a **Wheatstone Bridge**.




The Wheatstone bridge can be used to compare an unknown resistance R_X with others of known values. R_3 is varied until zero deflection is obtained on the ammeter. At this point the products of the diagonally opposite resistors are equal to each other because there is no current flow between point B and point C and the bridge is said to be balanced.

ie.
$$R_1 \times R_x = R_2 \times R_3$$
 from which

$$R_{x} = \underline{R_{2} \times R_{3}}_{R_{I}}$$

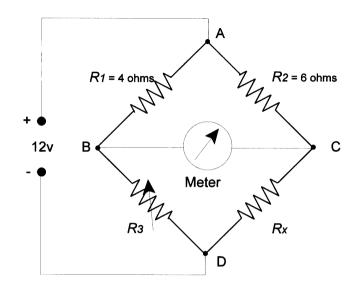Example:

If R_3 is adjusted until the ammeter reading is zero when R_3 is 3 ohms, what is the value of R_X ?



$$R_1 \times R_x = R_2 \times R_3$$
 from which

$$R_{x} = \frac{R_{2} \times R_{3}}{R_{1}}$$

therefore

$$R_{x} = \underline{6 \times 3}$$

$$R_{x} = \underline{18}$$

$$R_x = 4.5 \text{ ohms}$$

DC ELECTRICS SELF ASSESSMENT QUESTIONS - THEORY

Answers in chapter 9

- 1. All effects of electricity take place because of the existence of a tiny particle called the:
 - a) electric.
 - b) proton.
 - c) neutron.
 - d) electron.
- 2. The nucleus of an atom is:
 - a) positively charged.
 - b) negatively charged.
 - c) statically charged.
 - d) of zero potential.
- 3. An atom is electrically balanced when:
 - a) its protons and electrons balance each other.
 - b) the protons outnumber the electrons.
 - c) the electrons outnumber the protons.
 - d) the electric and static charges are balanced.
- 4. The electrons of an atom are:
 - a) positively charged.
 - b) neutral.
 - c) negatively charged.
 - d) of zero potential.
- 5. A material with a deficiency of electrons becomes:
 - a) positively charged.
 - b) negatively charged.
 - c) isolated.
 - d) overheated.

- 6. A material with a surplus of electrons becomes:
 - a) positively charged.
 - b) negatively charged.
 - c) over charged.
 - d) saturated.
- 7. Heat produces an electric charge when:
 - a) like poles are joined.
 - b) a hard and soft glass is heated.
 - c) the junction of two unlike metals is heated.
 - d) hard and soft material are rubbed together.
- 7. Friction causes:
 - a) mobile electricity.
 - b) basic electricity.
 - c) static electricity.
 - d) wild electricity.
- 8. Chemical action produces electricity in:
 - a) a light meter.
 - b) a generator.
 - c) a primary cell.
 - d) starter generator.
- 9. A photo electric cell produces electricity when:
 - a) two metals are heated.
 - b) exposed to a light source.
 - c) a light source is removed.
 - d) exposed to the heat of the sun.

UNITS 1

1.

ELECTRICS

	a)	KVAR's	
	b)	watts	
	c)	amps	
	d)	volts	
2.	The units of electrical power is measured in:		
	a)	watts	
	b)	amperes	
	۵)	ohms	
	c)		

a) b)

c)d)

4.

- a) current
- b) power dissipation

the volt

the watt

An ammeter measures:

the ampere

c) differences of electrical potential

The difference in electric potential is measured in:

- d) heat energy
- 5. Materials containing 'free electrons' are called:
 - a) insulators
 - b) resistors
 - c) collectors
 - d) conductors

6	The unit used for measuring the E.M.F. of electricity is:
υ.	The unit used for measuring the E.W.F. of electricity is:

- a) the ohm
- b) the ampere
- c) the volt
- d) the watt

7. The unit used for measuring:

- a) current is the volt.
- b) resistance is the ohm.
- c) electric power is the capacitor.
- d) E.M.F. is the amp.

8. Three resistance of 60 ohms each in parallel give a total resistance of:

- a) 180 ohms
- b) 40 ohms
- c) 30 ohms
- d) 20 ohms

9. A voltmeter measures:

- a) electro-motive force.
- b) the heat loss in a series circuit.
- c) the current flow in a circuit.
- d) the resistance provided by the trimming devices.

10. Watts =

- a) resistance squared x amps
- b) volts x ohms
- c) ohms x amps
- d) volts x amps

UNITS 2

ELECTRICS

- 1. The total resistance of a number of power consumer devices connected in series is:
 - a) the addition of the individual resistances.
 - b) the addition of the reciprocals of the individual resistance.
 - c) twice the reciprocal of the individual resistances.
 - d) the reciprocal of the total.
- 2. The total resistance of a number of resistances connected in parallel is:

a)
$$R = R_1 + R_2 + R_3 + R_4$$

b)
$$1 = \underline{1} + \underline{1} + \underline{1} + \underline{1} + \underline{1}$$

 $R_T R_1 R_2 R_3 R_4$

c)
$$\frac{1}{R_T} = R_1 + R_2 + R_3 + R_4$$

d)
$$R = \frac{1}{1} + \frac{R2}{1} + \frac{1}{1} + \frac{R4}{1}$$

- 3. Ohms Law states:
 - a) Current in amps = Resistance in ohms

Electromotive force in volts

b) Resistance in ohms = Current in amps

Electromotive force in volts

c) Current in amps = <u>Electromotive force in volts</u>

Resistance in ohms

- 4. A device consuming 80 watts at 8 amps would have a voltage supply of:
 - a) 640 volts.
 - b) 12 volts.
 - c) 10 volts.
 - d) 8 volts.

DC L	LLUIN	DAGE : Intelligence
5.	In a s	imple electrical circuit, if the resistors are in parallel, the total current consumed is equal to:
	a)	the sum of the currents taken by the devices divided by the number of devices.
	b)	the sum of the currents taken by the devices.
	c)	the average current taken by the devices times the number of the devices.
	d)	the sum of the reciprocals of the currents taken by the devices.
6.	The s	symbol for volts is:
	a)	E or W
	b)	V or E
	c)	I or V
	d)	R or W
7.	Elect	rical potential is measured in:
	a)	watts
	b)	bars
	c)	volts
	d)	ohms
8.		number of electrical consuming devices were connected in parallel the reciprocal of the total cance would be:
	a)	the sum of the currents.
	b)	the sum of the reciprocals of the individual resistances.
	c)	the sum of their resistances.
	d)	volts divided by the sum of the resistances.
9.	The	current flowing in an electrical circuit is measured in:
	a)	volts
	b)	ohms
	c)	inductance
	d)	amps
10.	Elect	tro-motive force is measured in:
	a)	amps x volts
	b)	watts
	c)	ohms
	d)	volts

DC ELECTRICS

MORE SELF ASSESSMENT QUESTIONS Answers page 1 - 23

Oxford Aviation College

- 1. OHMS law is given by the formula
 - a) $I = \underline{R}$
 - b) $V = \underline{R}$
 - c) $I = \frac{V}{R}$
 - d) $R = V \times I$
- 2. The current flowing in a circuit is
 - a) Directly proportional to resistance, indirectly proportional to voltage
 - b) Directly proportional to temperature, inversely proportional to resistance
 - c) Inversely proportional to resistance, directly proportional to voltage
 - d) Inversely proportional to applied voltage, directly proportional to temperature
- 3. The unit of EMF is the
 - a) Ampere
 - b) Volt
 - c) Watt
 - d) Ohm
- 4. Potential difference is measured in
 - a) Amps
 - b) Volts
 - c) Watts
 - d) Ohms

- a) Ampere
- b) Volt
- c) Watt
- d) Ohm

6. The unit of resistance is the

- a) Ampere
- b) Volt
- c) Watt
- d) Ohm

7. Electrical power is measured in

- a) Ampere
- b) Volt
- c) Watt
- d) Ohm

8. 1,250 ohms may also be expressed as

- a) 1250 K ohms
- b) 1.25 K ohms
- c) 1.25 M ohms
- d) 0.125 K ohms


9. 1.5 M ohms may also be expressed as

- a) 15000 ohms
- b) 1500 ohms
- c) 150000 ohms
- d) 1500 K ohms

10. 550 K ohms may also be expressed as

- a) 550000 M ohms
- b) 0.55 M ohms
- c) 55000 ohms
- d) 0.55 ohms

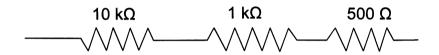- 11. The voltage applied to a simple resistor increases
 - a) Current will decrease but power consumed remains constant
 - b) Resistance and power decrease
 - c) Current flow will increase and power consumed will increase
 - d) Current flow increases and power consumed decreases
- 12. What is the total resistance in this circuit



- a) 11.5 ohms
- b) 11,500 K ohms
- c) 11.5 K ohms
- d) 11.5 M ohms


LOOK AT THE CIRCUIT AT ANNEX 'A' AND ANSWER THE FOLLOWING QUESTIONS

- 13. The total resistance of the circuit is
 - a) 14 ohms
 - b) 39.6 ohms
 - c) 25.6 ohms
 - d) varies with the applied voltage
- 14. The current flow indication on ammeter 'A' would be
 - a) 2 amps
 - b) 2 volts
 - c) 2.5 amps
 - d) 2.5 volts
- 15. The total power consumed in the circuit will be
 - a) 14 kilowatts
 - b) 56 kilowatts
 - c) 56 watts
 - d) 14 watts

- 16. The power consumed by R5 alone is
 - a) 14 watts
 - b) 28 watts
 - c) 112 watts
 - d) 28 kilowatts
- 17. The indication on voltmeter V1 will be
 - a) 2.3 volts
 - b) 28 volts
 - c) 9.2 volts
 - d) 92 volts
- 18. The indication on voltmeter V3 will be
 - a) 28 volts
 - b) 14 volts
 - c) 14 amps
 - d) 3.5 volts
- 19. The indication on voltmeter V2 will be
 - a) 28 volts
 - b) 4.8 volts
 - c) 9.6 volts
 - d) 14 volts
- 20. The current flowing through R2 is
 - a) 0.04 amps
 - b) 0.4 amps
 - c) 4 amps
 - d) 40 milliamps
- 21. The current flowing through R3 is
 - a) 0.04 amps
 - b) 0.4 amps
 - c) 4 amps
 - d) 40 milliamps

- 22. The current flowing through R4 is
 - a) 120 milliamps
 - b) 1.2 amps
 - c) 19.2 amps
 - d) 1.92 milliamps
- 23. The power consumed by R2 alone is
 - a) 1.92 kilowatts watts
 - b) 1.92 watts
 - c) 65.3 watts
 - d) 65.3 kilowatts
- 24. The power consumed by R3 alone is
 - a) 1.92 kilowatts watts
 - b) 1.92 watts
 - c) 65.3 watts
 - d) 65.3 kilowatts
- 25. The power consumed by R4 alone is
 - a) 5.76 kilowatts
 - b) 5.76 volts
 - c) 5.76 watts
 - d) 3.33 watts
- 26. The power consumed by R1 alone is
 - a) 18.4 kilowatts
 - b) 42.32 watts
 - c) 18.4 watts
 - d) 4.232 kilowatts

ANNEX 'A'

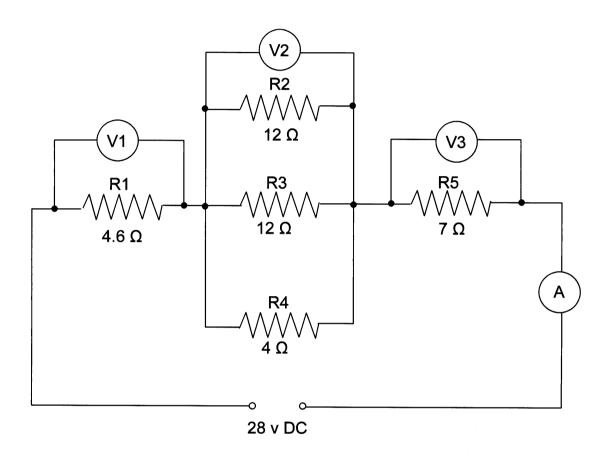

ANSWERS

- 1. C
- 2. C
- 3. B
- 4. B
- 5. A
- 6. D
- 7. C
- 8. B
- 9. D
- 10. B
- 11. C
- 12. C
- 13. Total circuit resistance, evaluate the total resistence of the three resistors in parallel first

$$\frac{1}{R_{T}} = \frac{1}{R_{1}} + \frac{1}{R_{2}} + \frac{1}{R_{3}}$$

$$\frac{1}{R_T} = \frac{1}{12} + \frac{1}{12} + \frac{1}{4}$$

$$\frac{1}{R_T} = \frac{1+1+3}{12}$$

$$\frac{1}{R_T} = \frac{5}{12}$$

$$R_{T} = \underline{12} = 2.4\Omega$$

Then add the resistances in series

$$4.6 + 2.4 + 7 = 14\Omega$$

14.
$$I = V = 2 \text{ amps}$$

ANSWERS

15.C

16.B

17.C

18.B

19.B

17.13

20.B

21.B

22.B

23.B

24.B 25.C

26.C

27.C

CHAPTER TWO - SWITCHES

Contents

		Page
2.1	SWITCHES	1.2 - 1
2.2	PROXIMITY DETECTORS	1.2 - 3
2.3	TIME SWITCHES	1.2 - 5
2.4	CENTRIFUGAL SWITCHES	1.2 - 5

2.1 SWITCHES

The initiation and control of aircraft circuits is achieved by switches and relays. Some typical switches are described here.

Toggle switch

A general purpose switch common in older aircraft having a number of isolating contacts inside. Can be a two position switch (on or off) or a multi position switch sprung biased to the centre or off position and then pressed and held to select in the desired direction.

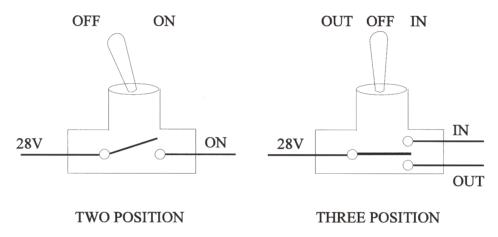


Figure 2.1

Switchlight

Switchlights have largely superceded toggle switches in modern aircraft and combine the functions of a switch with a push action and an indicator light for the associated function.

There are two basic types

- a) **Momentary action** press and hold to activate, release to deactivate.
- b) **Alternate action** press and release to activate, press and release a second time to deactivate.

The indicator in the lens confirms the selected position or provides a warning which requires the switch to be selected.

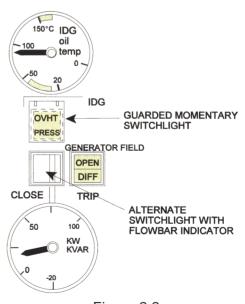


Figure 2.2

Guarded Switches

Toggle switches or switchlights can be guarded to prevent inadvertent operation. Eg. Generator disconnect, fuel dump master. (See previous diagram)

Micro switch

Microswitches are still used in modern aircraft to detect the position of a particular device eg. Door open or closed.

The name Microswitch describes the small movement between the 'make and break' position. Microswitches can activate indications on the flight deck or control relays for a sequenced operation. Largely replaced by proximity detectors nowadays.

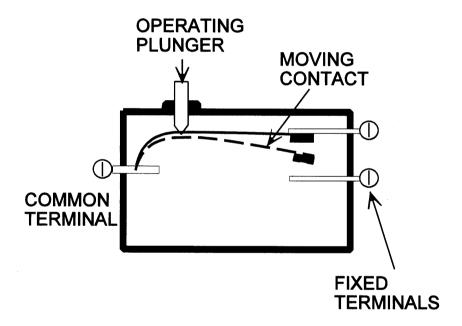


Figure 2.3

Bi-metallic switch (Thermal switch.)

Bi-metallic switches are temperature sensitive switches and are activated when a threshold value of temperature is reached to provide an indication to the pilot or to activate / deactivate a circuit. Eg Fire detection circuits, battery overheat switch, oil tem warning light.

2.2 PROXIMITY DETECTORS

Proximity Detectors are electrical or electronic sensors that respond to the presence of a material. The electrical or electronic response is used to activate a switch, relay or transistor. There are many types of proximity detectors, the major types being inductive, capacitive and magnetic. The inductive and magnetic sensors need the monitored material to be metal, but the capacitive type can monitor either metal or non-metal materials.

Inductive Type. This type of sensor has an inductance coil whose inductance changes when a ferromagnetic material (target) is brought into close proximity with it.

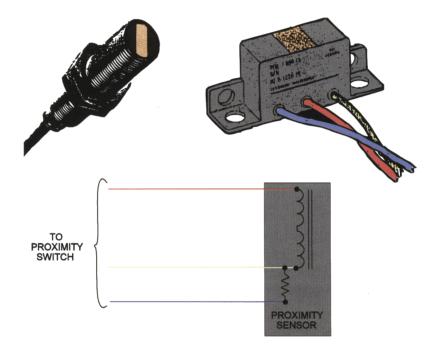


Figure 2.4

This type of sensor is used in undercarriage system in place of micro switches. A typical undercarriage system is described below. Each proximity switch consists of three components:

- a) A printed circuit card located in what is called the landing gear accessory unit.
- b) A sensor located on appropriate landing gear structure.
- c) An actuator (or target) for each sensor, located adjacent to its sensor.

The proximity sensor is a hermetically sealed unit, and is actuated by the presence of the actuator or target, ie. it is not touched by it. As a result, the proximity switch is unaffected by atmospheric conditions, and is highly reliable.

Capacitive Type. In this type of sensor detection is made by a capacitor undergoing a capacitance change owing to the proximity of material.

The capacitive proximity detector is an extremely versatile device in that it is capable of detecting all materials, liquid and solid. As well as detecting the presence of a ferrous or non-ferrous target, it can be used to detect high or low liquid levels in a hydraulic or fuel system.

Magnetic Type. A coil situated in a magnetic field will have an emf induced in it if the magnetic flux changes. The magnitude of the induced emf will depend on the rate at which the flux is changed. These are the basic principles on which the magnetic proximity detectors operate.

In its simplest form, a coil is wound around a bar magnet and one pole of the magnet is then located close to a ferrous object. If the ferrous object moves, the flux in the magnetic changes and an emf is induced in the coil. If a number of ferrous objects move past the magnet, a train of pulses is induced in the coil.

Magnetic detectors are most commonly used in conjunction with mild steel gear wheels, each tooth in the wheel being, in effect, a ferrous object. The detector is located radially and close to the periphery of the wheel and provides an output having a frequency equal to the frequency of passage of the teeth past the detector.

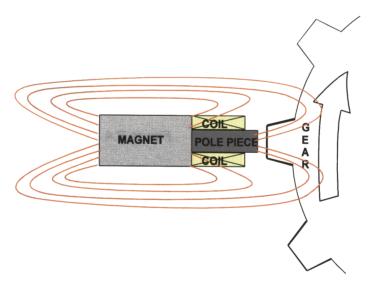


Figure 2.5

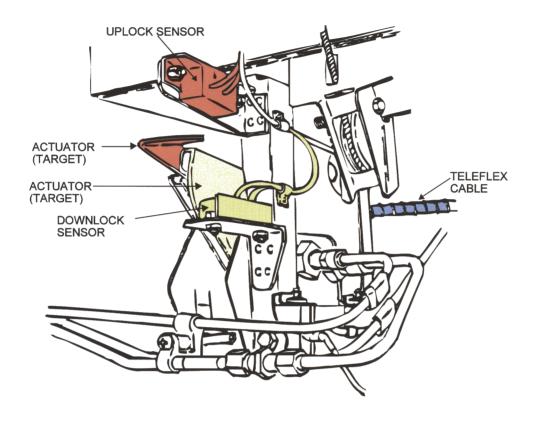


Figure 2.6 Landing Gear Position Sensors

2.3 TIME SWITCHES

Time switches or relays can be initiated electrically or mechanically to activate a circuit after a specific time interval has occurred. Eg. Auxiliary power unit air intake door closes 30 seconds after APU has shut down.

2.4 CENTRIFUGAL SWITCHES

These can be set to activate or de-activate a circuit as the rpm of a device increases or decreases. Eg. Starter motor cut out switch.

CHAPTER THREE - CIRCUIT PROTECTION AND CAPACITORS

Contents

		Page
3.1	ELECTRICAL FAULTS	1.3 - 1
3.2	CIRCUIT PROTECTION DEVICES	1.3 - 1
3.3	FUSES	1.3 - 1
3.4	THE CARTRIDGE FUSE	1.3 - 2
3.5	SPARE FUSES	1.3 - 3
3.6	HIGH RUPTURE CAPACITY (HRC) FUSES	1.3 - 3
3.7	DUMMY FUSES.	1.3 - 4
3.8	CURRENT LIMITERS	1.3 - 4
3.9	CIRCUIT BREAKERS	1.3 - 5
3.10	REVERSE CURRENT CIRCUIT BREAKERS	1.3 - 6
3.11	CAPACITORS	1.3 - 7
3.12	CAPACITANCE	1.3 - 8
3.13	CAPACITOR IN A DC CIRCUIT	1.3 - 9
3.14	CAPACITOR IN AN AC CIRCUIT	1.3 - 10
3.15	CAPACITORS IN PARALLEL	1.3 - 11
3.16	CAPACITORS IN SERIES	1.3 - 11
SELF	ASSESSMENT OUESTIONS	1.3 - 13

3.1 ELECTRICAL FAULTS

In an electrical circuit, abnormal conditions may arise for a variety of reasons, which can cause over current or over voltage conditions.

If allowed to persist, these abnormal conditions or faults will lead to damage or destruction of equipment and in extreme cases, loss of life. Certainly the essential power supplies will fail, and it is therefore necessary to protect circuits against all such faults, by the use of fuses and circuit breakers.

3.2 CIRCUIT PROTECTION DEVICES

There are a number of protection devices used in aircraft electrical systems but only 2 basic types are discussed here:

- a) Fuses.
- b) Circuit breakers.

The fundamental difference in the type of protection provided by fuses and circuit breakers is in their time of operation relative to the attainment of maximum fault current.

A fuse normally opens the circuit before full fault current is reached, whereas the circuit breaker opens after the full fault current is reached.

This means that when circuit breakers are used as the protection device, both the circuit breaker and the component must be capable of withstanding the full fault current for a short time.

The circuit breaker has the capability, which the fuse has not, of opening and closing the circuit, and can perform many such operations before replacement is necessary, it may also be used as a circuit isolation switch.

3.3 FUSES

There are 3 basic types of fuse currently in use on aircraft:

- a) cartridge fuse.
- b) high rupture capacity (HRC) fuse.
- c) current limiter fuse.

3.4 THE CARTRIDGE FUSE

The cartridge type fuse consists of a tubular glass or ceramic body, 2 brass end caps and a fuse element.

The element may be one of the following:

- a) tinned copper wire.
- b) silver wire.
- c) a strip of pure zinc electro tinned.

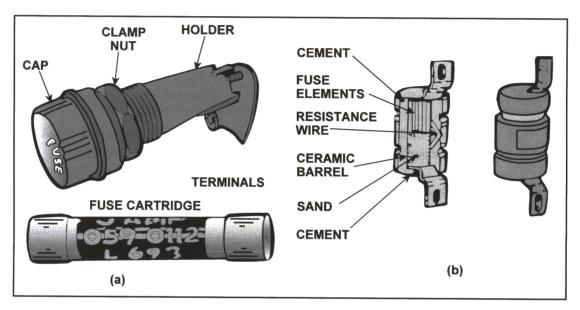


Figure 3.1. Typical Fuses, (a) A Light Duty Circuit Fuse. (b) A High Rapturing Capacity Fuse.

The latter type element is generally used in heavy duty circuits, the zinc strip being cut to a specified width.

A fuse operates when the current flowing through it is sufficient to melt the wire or strip element, the time taken varying inversely with the current.

All fuses are rated at a specific current value, i.e. the rating indicates the current they will carry continuously or intermittently without unduly heating up or deteriorating.

The rating of a fuse for a particular circuit is such that it is not less than the normal current flowing in the circuit, but that it operates ('blows') at a current level below the safety limit of the equipment or cable used.

DC ELECTRICS

For this reason only the specified fuse should be used in a particular circuit. The diagram shows typical aircraft fuses, the ratings can vary between .5 and 500 amps, the higher ratings being limited to the HRC or current limiter types.

Fuses are made of a type of wire which has a low melting point, and when it is placed in series with the electrical load it will melt, blow or rupture when a current of higher value than its ampere rating is placed upon it.

Fuses are rated in 'amps'.

A blown fuse may be replaced with another of the correct rating once only. If it blows again when switching on there is a defect in the system and the fuse must not be changed again until the circuit has been investigated.

3.5 SPARE FUSES.

The carriage of spare fuses is mandatory, the quantity of spares being at least 10% of the number of each rating installed, with a minimum of 3 of each.

3.6 HIGH RUPTURE CAPACITY (HRC) FUSES.

The high rupture capacity (HRC) fuse is an improvement on the cartridge type fuse. It is used mainly for high current rated circuits.

The body is a ceramic material of robust construction and has one or more element holes. The element holes are filled with powdered marble or clean quartz sand. The end caps are of plated brass or copper.

The HRC has the following advantages over the normal glass cartridge type;-

- a) more accurate operation.
- b) operates without flame.
- c) does not deteriorate with age, i.e. sagging etc.
- d) is more robust.
- e) operates rapidly.
- f) is not affected by ambient temperature.

3.7 DUMMY FUSES.

Aircraft electrical circuits which are not in use will have dummy fuses fitted. If it is necessary to isolate a particular circuit by the removal of the fuse in order that the system be made 'safe' or for work to be carried out, a dummy fuse or fuse holder should replace the fuse which has been removed.

To distinguish the dummy fuse, a red streamer is attached to it.

Dummy fuse links are manufactured to standard fuse dimensions from red plastic, the centre portion being square in section with corrugated sides to facilitate identification.

Services protected by circuit breakers are made safe in a similar manner, a warning flag or plate is clipped to the tripped circuit breaker, indicating that the service has been rendered safe for servicing.

3.8 CURRENT LIMITERS

Current limiters, as the name suggests, are designed to limit the current to some pre-determined amperage value.

They are also thermal devices, but unlike ordinary fuses they have a **high melting point**, so that their time/current characteristics permit them to carry a considerable overload current before rupturing.

For this reason their application is confined to the protection of heavy-duty power distribution circuits. The output of a Transformer Rectifier Unit would be a prime location for a current limiter to be used.

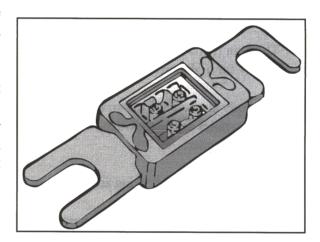


Figure 3.2 A Typical Current Limiter (An Airfuse).

A typical current limiter (manufactured under the name of 'Airfuse') is illustrated in Figure 3.2. it incorporates a fusible element which is, in effect, a single strip of tinned copper, drilled and shaped at each end for form lug type connections, with the central portion 'waisted' to the required width to form the fusing area.

The central portion is enclosed by a rectangular ceramic housing, one side of which is furnished with an inspection window which, depending on the type, may be glass or mica.

3.9 CIRCUIT BREAKERS

Circuit breakers combine the function of fuse and switch and can be used for switching circuits on and off in certain circumstances.

They are fitted to protect equipment from damage resulting from overload, or fault conditions. The design and construction of circuit breakers is wide and varied.

Generally, the circuit breaker incorporates an automatic thermo-sensitive tripping device and a manually or electrically operated switch.

Some electrical operated circuit breakers may also include electromagnetic and reverse current tripping devices.

The smaller type single button circuit breakers, shown in the diagram, range from 5 amps to 45 amps, whereas the larger reverse current circuit breakers can be rated up to 600amps.

Figure 3.3 shows two typical circuit breakers, the single push pull button type has a white marker band to assist in identifying a 'tripped' circuit breaker amongst a panel of many.

The circuit breaker at (b) is fitted with a "manual trip" button and is more usually associated with a heavy duty circuit.

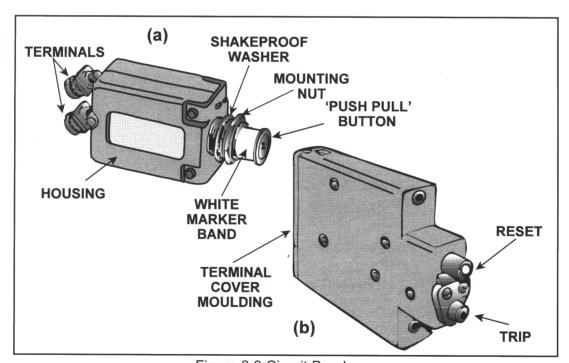


Figure 3.3 Circuit Breakers.

DC ELECTRICS

CIRCUIT PROTECTION AND CAPACITORS

Circuit breakers are common on the flight deck of modern aircraft and can be categorised as either;-

- a) a Non-Trip Free Circuit Breaker, or
- b) a Trip Free Circuit Breaker.

The **non-trip free circuit breaker** may be held in under fault conditions and the circuit will be made, this is clearly dangerous.

The **Trip free** circuit breaker if held in under the same circumstances the circuit can **not** be made.

Pressing the re-set button will reset either circuit breaker if the fault has been cleared.

3.10 REVERSE CURRENT CIRCUIT BREAKERS.

These circuit breakers are designed to protect power supply systems and associated circuits against fault currents reversing against the normal current direction of flow of a magnitude greater than those at which cut-outs normally operate.

They are furthermore designed to remain in a "locked-out" condition to ensure complete isolation of a circuit until a fault has been cleared.

3.11 CAPACITORS

Introduction:

A capacitor can perform three basic functions:

- 1. Store an electrical charge by creating an electric field between the plates.
- 2. Will behave as if it passes Alternating Current
- 3. Blocks Direct Current flow

Construction:

In its simplest form a capacitor consists of two metal plates separated by an insulator called a **dielectric**. Wires connected to the plates allow the capacitor to be connected into the circuit.

Figure 3.4 shows the construction of a simple capacitor

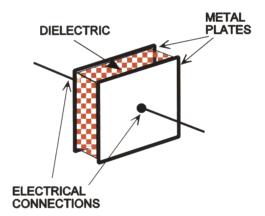


Figure 3.4

Symbols:

Figure 3.5 shows the electrical circuit symbols for various capacitors. With the polarised capacitor it is important to connect the positive terminal to the positive supply. Non-polarised types can be connected either way round



Figure 3.5 CAPACITOR SYMBOLS

3.12 CAPACITANCE

The capacitance (C) of a capacitor measures its ability to store an electrical charge. The unit of capacitance is the **FARAD** (F). The farad is subdivided into smaller, more convenient units.

1 micro farad $(1\mu F)$	= 1 millionth of a farad	$= 10^{-6} F$
1 nano farad (1nF)	= 1 thousand millionth of a farad	$= 10^{-9} \mathrm{F}$
1 picofarad (1pF)	= 1 millionth millionth of a farad	$= 10^{-12} F$

Factors Affecting Capacitance:

- a) Area of the plates a large area gives a large capacitance
- b) Distance between the plates a small distance gives a large capacitance
- Material of the dielectric different materials give different values of capacitance eg. paper, mica, air, fuel. The value of the dielectric is referred to as the dielectric constant (k). For example, waxed paper has a k value of about 3, whereas air has a k of 1. So a capacitor having waxed paper as its dielectric would have 3 times the capacitance of the same capacitor having air as its dielectric.

Working Voltage:

This is the largest voltage DC or Peak AC which can be applied across the capacitor. It is often marked on the case of the capacitor and if it is exceeded the dielectric may break down and permanent damage result.

3.13 CAPACITOR IN A DC CIRCUIT

Figure 3.6 shows a capacitor in series with a battery and a switch. If the switch is closed electrons are pushed by the battery on to plate Y building up a negative charge. This charge exerts a repelling force across the dielectric which causes electrons to leave the plate X and be attracted to the positive plate of the battery. While this charging action is taking place electrons are passing through the connecting wires **but no current flows through the dielectric.**

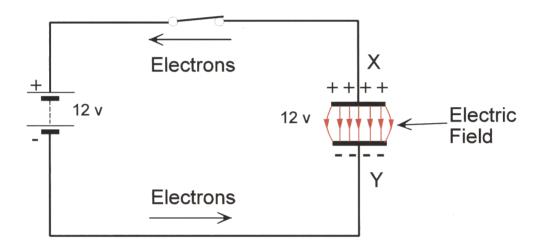


Figure 3.6

After a short time the difference in charge between the plates results in a potential difference existing between the plates. The flow of electrons will reduce and stop when the potential difference between the plates is equal to the supply voltage. The capacitor is now fully charged, current has stopped flowing, the plates are said to be charged and there exists an **electric field** between the plates. The **capacitor is now blocking DC flow.**


If the switch is opened and the capacitor is disconnected from the battery it holds its charge: a capacitor stores electrical energy by the formation of an electric field between the plates. The capacitor will only discharge if it is now connected to an external circuit.

3.14 CAPACITOR IN AN AC CIRCUIT

Figure 3.7 shows the battery replaced with an Alternating Current Supply. A light bulb is placed in series with the supply and the capacitor.

As the terminals X and Y are now changing from positive to negative at a rate depending on the frequency of the supply, current is first flowing in one direction, reversing and flowing in the opposite direction. The capacitor is charging in one direction, discharging and then charging in the opposite direction. This process continues until the supply is disconnected. The bulb will be continuously ON. Current flows in the wires but no current flows through the dielectric.

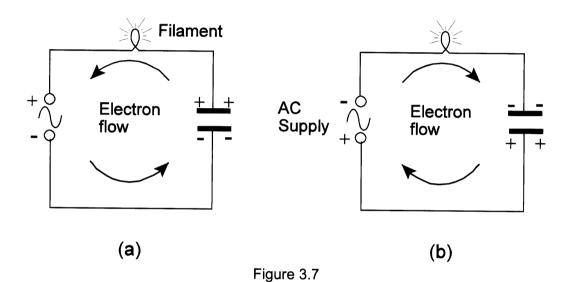Therefore: A capacitor appears to pass AC



3.15 CAPACITORS IN PARALLEL

Capacitors connected in parallel are effectively increasing the area of the plates. The total capacitance C_t can be found by adding the individual capacitances:

$$C_T = C_1 + C_2$$
 etc


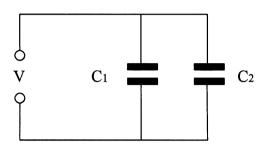


Figure 3.8

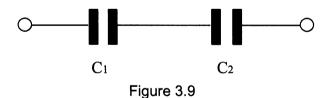3.16 CAPACITORS IN SERIES

Capacitors in series have effectively increased the distance between the plates and therefore the total capacitance has decreased. The total capacitance is found by using the formula for resistances in parallel:

$$\underline{1} = \underline{1} + \underline{1}
C_T C_1 C_2 etc$$



CIRCUIT PROTECTION AND CAPACITORS

CIRCUIT BREAKERS

ELECTRICS

- 1. In a circuit fitted with a non trip free circuit breaker if a fault occurs and persists:
 - a) if the reset button is depressed and held in, the circuit will be made.
 - b) the trip button may be pressed to reset, but not permanently.
 - c) a non trip free circuit breaker can never be by-passed.
 - d) the reset button may be pressed to make the circuit permanent.
- 2. A trip-free circuit breaker that has tripped due to overload:
 - a) can be reset and held in during rectification.
 - b) can never be reset.
 - c) can be reset after overhaul.
 - d) maybe reset manually after fault has been cleared.
- 3. Circuit breakers and fuses
 - a) are used in DC circuits only
 - b) are used in AC or DC circuits
 - c) are used in AC circuits only
 - d) are used in low current circuits only
- 4. A trip-free circuit breaker is one which:
 - a) cannot be reset by holding the lever in while the fault persists.
 - b) can be reset by holding the lever in while the fault persists.
 - c) must be held in during checks to find faults.
 - d) can be by passed.
- 5. If the reset button is pressed in the trip-free circuit breaker, the contacts with the fault cleared will:
 - a) be made and kept made.
 - b) only be made if there is a fuse in the circuit.
 - c) reset itself only after a delay of 20 seconds.
 - d) not be made and the reset will remain inoperative.

- 6. A circuit breaker is a device for:
 - a) controlling rotor movement only.
 - b) isolating the service on overload.
 - c) isolating the battery when using the ground batteries.
 - d) earthing the magnetos when switching off.
- 7. A non-trip free circuit breaker is:
 - a) one which can make a circuit in flight by pushing a button.
 - b) a wire placed in a conductor which melts under overload.
 - c) another type of voltage regulator.
 - d) an on-off type tumbler switch.
- 8. A non-trip-free circuit breaker that has tripped due to overload:
 - a) can never be reset.
 - b) can be reset but must not be held in.
 - c) can be reset and held in if necessary.
 - d) cannot be reset while the fault is still on and must be by passed to make the circuit in an emergency.
- 9. A thermal circuit breaker works on the principle of:
 - a) differential expansion of metals.
 - b) differential thickness of metals.
 - c) differential density of metals.
 - d) differential pressure of metals.
- 10. Circuit breakers are fitted in:
 - a) series with the load.
 - b) parallel with the load.
 - c) across the load.
 - d) shunt with the load.

FUSES

ELECTRICS

- 1. A fuse is said to have blown when:
 - a) an excess current has burst the outer cover and disconnected the circuit from the supply.
 - b) the circuit is reconnected.
 - a current of a higher value than the fuse rating has melted the conductor and disconnected the circuit from the supply.
 - d) the amperage has been sufficiently high to cause the fuse to trip out of its holder and has therefore, disconnected the circuit from the supply.
- 2. In a fused circuit the fuse is:
 - a) in parallel with the load.
 - b) in series with the load.
 - c) in the conductor between generator and regulator.
 - d) only fitted when loads are in series.
- 3. Overloading an electrical circuit causes the fuse to 'Blow'. This:
 - a) increases the weight of the insulation.
 - b) fractures the fuse case.
 - c) disconnects the fuse from its holder.
 - d) melts the fuse wire.
- 4. What must be checked before replacing a fuse:
 - a) the ohms of the circuit.
 - b) the amps being used in the circuit.
 - c) the amps capacity of the consuming device in the circuit.
 - d) the correct fuse volt or watts rating.
- 5. The size of fuse required for an electrical circuit whose power is 72 watts and whose voltage is 24 volts is:
 - a) 24 amps
 - b) 10 amps
 - c) 5 amps
 - d) 15 amps

DC ELECTRICS

CIRCUIT PROTECTION AND CAPACITORS

- 6. When selecting a fuse for an aircraft circuit the governing factor is:
 - a) the voltage of the circuit.
 - b) cable cross sectional area.
 - c) resistance of the circuit.
 - d) power requirements of the circuit.
- 7. A fuse in an electrical circuit is 'Blown' by:
 - a) cooler air.
 - b) the breaking of the glass tube.
 - c) excess voltage breaking the fuse wire.
 - d) excess current rupturing the fuse wire.
- 8. A fuse is used to protect an electrical circuit, it is:
 - a) of low melting point.
 - b) of high capacity.
 - c) of high melting point.
 - d) of low resistance.
- 9. Fuses:
 - a) protect the load.
 - b) protect the cable.
 - c) protect the generator.
 - d) protect both the circuit cable and load.
- 10. A current limiter:
 - a) is a fuse with a low melting point.
 - b) is a circuit breaker.
 - c) is a fuse with a high melting point.
 - d) is a fuse enclosed in a quartz or sand.

CHAPTER FOUR - BATTERIES

Contents

		Page
4.1	BATTERIES 1	1.4 - 1
4.2	SECONDARY CELLS	1.4 - 2
4.3	LEAD ACID BATTERY	1.4 - 3
4.4	ALKALINE BATTERY (NICKEL CADMIUM, NI-CAD)	1.4 - 6
4.5	BATTERY CHECKS	1.4 - 7
4.6	BATTERY CHARGING.	1.4 - 8
4.7	SECONDARY BATTERIES SUMMARY	1.4 - 9
SELF A	ASSESSMENT QUESTIONS	4 - 11

4.1 BATTERIES

The purpose of a battery in an aircraft is to provide an emergency source of power when the generator is not running and to provide power to start the engine.

A battery is made up of a number of **cells** which convert **chemical energy** into **electrical energy** by a transfer of electrons from one material to another causing a potential difference between them. During the transfer of electrons the chemical composition of the two materials changes.

Primary Cell

A primary cell consists of two electrodes immersed in a chemical called an electrolyte. The electrolyte encourages electron transfer between the electrodes until there is a potential difference between them. When the electron transfer ceases the cell is fully charged and the potential difference is approximately 1.5 Volts between the two electrodes.

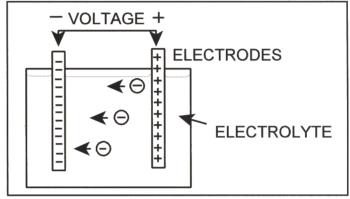


Figure 4.1. A Primary Cell

When the positive and negative terminals are connected to an external circuit electrons flow from the negative terminal to the positive terminal through the circuit. At the same time more electrons are allowed to transfer inside the cell from the positive electrode to the negative electrode. As this circulation of electrons continues the negative electron slowly dissolves in the electrolyte until it is eventually eaten away and the cell is then "dead" and is discarded. Primary cells cannot be recharged.

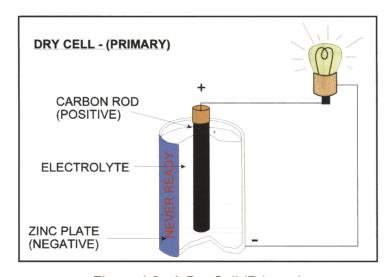


Figure 4.2. A Dry Cell (Primary)

4.2 SECONDARY CELLS

Secondary cells work on the same principle as primary cells but the chemical energy in the cell can be restored when the cell has been discharged by passing a "charging current" through the cell in the reverse direction to that of the discharge current. In this way the secondary cell can be discharged and recharged many times over a long period of time

During recharging electrical energy is converted into chemical energy which is retained until the cell is discharged again.


The **Capacity** of a cell is a measure of how much current a cell can provide in a certain time. Capacity is measured in **Ampere hours (Ah)** and is determined by the area of the plates, the bigger the cell the greater its capacity.

A cell with a capacity of 80 Ah should provide a current of 8A for 10 hours, or 80 A for 1 hr. Theoretically that should be true but in practice the capacity will reduce as the rate of discharge is increased. Capacity is normally measured at the 1 hour rate.

A single cell battery may be used on its own or cells may be connected 'in series' or 'in parallel' depending upon the voltage and capacity required

For cells in series the positive terminal of one cell is connected to the negative terminal of the next and so on. The total voltage is the sum of the individual cell voltages. But the capacity is that of one cell.

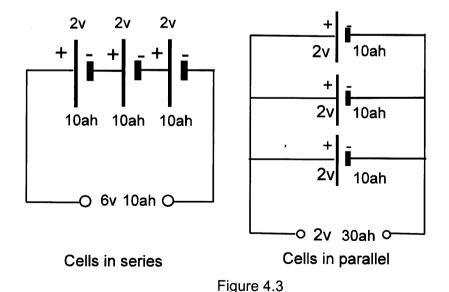For cells in parallel the positive terminals are joined together and the negative terminals are joined together. The total voltage is that of one cell but the capacity is the sum of the individual cell capacities.



1.4-2

4.3 LEAD ACID BATTERY

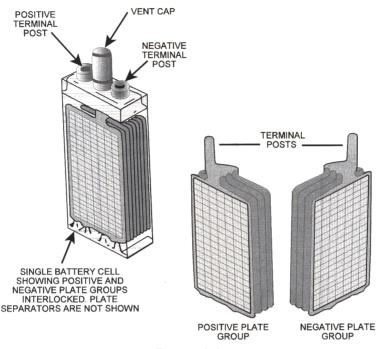


Figure 4.4

One of the most common types of secondary cell is the Lead Acid cell.

The active material of the positive plate is **lead peroxide** and the negative plate is **spongy lead**, both plates are immersed in an electrolyte solution of **water and sulphuric acid**. The container is glass or hard plastic with a filler cap to allow replenishment of distilled water, which is lost through evaporation during use. A vent hole in the cap allows the escape of hydrogen gas, which is produced when the cell is working

The state of charge of a lead acid cell can be determined by measuring the strength of the electrolyte solution. This is done with a hydrometer which measures the specific gravity. A fully charged cell will have a specific gravity of 1.27, a discharged cell will have a specific gravity of 1.17.

When the cell is connected to an external circuit and current is flowing lead sulphate is formed at both plates and the specific gravity will fall as the acid becomes weaker. When the SG has fallen to 1.17 and the voltage to 1.8 volts the cell should be recharged.

To charge a cell it is connected to a battery charger which applies a slightly higher voltage to the cell and causes current to flow in the reverse direction through the cell. While this is happening the lead sulphate which had been deposited on the plates is removed and the SG of the electrolyte rises to 1.27. The voltage 'on load' should have returned to just above 2V.

When charging a lead-acid battery it is important that the rate of charge is controlled. Charging too quickly can cause 'gassing' and evaporation to occur which may lead to boiling the battery dry and causing damage to the plates.

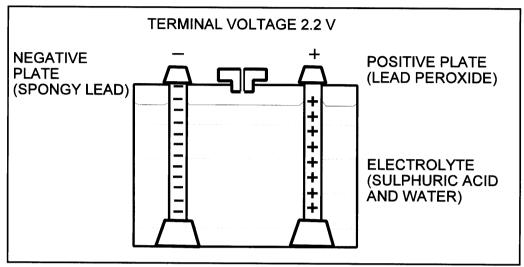


Figure 4.5. A Lead Acid Secondary Cell.

The specific gravity of the electrolyte is an indication of the battery's state of charge or serviceability. The value of the specific gravity is checked using a **hydrometer**. The level of the electrolyte is maintained just above the top of the plates by topping up with distilled water. Loss of water is caused by gassing at the plates when fully charged.

The on load voltage of each cell of a lead acid battery is 2 volts.

The off-load voltage of each cell of a lead acid battery is 2.2 volts.

Electrolytes are highly corrosive and if spilled in aircraft can cause extensive damage.

The neutralising agent to be used for an acid electrolyte is a sodium bicarbonate solution.

The performance of a battery is affected by temperature. In low temperatures the rate of discharge is decreased because of higher internal resistance. In warm temperatures the battery rate of discharge will increase. In general the battery performs better in warm temperatures (just like your car battery). As a lead acid battery discharges the specific gravity of the electrolyte reduces. In freezing temperatures with a discharged battery there is a risk of the electrolyte freezing. It is therefore important to maintain the battery in a fully charged state during winter operations.

Fig 4.6 shows free liquid type of lead acid battery where the electrolyte is in liquid form and Fig.4.7 shows an absorbed liquid type of lead acid battery where the electrolyte is absorbed into the active materials in the plates making it less prone to spillage.

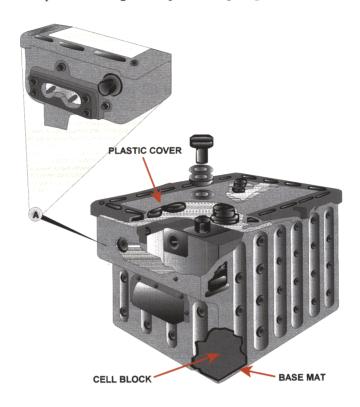


Figure 4.6. Lead Acid Battery (Free Liquid Type).

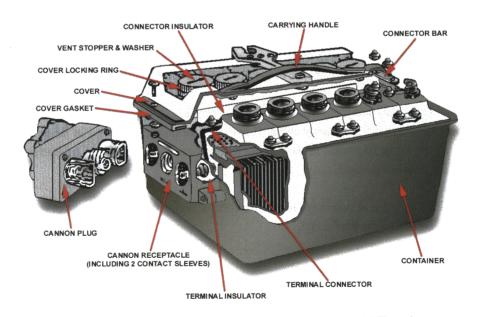


Figure 4.7. Lead Acid battery (Absorbed Liquid Type)

4.4 ALKALINE BATTERY (NICKEL CADMIUM, Ni-Cad)

Lead acid batteries are still used in some smaller aircraft but have been largely superceded by **Nickel Cadmium** (alkaline type) batteries. These use different materials for their plates and electrolyte. The plates are **nickel oxide** and **cadmium** and the electrolyte is **potassium hydroxide**. The Specific Gravity (S.G.) of the electrolyte is 1.240 - 1.300

The on load voltage of one cell is about 1.2 volts.

Unlike the lead acid battery, the relative SG of the nickel-cadmium battery electrolyte does not change and the voltage variation from "fully charged" to "fully discharged" is very slight. The only way to determine the state of charge is to carry out a measured discharge test i.e. a capacity test.

The terminal voltage remains substantially constant at 1.2V throughout most of the discharge. Due to its low internal resistance it is also capable of supplying high current during its discharge cycle and low current during recharging without violent fluctuations of terminal voltage.

NiCad batteries have a low thermal capacity, the heat generated in certain conditions is faster than it can dissipate, so causing a rapid increase in temperature.

This has the effect of lowering the effective internal resistance thus allowing an ever increasing charging current, which, unless checked, leads to the total destruction of the battery.

This condition is known as a **thermal runaway**, and can cause so much heat that the battery may explode. For this reason the charging of the battery must be closely monitored and includes some safety features

A built-in thermal switch monitors the temperature and operates on a pre-set value of temperature. This effectively isolates the battery from the charging source until a reduction in temperature reverts the switch back to its normal position. Associated with the temperature switch may be an indicator light on the flight deck to alert the pilot.

The nickel cadmium battery, however, is more robust and can hold a constant terminal voltage much better during the discharge cycle. It is therefore much preferred in large modern aircraft because in the event of a total failure of the aircraft generators the Ni-Cad battery will provide a much more stable voltage.

Figure 4.8 is a graphical representation of a comparison of the discharge voltage of a lead acid against a Ni-cad during discharge.

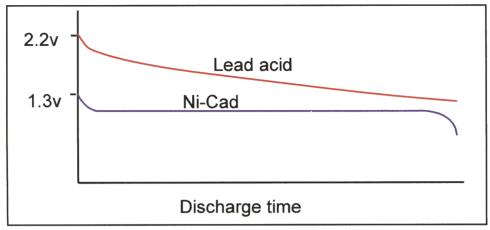


Figure 4.8

4.5 BATTERY CHECKS

The Capacity of a Battery is the product of the load in amperes that the manufacturers state it will deliver, and the time in hours that the battery is capable of supplying that load.

The capacity is measured in ampere hours (A/H).

A 40 A/H battery when discharged at the 1 hour rate should supply 40 amps for the 1 hour. This is known as the **'rated load'**. Alternatively the battery could supply 4 amps for 10 hours at the 10 hour rate.

Actual Capacity is determined by the battery's deterioration in service. If a 60 A/H battery when discharged at the 1 hour rate lasts only for .7 hour, or 42 mins, then the actual capacity is 70% of its rated capacity. In other words, the battery is only 70% efficient.

A Capacity Test, a test to determine the actual capacity of aircraft batteries, is carried out every 3 months, and the efficiency must be 80% or more for the battery to remain in service.

This capacity will ensure that essential loads can be supplied for a period of 30 minutes following a generator failure.

Loads would include; - attitude information, essential communication equipment, lighting, pitot heat, plus any other services necessary for continued safe flight, or loads which cannot easily be shed.

Spare batteries will be held ready for use in the electrical workshop. Lead acid batteries are stored in a charged state to prevent deterioration of the battery by sulphation, (para 4.3). Ni Cad batteries can be stored in a discharged state with no detrimental effect to the battery and therefore have a longer storage life or 'shelf life'.

The **On-load Check** is carried out by applying the rated load to the battery circuit for a short period of time, during which time the battery voltmeter reading must remain constant and not fall below a stated value. Modern aircraft use times as low as 10 - 20 seconds with the rated load selected.

The pilots Pre-Flight check of a battery may include comparing the 'on load' voltage with the 'off load' voltage to give an indication of the state of charge of the battery.

If the battery is not supplying any load then it is likely to show its nominal voltage, if the battery is then loaded up by switching on selective loads (eg. pitot heater, landing lights, blower motors) and the voltage is maintained then the battery is in a good state of charge. If the voltage falls below a stated value within a time limit determined by the manual then the battery is in a low state of charge and should be replaced.

4.6 BATTERY CHARGING

A Constant Voltage Charging system is employed with most lead acid batteries to maintain the battery in a fully charged condition during flight. With this system the output voltage of the generator is maintained constant at 14 volts for a 12 volt battery and 28 volts for a 24 volt battery.

ie. The generator voltage exceeds the battery voltage by 2 volts for every 12 volts of battery potential.

With alkaline batteries which are susceptible to thermal runaway it may be that a **constant current charging** system is employed by a dedicated battery charger which monitors battery temperature and voltage. Some charging systems use a method known as pulse charging, and once the battery is up to 85% capacity, the battery charger delivers short pulses of charging current.

NOTE:

After starting an engine using the aircraft's battery, whether it is a lead acid battery or an alkaline battery, the generator, when it is on line, recharges that battery.

This is indicated by the high initial reading on the generator's ammeter or the battery ammeter. This reading should quickly reduce as the battery is recharged, but if the charge rate increases, or remains high, it could be an indication of a faulty battery.

A high charge rate could result in a battery overheating and subsequent damage.

BATTERIES DC ELECTRICS

SECONDARY BATTERIES SUMMARY 4.7

Figure 4.9 is a summary of secondary batteries.

Secondary be Summary.	atteries:	CHAF	rged [DISCHARGED	
	POSITIVE	NEGATIVE	ELECTROLYTE	SPILLAGE	S.G.
LEAD-ACID	lead peroxide	spongy lead	sulphuric acid	Sodium 1.270 bicarbonate + water	1.270
	lead sulphate	lead sulphate	weak sulphuric acid		
ALKALINE	nickel oxide	cadmium	potassium hydroxide / distilled water	Boric acid	1.240 -
	nickel hydroxide	cadmium hydroxide	potassium		1.300

Figure 4.9 Secondary Batteries Summary

BATTERIES 1

- 1. Battery voltage is tested with:
 - a) a megometer.
 - b) a voltmeter on rated load.
 - c) an ammeter with a rated voltage.
 - d) a hygrometer.
- 2. Two 12V 40 amp/hour batteries connected in series will produce:
 - a) 12V 80 amp/hr
 - b) 12V 20 amp/hr
 - c) 24V 80 amp/hr
 - d) 24V 40 amp/hr
- 3. Two 12V 40 amp/hour batteries connected in parallel will produce:
 - a) 12V 80 amp/hr
 - b) 24V 80 amp/hr
 - c) 12V 20 amp/hr
 - d) 24V 40 amp/hr
- 4. A battery capacity test is carried out:
 - a) 6 monthly
 - b) 2 monthly
 - c) 3 monthly
 - d) every minor check
- 5. An aircraft has three batteries each of 12 volts with 40 amp/hr capacity connected in series. The resultant unit has:
 - a) a voltage of 36 and a capacity of 120 amp/hr.
 - b) a capacity of 120 amp/hr and a voltage of 12.
 - c) a capacity of 36 amp/hr and 120 watts.
 - d) a voltage of 36 and a capacity of 40 amp/hr.

6. An aircraft has a battery with a capacity of 40 amp/hr. Assuming that it will provide its normal capacity and is discharged at the 10 hour rate:

- a) it will pass 40 amps for 10 hrs.
- b) it will pass 10 amps for 4 hrs.
- c) it will pass 4 amps for 10 hrs.
- d) it will pass 40 amps for 1 hr.
- 7. Battery capacity percentage efficiency must always be:
 - a) 10% above saturation level
 - b) above 70%
 - c) above 80%
 - d) above 90%
- 8. The method of ascertaining the voltage of a standard aircraft lead-acid battery is by checking:
 - a) the voltage on open circuit.
 - b) the current flow with a rated voltage charge.
 - c) the voltage off load.
 - d) the voltage with rated load switched ON.
- 9. A battery is checked for serviceability by:
 - a) using an ammeter.
 - b) measuring the specific gravity of the electrolyte.
 - c) a boric acid solution.
 - d) using an ohmmeter.
- 10. In an AC circuit:
 - a) the battery is connected in series.
 - b) a battery cannot be used because the wire is too thick.
 - c) a battery cannot be used because it is DC.
 - d) only NICAD batteries can be used.

BATTERIES 2

		2 2			
1.	The s	The specific gravity of a fully charged lead acid cell is:			
	a)	1.270			
	b)	1.090			
	c)	1.120			
	d)	0.1270			
2.	The 1	The nominal voltage of the lead acid cell is:			
	a)	1.2 volts			
	b)	1.5 volts			
	c)	1.8 volts			
	d)	2.0 volts			
3.	A lea	A lead acid battery voltage should be checked:			
	a)	on open circuit			
	b)	using a trimmer circuit			
	c)	with an ammeter			
	d)	on load			
4.	In an	In an aircraft having a battery of 24 volts nominal and fully charged the voltmeter would read			
	a)	22 volts			
	b)	24 volts			
	c)	26 volts			
	d)	28 volts			
5.	The	system used to maintain aircraft batteries in a high state of charge is the:			
	a)	constant current system.			
	b)	constant load system.			
	c)	constant resistance system.			
	d)	constant voltage system.			
6.	If yo	If you connect two identical batteries in series it will:			
	a)	double the volts and halve the capacity.			
	b)	reduce the voltage by 50%.			
	c)	double the volts and leave the capacity the same.			
	d)	double the volts and double the amps flowing in a circuit with twice the resistance.			

- 7. The nominal voltage of an alkaline cell is:
 - a) 2.2 volts
 - b) 1.8 volts
 - c) 1.2 volts
 - d) 0.12 volts
- 8. The specific gravity of a fully charged alkaline cell is:
 - a) 0.120 0.130
 - b) 1.160
 - c) 1.240 1.30
 - d) 1.800
- 9. The electrolyte used in the lead acid cell is diluted:
 - a) hydrochloric acid.
 - b) sulphuric acid.
 - c) boric acid.
 - d) potassium hydroxide.
- 10. The electrolyte used in an alkaline battery is diluted:
 - a) a saline solution.
 - b) sulphuric acid.
 - c) cadmium and distilled water.
 - d) potassium hydroxide solution.

DC ELECTRICS BATTERIES

BATTERIES 3

1	T1 1	. C1 1	1 11 1	4 1	T1 X7-14	D-44:
1.	I ne number	of lead acid	l cells required	to make up a	a I weive voit	Battery is:

- a) 8
- b) 12
- c) 6
- d) 10
- 2. A Voltmeter across the terminals of a battery with all services off will indicate:
 - a) electromotive force.
 - b) resistance.
 - c) a flat battery.
 - d) residual voltage.
- 3. The voltage of a secondary cell is:
 - a) determined by the number of plates.
 - b) determined by the area of the plates.
 - c) determined by the diameter of the main terminals.
 - d) determined by the active materials on the plates.
- 4. The level of the electrolyte must be maintained:
 - a) just below the top plate.
 - b) above the plates level with the filler cap.
 - c) one inch below the top of the plates.
 - d) just above the top of the plates.
- 5. To top up the electrolyte add:
 - a) sulphuric acid.
 - b) distilled water.
 - c) sulphuric acid diluted with distilled water.
 - d) boric acid.
- 6. Non-spill vents are used on aircraft batteries to:
 - a) prevent spillage of electrolyte during violent manoeuvres.
 - b) stop spillage of the water only.
 - c) prevent the escape of gases.
 - d) prevent spillage during topping-up.

DC ELECTRICS BATTERIES

- 7. The capacity of a lead acid battery is:
 - a) determined by the area of the plates.
 - b) determined by the active materials on the plates.
 - c) determined by the size of the series coupling bars.
 - d) determined by the number of separators.
- 8. Acid spillage in an aircraft can be neutralised by using:
 - a) caustic soda.
 - b) soap and water.
 - c) soda and water.
 - d) bicarbonate of soda and water.
- 9. When the battery master switch is switched off in flight:
 - a) the generators are disconnected from the bus bar.
 - b) the ammeter reads maximum.
 - c) the battery is isolated from the bus bar.
 - d) the battery is discharged through the bonding circuit diodes.
- 10. When the generator is on line the battery is:
 - a) in parallel with the other loads.
 - b) in series with the generator.
 - c) in series when the generator is on line and is relayed when the generator is off line.
 - d) load sharing.

CHAPTER FIVE - MAGNETISM

Contents

		Page
5.1	MAGNETISM	1.5 - 1
5.2	TEMPORARY MAGNETS	1.5 - 2
5.3	PERMANENT MAGNETS	1.5 - 2
5.4	PERMEABILITY	1.5 - 3
5.5	MAGNETISM	1.5 - 3
5.6	THE MOLECULAR STRUCTURE OF MAGNETS	1.5 - 3
5.7	THE MAGNETIC EFFECT OF A CURRENT	1.5 - 3
5.8	THE CORKSCREW RULE	1.5 - 4
5.9	THE MAGNETIC FIELD OF A SOLENOID	1.5 - 6
5.10	THE RIGHT HAND GRASP RULE	1.5 - 6
5.11	THE STRENGTH OF THE FIELD OF A SOLENOID	1.5 - 6
5.12	SOLENOID AND RELAY	1.5 - 6
5.13	THE FORCES ON A CONDUCTOR WHICH IS CARRYING A CURRENT.	1.5 - 8
SELF A	ASSESSMENT OUESTIONS	1.5 - 9

5.1 MAGNETISM

A magnet has the following properties:

a) it will attract and pick up bits of iron and steel.

b) if freely suspended, it will come to rest pointing in a N-S direction.

c) a magnetic field (a region surrounding a magnet in which its magnetic effects can be detected)

If iron filings are sprinkled on to a sheet of paper which is placed over a magnet, the filings arrange themselves into a distinctive pattern. They trace out invisible lines of influence in the magnetic field. These lines are called **lines of flux or lines of force.**

We can give **direction** to the lines of flux by putting arrowheads on them in the direction a compass needle would point if placed in the magnetic field.

Lines of flux of a magnet emerge from the N pole and re-enter at the S pole.

Although, in diagrams, some lines of flux are shown incomplete they are in fact always continuous.

Lines of flux never cross.

When two magnets are brought close together their **resultant field** is modified by the fact that lines of flux cannot cross. Where lines of flux from the two magnets are in the same direction they reinforce one another and the flux density is increased.

When lines of flux from the two magnets oppose one another they tend to cancel each other out. Magnetic effects are most powerful at two points, usually near the ends of the magnet, called the **poles** of the magnet.

When a magnet is freely suspended and comes to rest, the end nearest to the earth's magnetic north pole is called the 'north seeking' or North (N) pole of the magnet. The other is the South (S) pole. If the N pole of a magnet is brought near the N pole of another magnet, the two poles repel each other. Similarly two S poles repel each other.

Attraction occurs between a N and a S pole.

LIKE POLES REPEL UNLIKE POLES ATTRACT

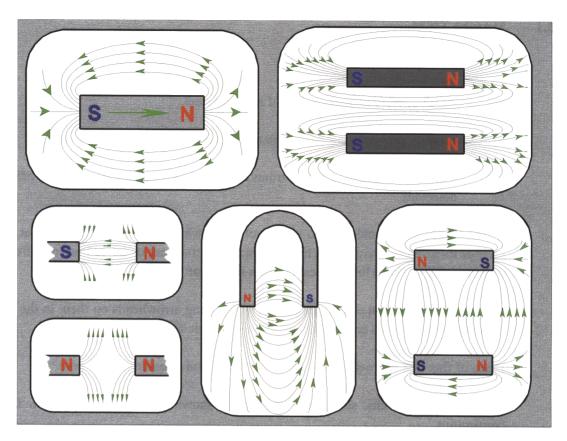


Figure 5.1. Flux Distribution

5.2 TEMPORARY MAGNETS

Temporary magnets are made from **soft iron** which is easily magnetised but readily loses its magnetic properties.

5.3 PERMANENT MAGNETS

Permanent magnets are made from hard alloy steels which are difficult to magnetise but retain their magnetism well.

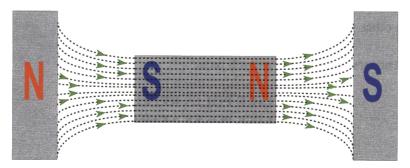


Figure 5.2. Temporary Magnet

5.4 PERMEABILITY

If an unmagnetised piece of soft iron is placed in a magnetic field, the lines of flux concentrate to flow through the iron. The iron itself becomes magnetised and produces additional lines of flux.

This property of increasing the flux density is called **permeability**.

If it is removed from the magnetic field, the soft iron loses most of its magnetism. Soft iron is said to have low magnetic **retentivity**. The little magnetism which remains is called its **residual magnetism**.

5.5 MAGNETISM

Magnetism may be destroyed by:

- a) heating the material.
- b) hammering the material.
- c) placing the material inside a solenoid which is supplied with an alternating current.

5.6 THE MOLECULAR STRUCTURE OF MAGNETS

In an unmagnetised piece of soft iron, the molecules tend to form closed chains. When the iron is magnetised, the magnetised molecules tend to line up with invisible lines of influence in the magnetic field which are called **the lines of flux**. When all the molecules line up, the magnet is said to be **saturated** and it cannot be magnetised further.

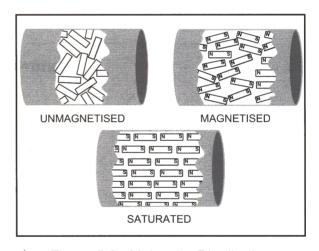


Figure 5.3. Molecular Distribution

5.7 THE MAGNETIC EFFECT OF A CURRENT

When a conductor carries a current, a magnetic field is set up about the conductor in the form of concentric lines of flux.

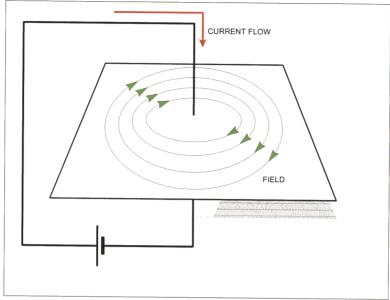


Figure 5.4. Magnetic Effect of a Current

5.8 THE CORKSCREW RULE

If a right-handed corkscrew is turned so as to move in the direction of the conventional current in the conductor, the direction of rotation of the corkscrew is the direction of the lines of flux.

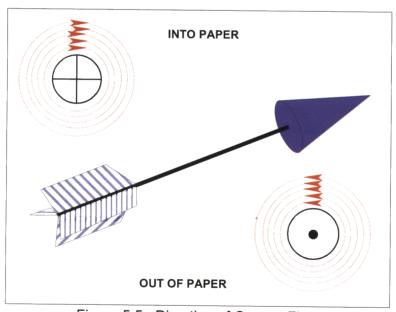


Figure 5.5. Direction of Current Flow

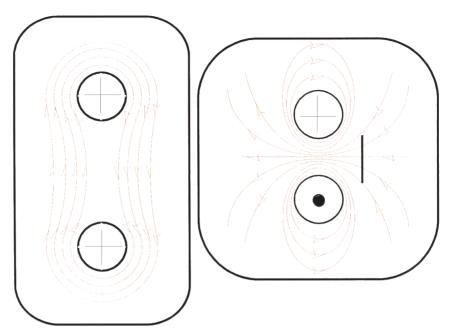


Figure 5.6. Combined Magnetic Fields

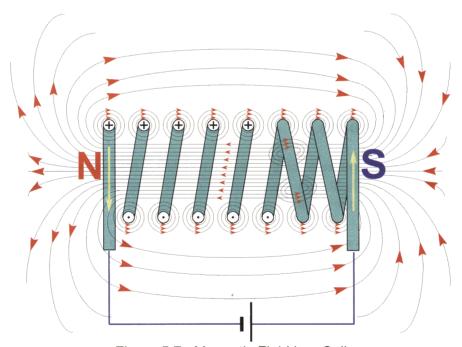


Figure 5.7. Magnetic Field in a Coil

5.9 THE MAGNETIC FIELD OF A SOLENOID

A **solenoid** (electromagnet) is a coil of a large number of turns of **insulated** wire. Between the coils the flux cancels out. The field pattern is similar to that of a bar magnet. The polarity of a solenoid may be found by the **Right Hand Grasp Rule**. Electromagnets and the principle of electromagnetism play an vital part in the operation and control of many aircraft electrical circuits.

5.10 THE RIGHT HAND GRASP RULE

If a solenoid is held in the right hand so that the fingers are curled round it pointing in the direction of the conventional current, the outstretched thumb points to the North pole of the solenoid.

5.11 THE STRENGTH OF THE FIELD OF A SOLENOID

The strength of the field of a solenoid can be increased by:

- a) increasing the number of turns on the coil.
- b) increasing the current.
- c) using a soft iron core.

When the current is switched off the magnetic field collapses leaving a little residual magnetism in the soft iron core.

5.12 SOLENOID AND RELAY

Solenoids and relays are nothing more than remotely controlled switches. By switching a small current from the flight deck a large current can be switched at the solenoid or relay. Eg. The starter solenoid in the starting circuit for a piston engine.

The solenoid has a moving core whereas the relay has a stationary core and an attracted armature.

The wires that form the coil of the solenoid or relay are insulated and have no physical or electrical contact with the circuit which is controlled by the contacts.

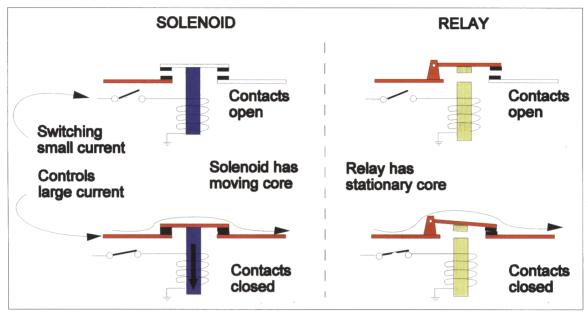


Figure 5.8. Solenoid and Relay

5.13 THE FORCES ON A CONDUCTOR WHICH IS CARRYING A CURRENT

If a current carrying conductor is placed between two magnets, the interaction of the two magnetic fields will produce a strong magnetic field on one side of the conductor and a weak magnetic field on the other. The resultant stronger force will cause the conductor to move.

This is the basic motor principle and the direction of movement can be deduced by using **Fleming's Left Hand Rule**. This will be explained in the section dealing with motors.

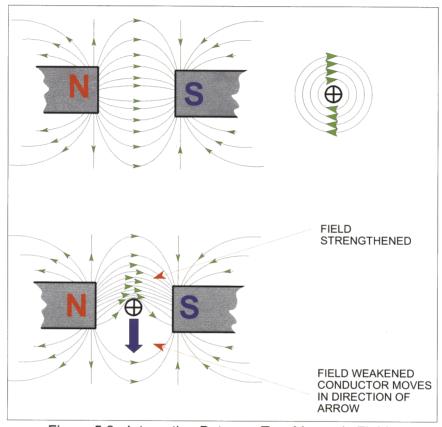


Figure 5.9. Interaction Between Two Magnetic Fields

MAGNETISM - SELF ASSESSMENT QUESTIONS

1. The area of force around a magnet is term	ed:
--	-----

- a) conductance.
- b) stable.
- c) magnetic resistance.
- d) magnetic field.
- 2. When a magnet is unable to accept any further magnetism it is termed:
 - a) reluctance.
 - b) saturation.
 - c) active.
 - d) reactance.
- 3. Permanent magnets are manufactured from:
 - a) steel.
 - b) plastic.
 - c) liquid.
 - d) glass.
- 4. Magnetic lines of force flow externally from:
 - a) one main line station to another.
 - b) the master station.
 - c) the north to the south pole.
 - d) in a random direction.
- 5. Which of the two poles has the greatest strength:
 - a) north seeking pole.
 - b) south seeking pole
 - c) both poles have the same strength.
 - d) the saturated pole.

- 6. Electromagnetism is a product of:
 - a) voltage.
 - b) current.
 - c) resistance.
 - d) engine resistance.
- 7. To increase electromagnetic force one would:
 - a) increase coil resistance.
 - b) reduce current flow.
 - c) lower EMF.
 - d) increase current flow.
- 8. If you bring two magnets together:
 - a) like poles will attract.
 - b) unlike poles will attract.
 - c) over heating will occur.
 - d) their magnetic fields will adjust to avoid overcrowding.
- 9. A soft iron core in an electromagnet:
 - a) increases flux density.
 - b) decreases flux density.
 - c) reduces arcing.
 - d) increases the lines of strength.

CHAPTER SIX - GENERATORS, ALTERNATORS AND MOTORS

Contents

	Page
6.1	ELECTROMAGNETIC INDUCTION & FLEMING'S RIGHT HAND RULE 1. 6 - 1
6.2	FARADAY'S LAW
6.3	LENZ'S LAW
6.4	SIMPLE GENERATOR 1. 6 - 4
6.5	SIMPLE DC GENERATOR
6.6	CHARACTERISTICS OF THE SERIES WOUND DC GENERATOR 1. 6 - 8
6.7	CHARACTERISTICS OF THE SHUNT WOUND DC GENERATOR 1. 6 - 9
6.8	A COMPOUND WOUND DC GENERATOR
6.9	FLASHING THE GENERATOR FIELD
6.10	ARMATURE REACTION 1. 6 - 11
6.11	COMMUTATOR RIPPLE
6.12	ALTERNATORS
6.13	VOLTAGE CONTROL
6.14	VOLTAGE REGULATOR OPERATION
6.15	LOAD SHARING CIRCUITS
6.16	OPERATION OF LOAD SHARING CIRCUIT
6.17	ELECTRIC MOTORS
6.18	FLEMING'S LEFT HAND RULE
6.19	PRACTICAL DC MOTOR
6.20	BACK E.M.F

6.21	SLOW START RESISTOR
6.22	COMMUTATION
6.23	SERIES WOUND MOTORS
6.24	SHUNT WOUND MOTORS
6.25	STARTER-GENERATOR SYSTEMS
6.26	ACTUATORS 1. 6 - 26
6.27	SOLENOID ACTUATORS
6.28	MOTOR ACTUATORS 1. 6 - 26
6.29	ROTARY ACTUATORS
6.30	LINEAR ACTUATORS
6.31	ACTUATOR BRAKES 1. 6 - 29
6.32	ACTUATOR CLUTCHES
6.33	VISUAL INDICATORS USED WITH LINEAR ACTUATORS 1. 6 - 29
6.34	VISUAL INDICATORS USED WITH ROTARY ACTUATORS 1. 6 - 29
6.35	INDICATOR LIGHTS
6.36	ELECTROMAGNETIC INDICATORS
6.37	ACTUATOR CONSTRUCTION
6.38	THE SPLIT FIELD SERIES ACTUATOR
6.39	THE SPLIT FIELD SERIES ACTUATOR OPERATION
	SELF ASSESSMENT QUESTIONS - GENERATOR THEORY 1. 6 - 33
	GENERATOR CONTROL
	ACTUATORS AND MOTORS

6.1 ELECTROMAGNETIC INDUCTION

Batteries are a good source of DC electricity by conversion of chemical energy, but they are not inexhaustible and will go flat after a period of time and need recharging. The primary source of electricity in an aircraft is always the generator or alternator.

Magnetism can be used to generate electricity by converting mechanical energy to electrical energy by **Electromagnetic Induction**.

If a conductor is moved in a magnetic field the conductor will 'cut through' the invisible lines of flux. When this happens an Electromotive Force EMF (voltage) is induced into the conductor as long as the conductor keeps moving. If the conductor stops the induced EMF ceases. It does not matter if the conductor or the magnetic field is moved as long as there is relative movement between the two.

If the conductor is connected to a complete circuit then a current will flow in the circuit in proportion to the induced EMF.

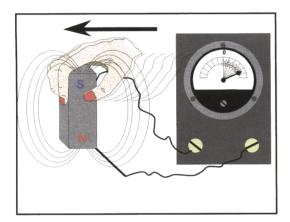


Figure 6.1 The Situation With Relative Motion Between the Magnet and the Coil

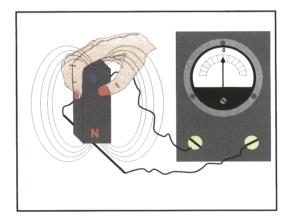


Figure 6.2 The Situation With the Magnet at Rest

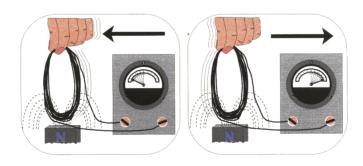


Figure 6.3 The Direction of the Relative Motion Determining the Direction of Current Flow

Fleming's Right Hand Rule

The direction of the current can be determined by Fleming's Right Hand Rule (Figure 6.4). To do so, align the first finger with the field from the North Pole to the South Pole. Point the thumb in the direction of rotation and the second finger will show the current direction.

For example, in Figure 6.4 the first finger is aligned with the field and the thumb is pointing upward in the direction of rotation of the red half of the armature. The second finger shows the current coming out of the red (negative) half of the armature. The blue half of the armature is moving downward therefore with the first finger still aligned with the field, if the hand is rotated through 180 degrees the second finger will show the current going into the armature.

If the direction of rotation or the field polarity is reversed, then so will be the direction of the current. However, if both are reversed the direction of current remains unchanged.

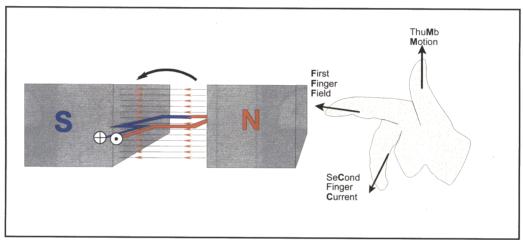


Figure 6.4 Fleming's Right Hand Rule

The magnitude of the induced voltage can be affected in three ways:

- a) The rate of cutting of lines of force. (Speed).
- b) The strength of the magnetic field. (Flux density).
- c) The number of turns of wire. (Larger coil).

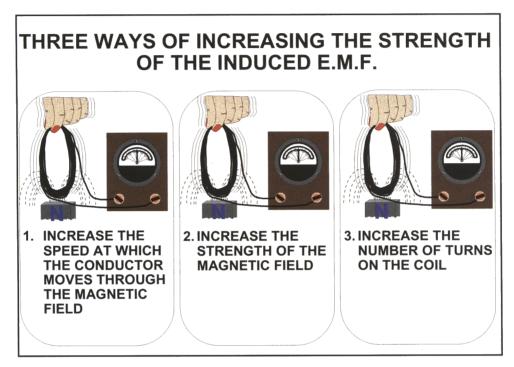


Figure 6.5 Factors Which Determine the Strength of the Induced EMF

6.2 FARADAY'S LAW

Faraday's law states:-

When the magnetic flux through a coil is made to vary, a voltage is set up. The magnitude of this induced voltage is proportional to the rate of change of flux.

6.3 LENZ'S LAW

Lenz's Law states:-

A change of flux through a closed circuit induces a voltage and sets up a current. The direction of this current is such that its magnetic field tends to oppose the change in flux.

This action produces a **back EMF.** (see Motors).

6.4 SIMPLE GENERATOR

The simplest form of a generator is a single loop of wire turning in a fixed magnetic field produced by a permanent magnet (figure 6.6). The closed circuit is made by attaching rotating slip rings to both ends of the loop which are in contact with stationery carbon brushes. Continuous contact between the slip rings and the brushes is maintained by spring pressure. The brushes are attached to cables which form a closed circuit.

The rotating loop is known as the armature.

The magnetic field is termed the field.

In a simple generator the armature rotates in the field.

An EMF is induced in the armature by electromagnetic induction.

The slip rings, brushes and cables complete the closed circuit and current will flow.

This type of generator produces an AC voltage in the armature and therefore an Alternating Current in the external circuit (first flowing one way, then changing direction and flowing the opposite way).

Figure 6.6 and 6.7 show the layout of a simple AC generator and the voltage output rising then falling then changing direction as the direction of movement of the armature sides reverse their direction through the magnetic field. The graphical view shows how a sine wave output of AC is generated. The maximum voltage is induced when there is maximum cutting of lines of flux, the position where no voltage is induced (position 1,3 and 5 figure 6.7), when the armature is moving parallel to the lines of flux, is known as the **neutral plane**.

A coil of wire can be wrapped around the two poles of the magnet. Passing a current through this coil will allow the magnetic field strength to be increased and so increase the voltage output of the generator. This is termed the **field coil** and is used to control the voltage to a fixed value irrespective of the generator speed.

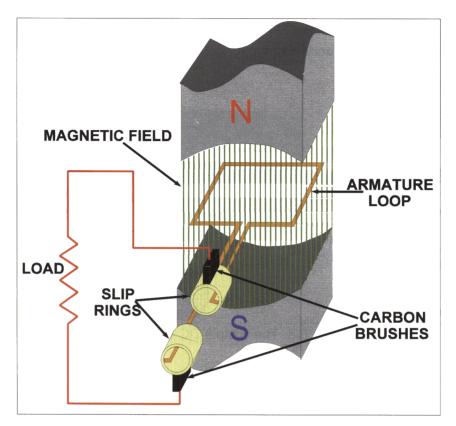


Figure 6.6 A Simple AC Generator

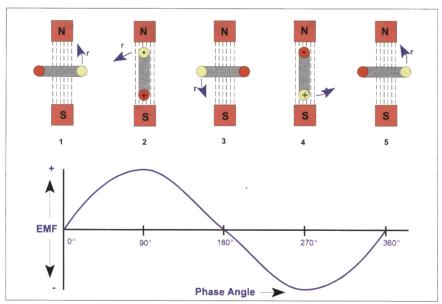


Figure 6.7 AC Generator Voltage Output

6.5 SIMPLE DC GENERATOR

To produce a DC output from the simple generator it is required to change the **AC EMF** induced into the armature to a **DC** output at the generator terminals. This is done by replacing the slip rings with a **Split Ring Commutator**.

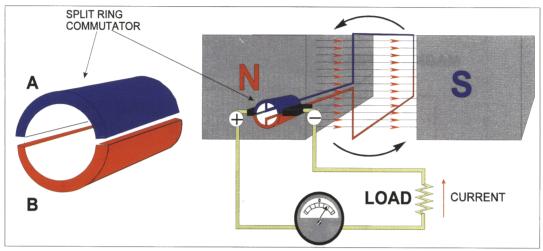


Figure 6.8 The Simple DC Generator

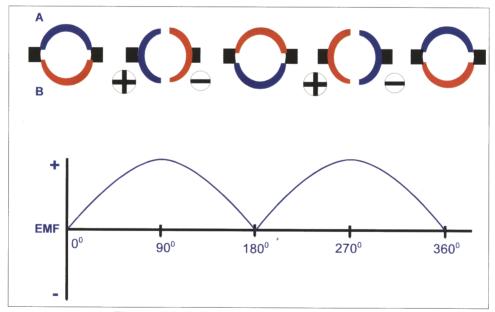


Figure 6.9 DC Generator Voltage Output

A split ring commutator is constructed of a single ring of conductive material with an insulator electrically separating each half of the ring. The armature is constructed with one end of the loop connected to one conductor of the split ring and the other end to the other one. The commutator rotates with the armature.

Electrical continuity from one side of the armature, through the armature circuit and to the other side of the armature is achieved by the use of carbon brushes.

As the armature rotates from 0^0 to 180^0 (figure 6.8) the positive brush is in contact with commutator segment A and the negative brush is in contact with commutator segment B. As it rotates from 180^0 to 360^0 the positive brush is in contact with commutator segment B and the negative brush is in contact with commutator segment A. The result is that every 180^0 the armature terminals are reversed. This causes the current and voltage in the armature circuit to become DC after commutation.

Layout of a generator system

In an aircraft system the generator, load and battery are all in parallel with each other. The busbar is a distribution point. The generator output voltage is maintained slightly higher than battery voltage to maintain the battery charged.

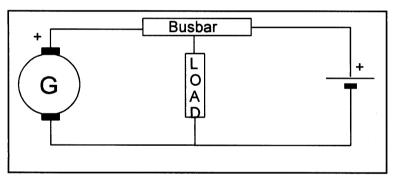


Figure 6.10 Diagram of a Generator System

6.6 CHARACTERISTICS OF THE SERIES WOUND DC GENERATOR

In a series wound DC generator, the **armature** (the rotating coil), **the field coils** (wire wrapped around the pole pieces to add strength to the magnetic field) **and the external circuit are all in series**.

This means that the same current which flows through the armature and external circuit also flows through the field coils.

Since the field current, which is also the load current, is large, the required strength of magnetic flux is obtained with a relatively small number of turns in the field windings. As the load draws more current from the generator, this additional current increases the field strength and generates more voltage in the armature winding. A point is soon reached (A) where further increase in load current does not result in greater voltage, because the magnetic field has reached saturation point (the point where no more magnetic lines of force can be absorbed by the pole pieces).

Because a constant voltage is required for aircraft systems the series generator cannot be used.

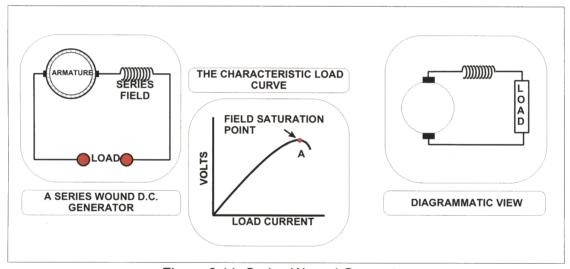


Figure 6.11 Series Wound Generator

6.7 CHARACTERISTICS OF THE SHUNT WOUND DC GENERATOR

A shunt wound DC generator has its field winding connected in **parallel (or shunt)** with the armature. Therefore the current through the field coils is determined by the terminal voltage and the resistance of the field.

The shunt field windings have a large number of turns, and therefore require a relatively small current to produce the necessary field flux.

When a shunt generator is started, the build-up time for rated terminal voltage (the maximum voltage at which the generator can continuously supply its rated load current) at the brushes is very rapid since field current flows even though the external circuit is open.

The figure below shows a schematic diagram and characteristic curve for the shunt generator. It should be noted that over the normal operating range of 'no load' to 'full load', the drop in terminal voltage as the load current increases is relatively small. The shunt generator is therefore used where a virtually constant voltage is desired, regardless of load changes.

The terminal voltage of a shunt generator can be controlled by a variable resistance connected in series with the shunt field coils.

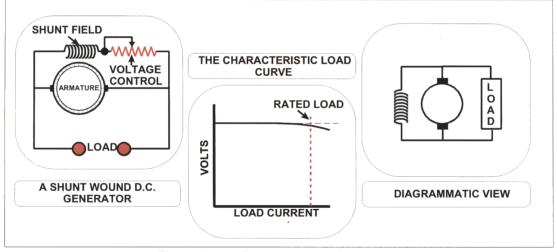


Figure 6.12 Shunt Wound Generator

6.8 A COMPOUND WOUND DC GENERATOR

A compound wound generator is a generator with combined series and shunt windings. There are two sets of field coils, one in series with the armature, and one in parallel with the armature. One shunt coil and one series coil are always mounted on a common pole piece and are sometimes enclosed in a common covering.

Compound wound generators were designed to overcome the drop in terminal voltage which occurs in a shunt wound generator when the load is increased. This voltage drop is undesirable where constant voltage loads are used. By adding the series field, which increases the strength of the total magnetic field when the load current is increased, the voltage drop caused by the increased load current flowing through the resistance of the armature is overcome, and it is possible to obtain an almost constant voltage output.

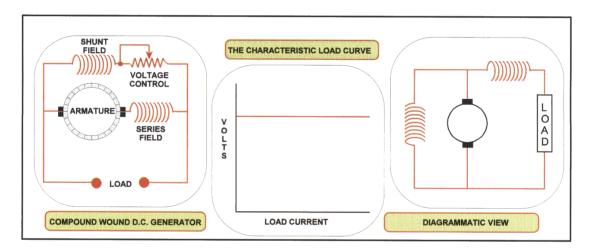


Figure 6.13 Compound Wound Generator

6.9 FLASHING THE GENERATOR FIELD

The DC generator is normally self excited due to the residual magnetism which remains in the field pole pieces when the machine is inactive or static. **Self excited** means that because of the residual magnetism as soon as the generator is rotated there will be a voltage produced. Some of this voltage can be applied to the **field coil** to increase the magnetism and cause the voltage to increase further until it reaches its controlled value. An **externally excited** generator is one which has no residual magnetism and requires a battery to supply the field coil with current to start the generating process.

It will have been noted that magnetism can be lost, destroyed or reversed due to the passage of time, the effects of heat, exposure to an AC field, hammering or shock, and the application of a reversal of polarity. The loss of residual magnetism in a DC generator, which will prevent any build up in output voltage, can be corrected by momentarily passing a current through the field in the normal direction.

This procedure is known as "**flashing the field**". In practice some aircraft might have a button or switch to allow this procedure to be carried out from the cockpit.

6.10 ARMATURE REACTION

The armature of a generator is wound with many coils of wire which rotate inside the stationary generator field. As the load on the generator increases then the current flowing through the armature coils increases. The current flowing through the coils creates a magnetic field in the armature which interacts with the stationary magnetic field, causing a distortion of the main field. This has the effect of shifting the **neutral plane** (the position where the armature windings are moving parallel to the lines of flux, where no voltage is induced see fig 6.7).

This distortion is known as **armature reaction** (see fig. 6.14) and is proportional to the current flowing through the armature. The brushes of the generator must be set in the neutral plane otherwise arcing and loss of power can occur. Armature reaction causes the neutral plane to move in the direction of rotation as the current increases, so a corrective system must be incorporated to prevent excessive arcing and loss of power.

The best means to maintain a constant neutral plane and therefore reduce arcing and power loss is by the use of special field poles called **interpoles** which counteract the effect of armature reaction. Interpoles, as their name suggests, are fitted between the poles of the stationary field and are coils of wire connected in series with the load. The polarity of the field produced by the interpole windings is arranged to be opposite to that of the armature field and so they have the effect of bending the main field and so the neutral plane back to its correct position. This ensures that there is minimum arcing at the commutator brushes and minimum overall loss power.

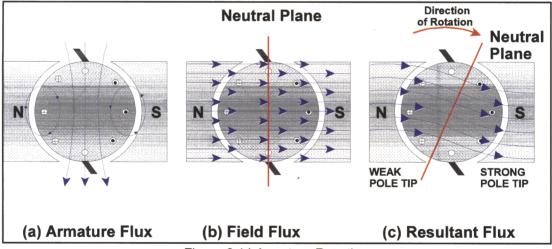


Figure 6.14 Armature Reaction

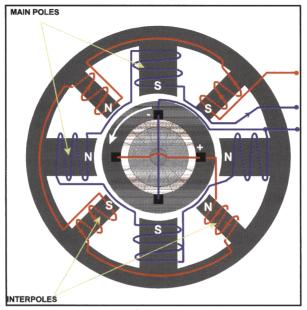


Figure 6.15 Interpole Generator

6.11 COMMUTATOR RIPPLE

Commutator ripple is the term given to the fluctuation of the voltage output of a DC generator as the voltage rises and falls during the rotation of the armature loop, particularly at low RPM. By increasing the number of coils in the armature or the number of field coils, or indeed both then the pulsating or ripple effect of the DC produced by a generator can be reduced. the diagram below compares a single coil armature with a multiple coil.

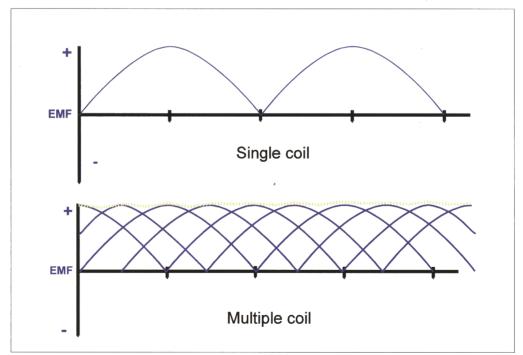


Figure 6.16 Single Coil and Multiple Coil Armature Outputs

6.12 ALTERNATORS

Most modern light aircraft use an **alternator** rather than a DC generator to provide constant voltage electricity for its electrical system because of the advantages an alternator has.

The alternator has a much better power to weight ratio, will produce a stable output at low RPM and does not suffer with the problems of a commutator as it uses a rectifier to convert AC to DC.

The following table and diagram identify the constructional differences between the DC generator and the alternator.

DC GENERATOR	ALTERNATOR
Rotating Armature	Stationary Armature
Stationary Field	Rotating Field
Converts AC to DC by means of a commutator	Converts AC to DC by means of a rectifier
Suffers from arcing and sparking at the commutator as the high load current has to flow through the commutator and brushes	High load current taken from stationary armature eliminates arcing and sparking. Small field current only flows through slip rings.

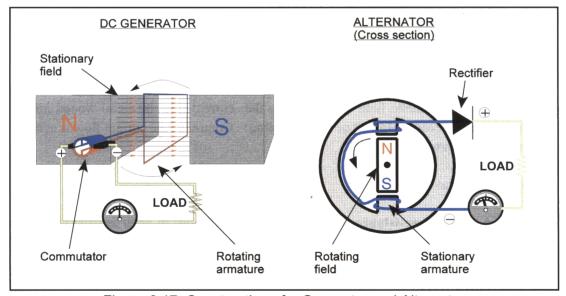


Figure 6.17 Construction of a Generator and Alternator

6.13 VOLTAGE CONTROL

The output voltage of a generator or alternator is dependent upon:-

- a) The speed of rotation of the armature or field.
- b) The strength of the magnetic field.
- c) The number of turns in the armature.
- d) The size and shape of the turns in the armature.

Most light aircraft DC electrical systems operate at 14 volts and so all the equipment it designed to operate correctly when supplied with 14 volts. It is therefore necessary for the output of the generator or alternator to be controlled, or regulated, to ensure that at all times it supplies 14 volts.

As can be seen from the table above, there are four factors which influence the output voltage of a generator or alternator.

The number and size and shape of the turns is a design factor and therefore the operator cannot alter them.

The generator or alternator is driven by a drivebelt or an engine accessory gearbox and therefore the speed of rotation of the armature or field is linked to the speed of rotation of the engine. Controlling the output voltage by controlling the speed of the engine is not a practical solution.

Remember back to basic magnetism, the strength of the magnetic field produced by a coil of wire is proportional to the current flowing through the coil (an electromagnet).

The only practical method of controlling the output voltage of a generator is to control the strength of the magnetic field by controlling the current flow in a coil wound around the magnetic pole pieces (field coil or field winding). Control of the current flow is achieved by a voltage regulator.

A voltage regulator consist of:-

- a) A variable resistance in series with the field coil. In older voltage regulators the variable resistance was achieved using a Carbon Pile. In modern voltage regulators it is achieved by employing an electronic solid state system of transistors, diodes and resistors. The net result is the same which ever is used.
- b) A control coil in parallel with the field coil and the armature. This is used to sense the generator output voltage and vary the resistance to control the current through the field coil, therefore controlling the voltage.

The voltage regulator senses the output voltage of the generator or alternator and adjusts the field current to maintain the correct output voltage irrespective of generator speed or electrical load

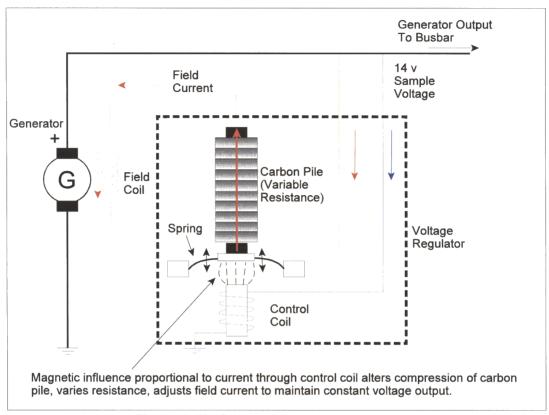


Figure 6.18 Carbon Pile Voltage Regulator

6.14 VOLTAGE REGULATOR OPERATION.

A **Carbon Pile voltage regulator** uses the carbon pile as a variable resistor. The carbon pile is a stack of carbon discs whose overall resistance is proportional to the amount of compression of the stack. The more the stack is compressed the lower the resistance.

In fig. 6.18 the **control coil**, which is in parallel with the generator armature, has the generator output supplied across it. Because the control coil has a fixed resistance and Ohms Laws states that V = I R, the current through the control coil will vary in direct proportion to the generator output voltage. As the current varies so will the strength of the magnetic field produced by the coil.

The strength of the magnetic field produced by the control coil effects the value of the **variable resistance**, (the compression of the carbon pile) which is in **series with the field coil**. As the resistance in the variable resistor varies, because V = I R, so the current in the field coil varies. As the current through the field coil varies so does the strength of the magnetic field it produces, and therefore the EMF induced into the armature, and the output voltage of the generator is controlled automatically.

In fig. 6.18 the field coil is shown outside of the generator for clarity, in fact it is an integral part of the generator construction.

The vibrating contact voltage regulator (fig. 6.19) controls the voltage output in a similar fashion but instead of varying a resistance it rapidly switches in and out a fixed resistance.

When the generator is started both sets of spring biased contacts are closed. Generator voltage is felt at the shunt winding and series winding of the voltage regulator. Current flows through the series winding and closed voltage regulator contact breaker to the field coil to enable the output voltage to build up.

As the regulated voltage is achieved the current through the shunt and series winding cause an electromagnetic effect which is sufficient to open the contact breaker points. This open circuits the series winding and causes the field current to pass through the fixed resistor causing a reduction of field current and therefore voltage. As the electromagnetic effect of the series winding is lost the contact breaker closes under spring action and restores field current and therefore output voltage until the cycle occurs again.

The frequency of operation of the contact depends on the load on the generator but is typically between 50 and 200 times a second.

The current regulator or current limiter limits the maximum output current in a similar fashion when the demand on the generator may exceed its maximum safe load. The current regulator contacts will open switching in the resistor to reduce excitation current.

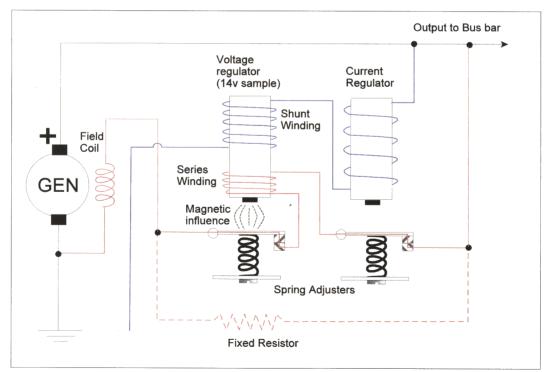


Figure 6.19 Vibrating Contact Voltage Regulator

6.15 LOAD SHARING CIRCUITS

When the aircraft electrical system has two generators feeding one Bus Bar it is known as **PARALLELLING GENERATORS**. The advantage of operating generators in parallel is much the same of having two batteries in parallel - double the capacity. It also allows the generators to share the total load of the aircraft and enables power to be maintained in the event of a generator failure.

When parallelling generators it is necessary for each generator to supply half of the total current demanded by the loads on the Bus Bar. This is known as **LOAD SHARING**.

To achieve Load Sharing the output voltage of both generators must be exactly the same. If there is any potential difference between the generator outputs then current will flow from the higher potential generator to the lower potential generator. This is known as **recirculating current**.

If this is the case then generator with the higher voltage output will be supplying all the current demanded by the Bus Bar loads and what ever current is demanded by the potential difference between the generator outputs. The generator with the lower voltage output will be supplying no current to the Bus Bar. There will be no load sharing, and the current flowing to the low output generator will be attempting to turn the generator into a motor. The direction of rotation of the motor will be in opposition to the direction of rotation of the engine. Flow of current to the low output generator is undesirable and parallel systems will have **reverse current relays** fitted to protect against this fault in the event of a failure of the load sharing circuit.

The load sharing circuit is comprised of **equalising coils in the voltage regulators** which finely adjust each generator field current to ensure the output voltages of the parallelled generators are equal.

In each voltage regulator the equalising coil is positioned such that it effects the magnetic field produced by the control coil, which effects the value of the variable resistance, which in turn affects the current through the shut field coil and so regulates the output voltage of the generator. The direction of flow of current through the equalising coil will determine whether the voltage output of the generator is increased or decreased.

6.16 OPERATION OF LOAD SHARING CIRCUIT

(See Figure 6.20)

a) With both generators "off line" there is no output from either generator and both Equalising Relays and Line Contactors are open. (The line contactor is a large solenoid operated contact which enables the output line of the generator to be connected to the busbar when the output voltage of the generator has been checked and found to be acceptable. It may be closed automatically or manually from the cockpit.)

- b) When N° 1 generator is brought "on line", N° 1 generator line conactor closes and its output, regulated by its voltage regulator, is supplied to the Aircraft Bus Bar. N° 1 Equalising Relay, which is part of the generator line contactor, is closed.
- When N° 2 generator is brought "on line", N° 2 generator line contactor is closed and its output, regulated by its voltage regulator, is supplied to the Aircraft Bus Bar.
 N° 2. Equalising Relay is also closed. This now connects both generator voltage regulators into the Equalising circuit.
- d) If there is any potential difference between the output of generator 1 and 2 there will be a current flow through the equalising coils which will apply correcting values to each voltage regulator increasing the voltage of the lower voltage generator and reducing the voltage of the higher generator until they are the same, equally sharing the total aircraft load.

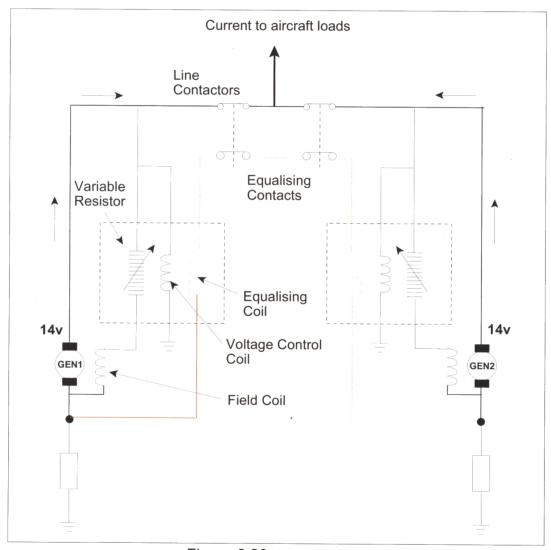


Figure 6.20 Load Sharing

DC ELECTRICS DC MOTORS

DC. MOTORS

6.17 ELECTRIC MOTORS

An electric motor is a machine for converting electrical energy into mechanical energy. Its function is, therefore, the reverse of that of a generator. There is little difference between the construction of D.C. motors and D.C. generators, both have essentially the same parts and they look alike. In fact, in many cases, a D.C. machine can be used either as a motor or a generator.

Remember back to magnetic principles, a current flowing through a wire placed in a magnetic field causes the wire to move due to a force acting on the wire; a motor works on this principle.

6.18 FLEMINGS LEFT HAND RULE

The direction of rotation of a motor can be determined by Fleming's Left Hand Rule (Figure 6.21). To do so, align the first finger with the field from the North Pole to the South Pole. Point the second finger in the direction of the current flowing into or out of the armature and the thumb will indicate the direction of motion.

For example, in Figure 6. 21 the first finger is aligned with the field and the second finger is pointing in the direction of the current coming out of the red (negative) half of the armature. The thumb is pointing upward indicating that the motion is upwards and therefore anticlockwise. In the blue (positive) half of the armature the current is flowing into the armature. Therefore, with the first finger still aligned with the field if the hand rotated through 180 degrees the thumb will now be pointing downward confirming anticlockwise rotation of the armature.

If the current or the field polarity is reversed, then so will be the direction of rotation of the motor. However, if both are reversed the direction of rotation of the motor remains unchanged.

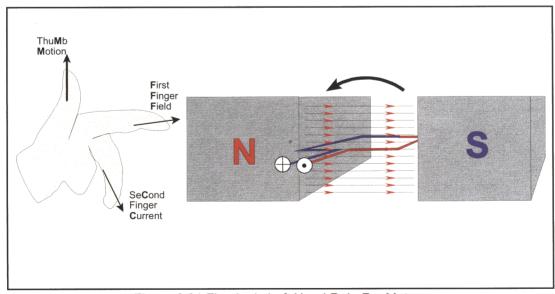


Figure 6.21 Fleming's Left Hand Rule For Motors

DC ELECTRICS DC MOTORS

6.19 PRACTICAL DC MOTOR

The simple DC generator shown earlier and the DC motor below are not practical and can be improved by adding further armature/s and improving the shape of the poles pieces. (Figure 6.22b). Generator voltage output and motor speed can be controlled by the addition of field windings which enable the field strength to be adjusted. Figure 6. 23 shows a sectional view of a practical DC generator which is similar to a DC motor.

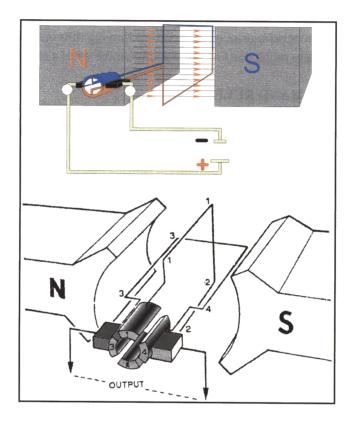


Figure 6.22 a Simple DC Motor and Figure 6.22b Improved DC Motor

DC ELECTRICS DC MOTORS

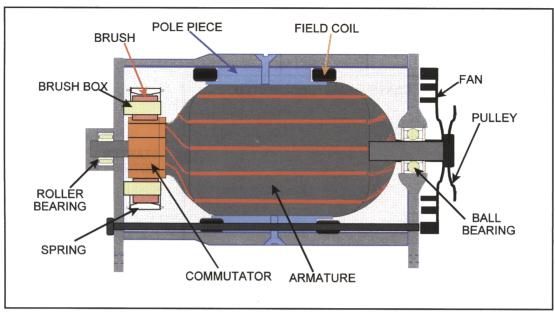


Figure 6.23 Sectional View of DC Rotating Armature Generator

6.20 BACK E.M.F

The movement of the conductor in the magnetic field induces in it an electromotive force (EMF) which we know from Lenz' law will oppose the rate of change of magnetic flux producing it. So an EMF is induced into the rotating part of the motor which tends to oppose the rotation of the motor. That is to say, the induced voltage will oppose the supply voltage. It is therefore called the **back EMF**.

The back EMF is proportional to motor speed and can never be as great as the supply input voltage. The difference between the applied EMF and the back EMF is always such that current can flow in the conductor and produce motion.

6.21 SLOW START RESISTOR

Some motors may have a **slow start resistor** in the circuit which is switched in series with the armature when the motor is first started to reduce the initial starting current before a back EMF has been established. The resistor is then by-passed by a centrifugal or time switch when the motor is turning to apply full current to the armature.

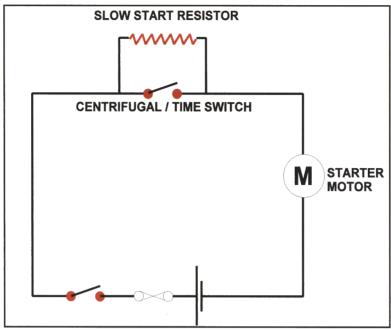


Figure 6.23 Slow Start Resistor Circuit

6.22 COMMUTATION

The simplest form of motor has a single loop of wire able to rotate freely between the poles of a permanent magnet. A connection is made from the DC supply source, (a battery) to the loop, by brushes on a commutator; the 2 segments of which are connected to opposite ends of the loop, an example of this type of motor is shown (figure 6.22a).

A single loop D.C. motor would not be able to turn heavy loads. To obtain a large mechanical output, with smooth running, the same improvements are made as in the case of the D.C. generator. That is, a laminated iron core carrying a number of armature coils is used, and a corresponding number of commutator segments. The magnetic field is produced by an electro-magnet and its field coils and the spacing between the armature and pole pieces is kept as small as possible.

6.23 SERIES WOUND MOTORS

The series wound motor has its field connected in series with the armature. The field coil consists of a few turns of heavy wire, and since the entire armature current flows through it, the field strength varies with the armature current. If the load on the motor increases, it slows down and the back EMF decreases, which allows the armature and field current to increase and so provide the heavier torque needed.

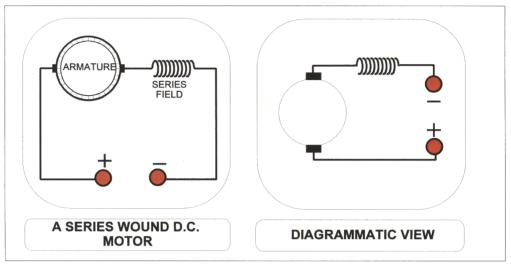


Figure 6.25 Series Wound Motor

Series motors run slowly with heavy loads and very rapidly with light loads. If the load is completely removed the motor can dangerously overspeed and possibly disintegrate.

The reason for this is that the current required to rotate the motor with only a light load is very small, and consequently the series wound field coils produce only a weak magnetic field. This means that the motor cannot turn fast enough to generate the amount of back E.M.F. needed to restore the balance. Series wound motors are variable speed motors, that is their speed changes with the applied load, for this reason they are not used either when a constant speed condition is needed, or where the load is intermittent. The series wound motor has a high starting torque and because of this it must never be started off load. Use of the series wound motor is mainly confined to electric actuators, starter motors and landing gear actuation.

6.24 SHUNT WOUND MOTORS

In a shunt wound motor, the field is connected directly across the voltage source, and is therefore independent of variation in load and armature current. The field coil consists of many turns of fine wire. The torque developed varies directly with the armature current.

If the load on the motor increases, the motor slows down, reducing the back E.M.F. (which depends upon speed as well as on the constant field strength).

The reduced back E.M.F. allows the armature current to increase, thereby furnishing the heavier torque needed to drive the increased load.

If the load is decreased, the motor speeds up, increasing the back em.f. and thereby decreasing the armature current and the torque developed whereupon the motor slows down. In a shunt wound motor, the variation of speed from 'no-load' to normal or 'full' load is only 10 % of the 'no-load' speed. Shunt wound motors are therefore considered constant speed motors.

Shunt wound motors are normally used where constant speeds under varying loads are required, and tasks where it is possible for the motor to start under light or no-load conditions, such as fans, centrifugal pumps and motor generator units.

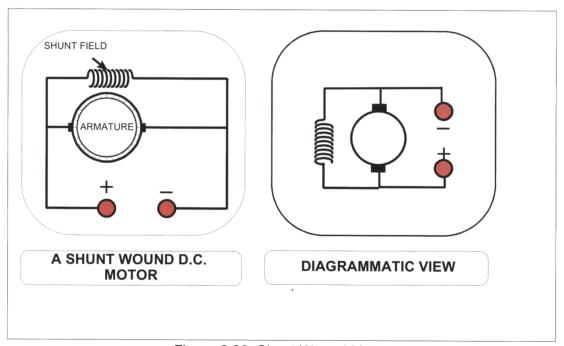


Figure 6.26 Shunt Wound Motor

6.25 STARTER-GENERATOR SYSTEMS

Several types of turbine-powered aircraft are equipped with starter systems which use a **starter generator** having the dual function of engine starting and of supplying DC power to the aircraft's electrical system.

Starter-generator units are basically compound-wound machines with two sets of field windings, one armature winding and a commutator. They are permanently coupled with the appropriate engine via a drive shaft and gear train.

For starting purposes, the unit functions as a fully compounded motor, the shunt field winding being supplied with current via a field changeover relay.

When the engine is running and the starter motor circuit is isolated from the power supply, the changeover relay is also automatically de-energized and its contacts connect the shunt-field winding to a voltage regulator. The changeover relay contacts also permit DC to flow through the shunt winding to provide initial excitation of the field.

The machine thereafter functions as a conventional DC generator, its output being connected to the bus-bar when it reaches the regulated level.

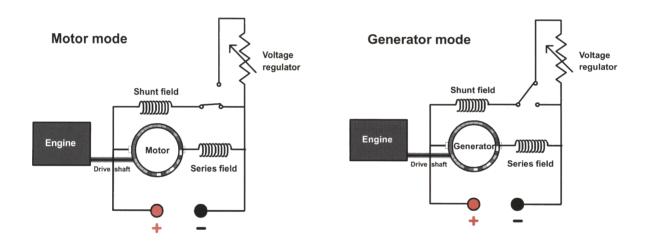


Figure 6.27 Compound Wound Motor Generator

The advantage of the starter - generator is that only one device provides both functions, thereby saving weight and complexity. The disadvantage is its inability to maintain full output at low rpm hence their use is typical on turbine engines which maintain a high engine rpm. A typical starter generator supplies 300 amps at 28 volts.

6.26 ACTUATORS

Equipment and components which are installed in the modern aircraft are generally inaccessible for manual operation by the pilot or crew. Remote control of such items is achieved by the use of electrical actuators.

These actuators may be divided into two main groups;-

- a) Solenoid actuators.
- b) Motor actuators.

6.27 SOLENOID ACTUATORS

Solenoid actuators are used to control hydraulic and pneumatic system selectors. Application of electrical power to a solenoid results in a valve opening under magnetic attraction.

6.28 MOTOR ACTUATORS

There are two types of motor actuators in use:-

- a) Rotary actuators.
- b) Linear actuators.

6.29 ROTARY ACTUATORS

Rotary Actuators are operated by small reversible motors which rotate an output shaft through a gearbox.

They are used for the operation of fuel valves and air/oil shut-off valves.

Control is by means of an ON / OFF or OPEN / SHUT selector switch. Two limit micro-switches control the extent and direction of travel and also operate the visual indicators in the cockpit. One limit switch is always closed, allowing current from the selector switch to the actuator. The limit switches change over at the end of travel.

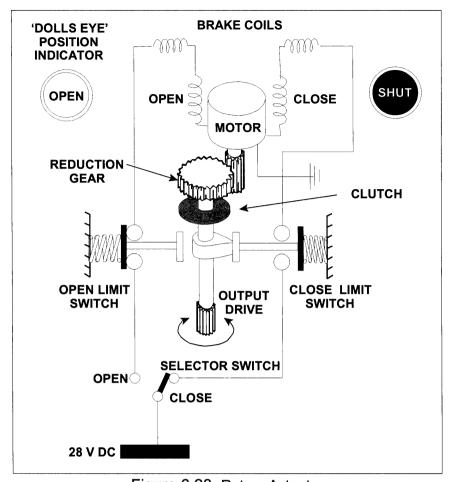


Figure 6.28 Rotary Actuator

6.30 LINEAR ACTUATORS

Linear actuators have small reversible motors which are coupled through a reduction gear to a screwjack which extends or retracts a ram or plunger.

They are used for any operation which requires a push / pull action, e.g. flaps, undercarriage, trim tabs, and also as inching controls for oil cooler shutters.

Operation is by means of selector switches when used for full up/down operation, but for small movements, such as those required with trimming controls, a spring-loaded self-centering 'OFF' switch is used, movement of the switch one way or the other away from centre supplying power to the actuator motor, which will then operate in the selected sense.

Two limit switches control the extent of travel and direction, and also operate visual indicators. The respective switch opens to stop the motor at full travel.

With an inching actuator, both limit switches will be closed at any time the actuator is not at a full travel position, this will facilitate motor reversal by means of the inching control switch.

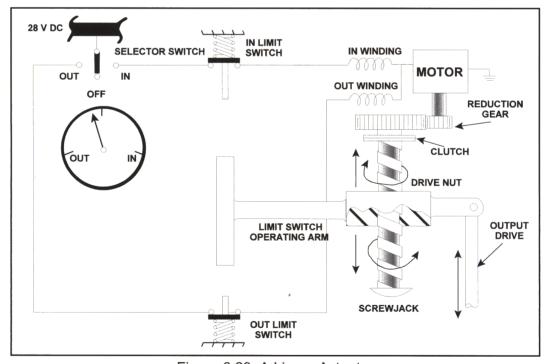


Figure 6.29 A Linear Actuator.

6.31 ACTUATOR BRAKES

Many actuators are fitted with electro-magnetic brakes to prevent over-travel when the motor is switched off.

The design of brake systems vary with the type and size of the actuator, but in all cases the brakes are spring-loaded to the 'on' condition when the motor is de-energised, and the operating solenoids are connected in series with the armature so that the brakes are withdrawn immediately power is applied.

6.32 ACTUATOR CLUTCHES

Friction clutches are incorporated in the transmission systems of actuators to protect them against the effects of mechanical over-loading.

6.33 VISUAL INDICATORS USED WITH LINEAR ACTUATORS

Press-to-test lights or magnetic indicators are used where no intermediate stopping positions between actuator limits are required.

Position indicators with a graduated scale are fitted in situations where movement either side of a datum, or between open and closed, is to be shown.

6.34 VISUAL INDICATORS USED WITH ROTARY ACTUATORS

These indicate to the pilot the position of the actuated equipment which would typically be fuel or oil valves. These are only ever in the 'OPEN' or 'SHUT' position.

In both cases an indication of either Loss of Power supply, or that the actuator is travelling between selected positions, will be required.

6.35 INDICATOR LIGHTS

Indicator lights are usually of the 'press-to-test' type. Application of finger pressure on the front glass of the lamp unit enables the filament to be tested without operating the control switches of the actuator.

6.36 ELECTROMAGNETIC INDICATORS

The electromagnetic indicator was introduced as a replacement for the simple filament lamp indicator.

The types in common use are the dolls-eye, prism and flag indicators which are illustrated in Figure 6.30. The pictorial presentations offered by these indicators is further improved by the painting of 'flow lines' on the appropriate panels so that they interconnect the indicators with the system control switches, essential indicators and warning lights.

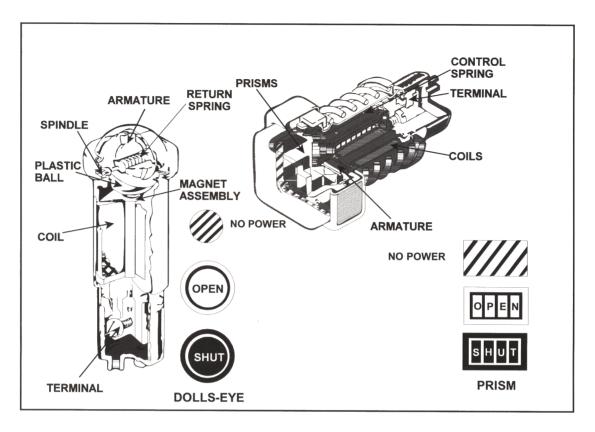


Figure 6.30 Electro-Magnetic Indicators

6.37 ACTUATOR CONSTRUCTION

The actuator motor is a high speed reversible motor and it is widely used for the electrical operation of fuel valves, cooler shutters, trimming tabs, etc.

A wide ratio gear train is used to transmit the power and the actuator can be either rotary or linear in movement.

6.38 THE SPLIT FIELD SERIES ACTUATOR

This type of actuator has two differentially wound series field windings, each producing a flux in the opposite direction. Only one winding can be energised at any one time, and the direction of rotation depends on which winding is energised.

Limit switches which are operated by the mechanical load, are normally fitted in series with the field windings, these stop the motor automatically when the load reaches the limits of its travel.

6.39 THE SPLIT FIELD SERIES ACTUATOR OPERATION

With an **OPEN** selection, a supply is fed to the armature via the limit switch, the open field and brake coils. Energising the brake coils releases the brake (if fitted) allowing the motor to operate.

On completion of the actuator travel the limit switches are tripped as follows:-

- a) Open Limit Switch. This breaks the supply to the motor on completion of travel and makes the circuit to the 'open' position indicator.
- b) Close Limit Switch. This sets up the 'close' circuit ready for completion when a selection of 'close' is made on the control switch.

Note:- the brake solenoid operates immediately the supply is broken thus preventing over-runs or creep.

A slipping clutch may also be fitted between the armature shaft and gearing to prevent damage which could be caused by mechanical over load.

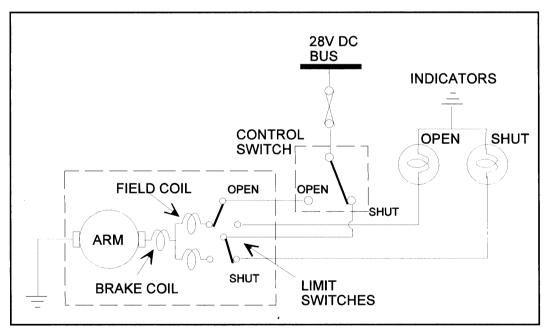


Figure 6.31

SELF ASSESSMENT QUESTIONS GENERATORS AND MOTORS

SELF ASSESSMENT QUESTIONS - GENERATOR THEORY

- 1. An EMF is induced in a conductor rotating in a magnetic field by:
 - a) capacitive reaction.
 - b) the reverse current relay.
 - c) electro transmission.
 - d) electro magnetic induction.
- 2. Magnetic field strength is controlled by:
 - a) battery bus bar current.
 - b) current in the field coil.
 - c) current in the armature.
 - d) current flow to the battery.
- 3. If a conductor is placed in a magnetic field:
 - a) an EMF is induced in the conductor.
 - b) an EMF is induced in the conductor only when the conductor rotates.
 - c) the applied resistance assists the back EMF.
 - d) an EMF is induced in the conductor only when the conductor is stationary.
- 4. The output of a basic generator before commutation is:
 - a) AC
 - b) DC and after commutation is AC.
 - c) DC
 - d) synchronised AC and DC.
- 5. An internally excited generator is one where:
 - a) the field is produced within the distribution.
 - b) the field is initiated by a HT and LT coil.
 - c) the field is initiated by the battery.
 - d) the field is initiated within the generator.
- 6. A DC generator has a commutator whose purpose is to:
 - a) change AC to give a generator output of DC.
 - b) change DC to AC.
 - c) transmit the generator output to the electrical circuit and to cool the generator.
 - d) maintain a constant resistance.

SELF ASSESSMENT QUESTIONS GENERATORS AND MOTORS

- 7. Another name for a number of conductors rotating in a magnetic field is:
 - a) a capacitor.
 - b) an armature.
 - c) a condenser.
 - d) a commutator.
- 8. A generator is governed so that:
 - a) the EMF is constant and the rate of flow varies.
 - b) the rate of flow is constant and the EMF varies.
 - c) the generator voltage reduces generator temperature.
 - d) back EMF is equal and opposite to the applied EMF.
- 9. The voltage regulator:
 - a) senses cut out pressure and adjusts field current.
 - b) senses generator output pressure and adjusts field current.
 - c) senses generator output current and adjusts the field voltage.
 - d) senses back EMF.
- 10. The generator master switch is normally:
 - a) fitted with a mechanical safety catch.
 - b) in the field circuit which is connected in parallel with the generator output.
 - c) in the field circuit which is in parallel with the voltage regulator.
 - d) fitted in series with the commutator.

SELF ASSESSMENT QUESTIONS GENERATORS AND MOTORS

GENERATOR CONTROL

- 1. The voltage regulator:
 - a) provides a constant current flow from the generator with changes of generator speed.
 - b) senses current output.
 - c) maintains a steady generator voltage with changes of generator speed.
 - d) regulates the amount of current supplied by the battery to operate the generator.
- 2. Voltage is controlled in a generator by:
 - a) a reverse current relay.
 - b) moving the brushes.
 - c) a voltage regulator.
 - d) it is uncontrollable.
- 3. On aircraft, generator voltage is regulated by:
 - a) varying the generator field strength.
 - b) increasing and decreasing the load.
 - c) changing the generator speed.
 - d) changing generator load.
- 4. In an aircraft having a battery with a nominal voltage of 24v, generator output would be:
 - a) 24 volts.
 - b) 28amps.
 - c) 28 volts.
 - d) 24 amps.
- 5. In DC electrical generating systems, the voltage regulator controls the system voltage within prescribed limits:
 - a) regardless of varying engine RPM and electrical load, by varying the current in the generator field windings.
 - b) by means of a relay which closes contacts in the output line when a certain RPM is reached.
 - c) by temperature.
 - d) by a variable resistance which limits the voltage given by the batteries.

SELF ASSESSMENT QUESTIONS GENERATORS AND MOTORS

- 6. A voltage regulator is fitted to:
 - a) prevent high circulating currents.
 - b) prevent backlash.
 - c) to ensure correct voltage output to battery.
 - d) to prevent battery feedback to the generator.
- 7. If an aircraft electrical system is quoted as 24 volts DC the output of the generator is:
 - a) 12 volts with the generators connected in series.
 - b) 28 volts with the generators connected in parallel.
 - c) 36 volts with the generators connected in series/parallel.
 - d) 42 volts.
- 8. If a circuit is designed for 12 volts the generator will:
 - a) give parallelled output only.
 - b) give controlled 14 volts.
 - c) 14 volts wild DC.
 - d) give controlled 12 volts.
- 9. The aircraft electrical generator output is controlled in flight by:
 - a) sensing the generator output pressure.
 - b) ram air.
 - c) a resistance in the generator output circuit.
 - d) the resistance of the armature circuit.
- 10. In a generator control circuit the strength of the magnetic field is controlled by:
 - a) the commutator.
 - b) the voltage regulator
 - c) the reverse current contactor.
 - d) the output C/B.

SELF ASSESSMENT QUESTIONS GENERATORS AND MOTORS

ACTUATORS AND MOTORS

- 1. Rotary actuators are used for:
 - a) undercarriage retraction.
 - b) centre of gravity assessment.
 - c) operation of fuel cocks.
 - d) movement of control surfaces.
- 2. Actuator normal travel is controlled by:
 - a) a clutch.
 - b) limit micro switches.
 - c) mechanical indicators.
 - d) mechanical stops.
- 3. AC current from an engine driven generator is converted to DC current by:
 - a) a commutator
 - b) a convertor.
 - c) an alternator.
 - d) a rotary actuator.
- 4. On a twin engined DC aircraft having two DC generators load sharing is achieved by:
 - a) equalising engine RPM's
 - b) an equalising circuit to sense the difference and equalise the voltages of the two generators
 - c) synchronising relays and voltage coil tuners
 - d) an equalising circuit to sense the difference and equalise the field currents of the two generators
- 5. Pilots are informed of rotary actuator positions by:
 - a) non return valves.
 - b) lights or dolls eye indicators.
 - c) travel indicators.
 - d) veger counters.

SELF ASSESSMENT QUESTIONS GENERATORS AND MOTORS

- 6. To supply direct current from a generator giving alternating current it is normal to fit:
 - a) a commutator
 - b) a rotary inverter.
 - c) an alternator.
 - d) a static inverter.
- 7. Press to test lights are used:
 - a) to indicate to the pilot that the circuit has power and is complete.
 - b) to control the movement of a rotary actuator.
 - c) to indicate to the pilot that the circuit has operated.
 - d) only to indicate to the pilot that the equipment has malfunctioned.
- 8. A device for changing AC to DC is:
 - a) an inverter.
 - b) a rotary transformer.
 - c) a rectifier.
 - d) an alternator.
- 9. An inching control is used in conjunction with:
 - a) a linear actuator.
 - b) a rotary actuator.
 - c) a combination of linear and rotary actuator.
 - d) a rectifier.
- 10. Friction clutches are fitted to actuators for:
 - a) protection against mechanical overload.
 - b) protection against brake on loads.
 - c) protection against non return valve failure.
 - d) protection against supply failures.

CHAPTER SEVEN - AIRCRAFT ELECTRICAL POWER SYSTEMS

Contents

		Page	
7.1	AIRCRAFT ELECTRICAL POWER SYSTEMS	1.7 - 1	
7.2	DI - POLE OR TWO WIRE SYSTEM	1.7 - 1	
7.3	SINGLE POLE (UNIPOLE OR EARTH RETURN) SYSTEM	1.7 - 1	
7.4	GENERATORS AND ALTERNATORS	1.7 - 2	
7.5	VOLTAGE REGULATORS	1.7 - 2	
7.6	OVERVOLTAGE PROTECTION UNIT	1.7 - 3	
7.7	GENERATOR CUT-OUT OR REVERSE CURRENT RELAY	1.7 - 3	
7.8	RECTIFIERS	1.7 - 3	
7.9	INVERTERS	1.7 - 3	
7.10	THE GENERATOR DIFFERENTIAL CUT-OUT	1.7 - 3	
7.11	GENERATOR WARNING LIGHT	1.7 - 4	
7.12	GENERATOR (OR ALTERNATOR) MASTER SWITCH	1.7 - 4	
7.13	MONITORING INSTRUMENTS	1.7 - 5	
7.14	AMMETERS AND VOLTMETERS	1.7 - 6	
7.15	THE BATTERY	1.7 - 7	
7.16	THE BUS-BARS	1.7 - 7	
7.17	BUSBARS	1.7 - 9	
7.18	BUSBAR SYSTEMS	.7 - 10	
7.19	LOAD SHEDDING	.7 - 11	
7.20	GENERATOR OR ALTERNATOR FAILURE	.7 - 11	
SELF ASSESSMENT QUESTIONS			

7.1 AIRCRAFT ELECTRICAL POWER SYSTEMS

The power system for a single-engine aircraft consists of a generator or alternator with the control and indication equipment necessary to supply all the electrical power once the system is **on-line.**

The term on-line means that the generator or alternator has been switched into the electrical system and is actually supplying power to the system.

With multi-engine aircraft two or more generators or alternators are installed in parallel. The ampere capacity of an aircraft electrical system is determined by the number of power-consuming devices fitted.

7.2 DI - POLE OR TWO WIRE SYSTEM

A dipole or two wire system is required where an aircraft is made of a non conductive material. The current needs a complete circuit to flow and therefore needs a negative wire to connect the load to the negative side of the generator as well as a positive or 'live wire' to connect from the Busbar (distribution point) to the load.

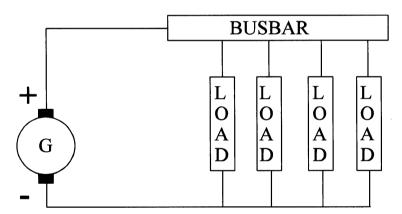


Figure 7.1 Dipole System

7.3 SINGLE POLE (UNIPOLE OR EARTH RETURN) SYSTEM

This is the most common type of system on an aircraft with metal construction. The metal airframe is used as the negative conductor completing the circuit for the current flow. The negative side of the generator is connected to an 'airframe earth' as is the negative side of each load.

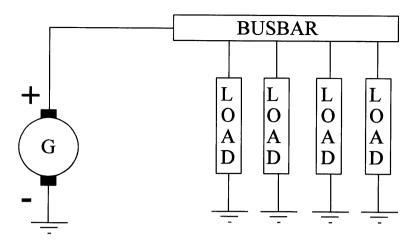


Figure 7.2 Unipole System

7.4 GENERATORS AND ALTERNATORS

Generators or Alternators are used to convert mechanical energy to electrical energy.

A generator produces direct current (DC) by using a rotating armature, stationary field and a commutator as described in the previous chapter. Whereas an alternator produces alternating current (AC) by using a rotating field and a stationary armature. If it is required to convert the AC output of an alternator to DC a diode rectifier is used, fitted in the end frame of the alternator.

Most modern light aircraft have a direct current system which is powered by an alternator.

The full power output of a generator is closely related to the rpm of the engine and is usually attained with the engine running at half speed whereas the full power output of an alternator can be attained at slow running, one obvious advantage that an alternator has over a generator. The generator is driven at a speed which is approximately three times that of the engine.

7.5 VOLTAGE REGULATORS

The Voltage Regulator maintains the output voltage of the generator or alternator at a constant value, irrespective of the engine rpm or electrical loads. This is achieved by controlling either the current flow in the field coils of a generator, or the current flow in the exciter field of an alternator.

The basic voltage regulator setting controls the generator output to maintain 14 volts for a 14 volt system with a 12 volt battery and 28 volts for a 28 volt system with a 24 volt battery.

7.6 OVERVOLTAGE PROTECTION UNIT

An overvoltage protection unit is fitted to protect against the output voltage of the generator rising dangerously high and causing damage to aircraft circuits due to overheating (V=IR). Protects against voltage regulator failure.

The overvoltage protection circuit will automatically disconnect the field circuit if the voltage rises to typically 16.5 volts in a 14v system, thereby reducing the generator output to zero and safeguarding the system.

It may also open the generator cut out to prevent reverse current flow.

7.7 GENERATOR CUT-OUT OR REVERSE CURRENT RELAY.

The generator cut out permits the generator voltage to build up to a preset figure before its contacts close and put the generator on-line. It will open to prevent the battery feeding current back into the generator when the generator voltage is below that of the battery voltage.

The contacts of a cut out are closed by rising voltage and opened by reverse current. A cut-out is not fitted in an alternator system as the diodes provide reverse current protection.

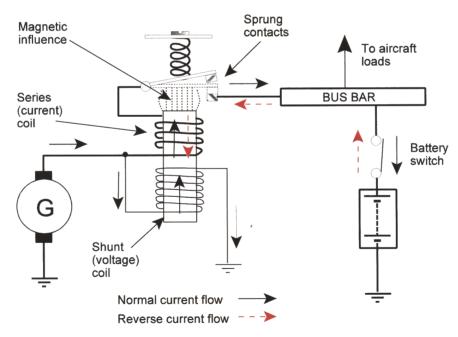


Figure 7.3 Reverse Current Cut-Out Relay

The reverse current cut-out relay shown above would be used with a DC generator. It may be an integral part of the voltage regulator or it may be a separate unit. Before the generator is started the spring holds the contacts open. As the generator builds up voltage, that voltage is applied to the voltage (shunt) coil which has many turns of thin wire and is connected in parallel with the generator output. When the voltage has built up above the battery voltage the current through the voltage coil causes a magnetic influence to close the contacts and connect the generator to the busbar. The current flows through the current coil, which has a few turns of thick wire and through the contacts to the bus bar and the aircraft loads. The current flow through the current coil increases the magnetic effect and helps to keep the contacts closed against the spring.

When the output voltage of the generator falls below battery voltage then current flow is reversed and current flows back toward the generator. The falling voltage of the generator causes the magnetic influence of the voltage coil to reduce and as the current flow through the current coil is reversed it reverses the magnetic field produced by the current coil. This opposes the field produced by the voltage coil and allows the contacts to open by the spring, disconnecting the generator from the busbar and preventing reverse current into the generator.

7.8 RECTIFIERS

The rectifiers in the alternator end frame convert AC to DC and permit the current to flow out from the alternator but not into it from the battery.

7.9 INVERTERS

Static inverter

Static inverters are solid state devices which covert DC to constant frequency AC. A typical inputs to a static inverter would be 18 - 30 volts DC and the output would be 115 volts AC at 400 hertz frequency. The internal circuitry of a static inverter contains standard electrical and electronic components such as oscillators, diodes, transistors, capacitors and transformers.

Rotary inverter

Rotary inverters convert DC to AC by using a constant speed DC motor to drive an alternator thereby producing constant frequency AC.

7.10 THE GENERATOR DIFFERENTIAL CUT-OUT

The generator differential cut out is fitted in a multi-engine aircraft to prevent circulating currents between a generator which is already on-line and one which is coming on-line.

The on-coming generator cannot switch on-line until its output voltage is 2% above the output voltage of the generator which is already on-line. The 2% difference in potential is between the on-coming generator output and the battery bus-bar.

7.11 GENERATOR (OR ALTERNATOR) WARNING LIGHT

The generator or alternator warning light indicates to the pilot that the generator or alternator voltage has fallen below battery voltage. Illumination of the light is usually associated with the generator cut out position or a reverse current detector.

7.12 GENERATOR (OR ALTERNATOR) MASTER SWITCH

The master switch enables the pilot to electrically isolate the generator or alternator. Opening the master switch breaks the generator field circuit or the alternator exciter circuit and the electrical output falls to its residual level which is virtually zero.

7.13 MONITORING INSTRUMENTS

Instruments and warning lights must be provided for the pilot to monitor the aircraft DC or AC electrical system. The AC system is covered in the AC chapter, here we will examine typical meters and show their use in a DC system.

7.14 AMMETERS AND VOLTMETERS.

Ammeters and voltmeters are provided in AC and DC systems and in most cases are of the **moving coil** type of instrument shown in the following diagram. The instrument consists of a permanent magnet with a soft iron core between the poles, inside which fits a former on a spindle which is free to rotate inside the magnetic field. A coil of wire is wound around the former and current is allowed to flow around the coil. Two hairsprings are fitted to restrain the movement of the coil, as the coil rotates one spring is wound up, the other unwound. The hairsprings allow the current to be fed into and out of the coil. The coil and former carry a pointer which is arranged to move over a scale as the coil rotates.

When current flows through the coil a magnetic field is created which interacts with the main field and causes the coil to rotate moving the indicator pointer across the scale until the torque is balanced by the hairspring. The greater the current flow through the coil, the greater will be the movement of the pointer. When the current flow reduces the pointer will be returned to its 'zero' mark by the hairspring. So the deflection of the pointer is proportional to the current flowing through the coil, giving rise to an evenly divided scale.

The meter is likely to be housed inside a case made of soft iron to prevent stray magnetism affecting the indication.

To enable the range of the instrument to be extended a **shunt** (resistor of low resistance value) can be fitted in conjunction with this type of meter when used as an ammeter. When used as a voltmeter, a **multiplier** (resistor of high resistance value) is fitted. A shunt or multiplier will allow only a proportion of the total current to be allowed through the instrument therefore protecting the delicate mechanism but still allowing it to measure large values.

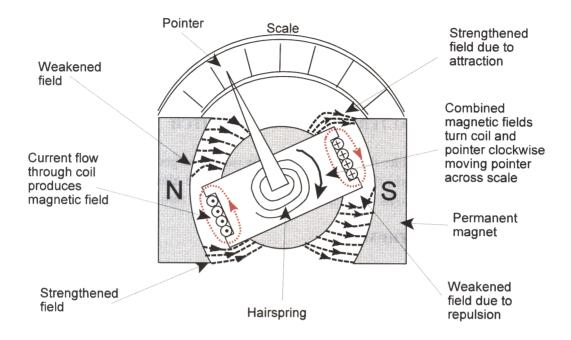


Figure 7.4 A Moving Coil Instrument

The number of indicating devices required and the types employed depends on the type of aircraft and the overall nature of its electrical installation.

One ammeter (or loadmeter) is normally provided for each possible source of power, and a single voltmeter with multiple selections for each DC system.

There are basically two types of ammeter;-

- a) the **charge** / **discharge** ammeter (or 'centre zero' ammeter) see Figure 7.5.
- b) the **generator ammeter or loadmeter** ('left zero' ammeter) see Figure 7.5

The **charge** / **discharge** or zero-centre type ammeter displays information about current flow into or out of the battery.

If the needle is to the right of zero, the alternator is working and supplying power to the electrical system and charging the battery.

If the needle is to the left of zero, then the battery is discharging, indicating that the alternator is not supplying power to the electrical system.

The **loadmeter** or left zero type of ammeter displays actual current draw (system demand) from the alternator.

If the loadmeter reads zero, then the alternator is not supplying power to the system, leaving the battery as the sole source of power in a single engine system.

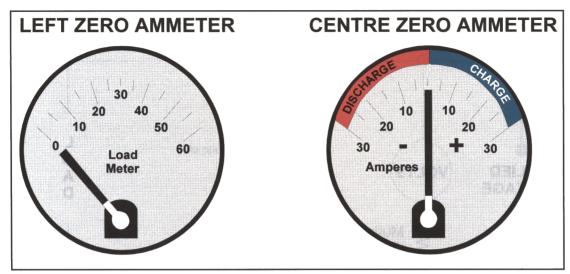


Figure 7.5. Simple Ammeters.

If an alternator fails in flight, all operating electrical equipment begins to deplete the battery. The pilot must therefore immediately assess the situation to determine what equipment is absolutely essential to the safety of flight at that moment and turn off everything else to conserve battery power.

This procedure is known as **load shedding**.

Figure 7.6. shows both how current is measured with an **ammeter** placed in the current flow so that it measures the current flowing through it and how emf and pd are measured with a **voltmeter** connected to the two points between which the potential difference is to be measured.

Voltmeters have a high internal resistance and are connected in **parallel** to measure the voltage **between** two points. It may have a **multiplier** fitted in series with the meter to increase the indicating range of the instrument.

Ammeters have a low internal resistance and are placed in **series** to measure current **through** the load It may have a **shunt** fitted in parallel with the meter to increase the indicating range of the instrument.

7.15 THE BATTERY

The battery would normally be a 12 or 24 volt lead-acid or alkaline and can be used to start the engines, or to supply electrical power in the event of generator or alternator failure.

7.16 THE BUS-BARS

The bus bars are the collection and distribution centre for a generator or alternator power supply. They utilise solid copper bars which can be drilled to permit supply and distribution cables to be attached.

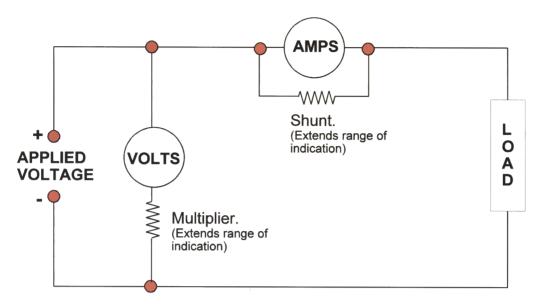


Figure 7.6. Ammeter and Voltmeter Connections.

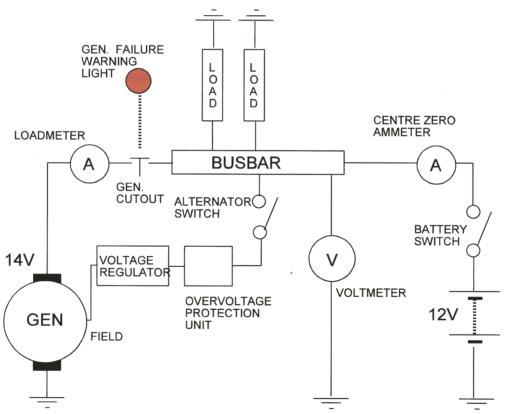


Figure 7.7 General Arrangement- Single Engine Light Aircraft

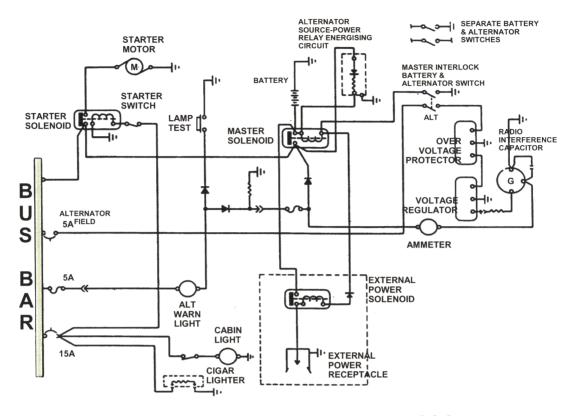


Figure 7.8. A Typical Light Aircraft Single Alternator DC System

7.17 BUSBARS

In most types of aircraft, the output from the generating sources is coupled to one or more low impedance conductors referred to as busbars.

Busbars are usually situated in junction boxes or distribution panels located at central points within the aircraft, and they provide a convenient means for connecting power supplies to the various consumer circuits; in other words, they perform a 'carry-all' function.

Busbars vary in form dependent on the methods to be adopted in meeting the electrical power requirements of a particular aircraft type.

In its simplest form a busbar can take the form of a strip of interlinked terminals, while in the more complex systems main busbars are thick metal (usually copper) strips or rods to which input and output supply connections can be made.

The strips or rods are insulated from the main structure and are normally provided with some form of protective covering. Flat, flexible strips of braided copper wire are also used in some aircraft and serve as subsidiary busbars.

7.18 BUSBAR SYSTEMS

The function of a distribution system is primarily a simple one, but it is complicated by having to meet additional requirements which concern a power source, or a power consumer system operating either separately or collectively, under abnormal conditions.

The requirements and abnormal conditions may be considered in relation to three main areas, which are summarized as follows:

- a) Power-consuming equipment must not be deprived of power in the event of power source failures unless the total power demand exceeds the available supply.
- b) Faults on the distribution system (e.g. fault currents, grounding or earthing at a busbar) should have the minimum effect on system functioning and should constitute minimum possible fire risk.
- c) Power-consuming equipment faults must not endanger the supply of power to other equipment.

These requirements are met in a combined manner by **paralleling** generators where appropriate, by providing adequate **circuit protection** devices, and by arranging for failed **generators to be isolated** from the distribution system.

The operating principle of these methods is concerned with the additional one of arranging busbars and distribution circuits so that they may be fed from different power sources.

In adopting this arrangement it is usual to categorize all consumer services into their order of importance and, in general, they fall into three groups;

- a) vital,
- b) essential,
- c) non-essential.

Vital services are those which would be required after an emergency wheels-up landing, e.g. emergency lighting and crash switch operation of fire extinguishers. These services are connected directly to the battery.

Essential services are those required to ensure safe flight in an in-flight emergency situation. They are connected to DC and AC busbars, as appropriate, and in such a way that they can always be supplied from a generator or from batteries.

Non-essential services are those which can be isolated in an in-flight emergency for load shedding purposes (see below), and are connected to DC and AC busbars, as appropriate, and are supplied from a generator.

7.19 LOAD SHEDDING.

Load shedding is the overall reduction of the electrical loads on the power supply system in the event that the generators cannot supply all of the load demanded. In some aircraft it can be automatically achieved, in other aircraft the pilot must monitor the electrical load by use of the ammeters or loadmeters and maintaining the total load within the rated value of the generator or alternator. After generator failure some non essential loads would be switched off to prevent overloading the remaining generator or battery. This will result in a decrease in current demand from the bus-bar and enable the essential loads to be supplied..

7.20 GENERATOR OR ALTERNATOR FAILURE.

The indications of a generator or alternator failure would consist of a **generator or alternator** warning light illuminating and the ammeter or loadmeter showing either zero, or a discharge if it was the centre reading type. Typical actions to be carried out in the event of a Generator or Alternator Failure are as follows:-

- a) switch off all unnecessary electrical loads. Details are given in the aircraft handling notes of the items to be the subject of load shedding.
- b) isolate the generator or alternator electrically by turning the master switch or alternator switch "off". This will break the field circuit and the output voltage will fall to zero or a residual value, making the failed system 'safe'.
- c) in most cases a failure of the generator will cause the reverse current relay to operate, isolating the generator output from the bus bar.

AIRCRAFT ELECTRICAL POWER SYSTEMS

Figure 7.9. illustrates, in a very simplified form, the principle of dividing categorized consumer services between individual busbars, this is an example of a **split busbar system**.

In this example, the power distribution system is one in which the power supplies are 28 volts DC, from engine-driven generators operating in parallel, 115 volts 400 Hz AC from inverters, and 24 volts DC from batteries.

Figure 7.9. shows that each generator has its own busbar to which are connected the non-essential consumer services.

Both busbars are in turn connected to a single busbar which supplies power to the essential services. Thus, with both generators operating, all consumers requiring DC power are supplied.

The essential services busbar is also connected to the battery busbar thereby ensuring that the batteries are maintained in the charged condition.

The battery busbar may be referred to as a 'hot bus' or 'hot battery bus' because it is always connected to the battery.

In the event that one generator should fail it is automatically isolated from its respective busbar and all busbar loads are then taken over by the operating generator.

Should both generators fail however, non-essential consumers can no longer be supplied, but the batteries will automatically supply power to the essential services and keep them operating for a pre-determined period calculated on the basis of consumer load requirements and battery state of charge. (Normally 30 minutes).

In the case of the system represented in Figure 7.9., the DC supply to power the inverters is taken from busbars appropriate to the importance of the AC operated consumers.

Thus, essential AC consumers are operated by No. 1 inverter and so it is supplied with DC from the essential services busbar.

No. 2 and No. 3 inverters supply AC to non-essential services and so they are powered by DC from the No. 1 and No. 2 busbars.

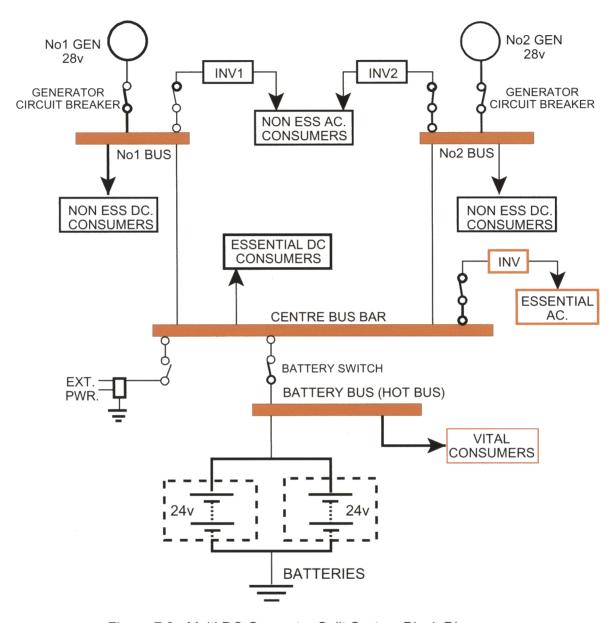


Figure 7.9. Multi DC Generator Split System Block Diagram.

SELF ASSESSMENT QUESTIONS - GENERATOR CUT-OUT

- 1. In an electrical circuit the reverse current cut-out relay will open:
 - a) when battery voltage exceeds generator voltage.
 - b) when circuit voltage is less than generator voltage.
 - c) when the main output C/B is reset.
 - d) when the batteries are flat.
- 2. A generator cut-out is provided:
 - a) to prevent the battery over heating.
 - b) to prevent the battery from being overcharged.
 - c) to allow the generator to be isolated in a crash.
 - d) to prevent discharge of the battery through the generator.
- 3. A generator cut-out will open when:
 - a) circuit loads equal the battery voltage.
 - b) the air temperature reaches 45°C.
 - c) circuit loads equal the generator voltage.
 - d) generator voltage falls below battery voltage.
- 4. A generator cut-out is fitted to prevent:
 - a) the battery discharging through the generator windings.
 - b) the generator overcharging the battery.
 - c) fire in the event of overloading the system.
 - d) out of phasing.
- 5. In the event of the cut-out points sticking in the closed position, the most probable results, when the engine stopped would be:
 - a) gain of engine power.
 - b) a burnt out generator.
 - c) loss of residual magnetism.
 - d) no apparent reaction.

c)

d)

AIRCRAFT ELECTRICAL POWER SYSTEMS

6.	To prevent circulating currents when more than one generator is being connected to the same bus bar:			
	a)	reverse current relays are fitted.		
	b)	the generators are connected in series.		
	c)	rectifiers are fitted.		
	d)	differential cut-outs are used.		
7.	A generator cut-out is fitted:			
	a)	in series with the generator output.		
	b)	in the diode circuit.		

- a) 36 volts.
- b) 24 volts.
- c) 28 volts.
- d) 26 volts.
- 9. A component whose job is similar to a generator cut out is:

in parallel with the generator output.

in the field circuit.

- a) a rectifier.
- b) a converter.
- c) an inverter.
- d) a reverse current relay.
- 10. If the cut-out is open, the battery is feeding the loads which are:
 - a) in series with the battery.
 - b) in parallel with the battery.
 - c) in sequence with the cut-out.
 - d) cross coupled.

GENERATOR CIRCUIT 1

- 1. In a two engine aircraft with two generators, there would be:
 - a) one ammeter for each generator and one voltmeter switchable to indicate either generator voltage or battery voltage.
 - b) one voltmeter for each generator, and one ammeter switchable to indicate either generator current or battery current.
 - c) one ammeter showing the total output and one switchable voltmeter.
 - d) one ammeter and one voltmeter each showing the average current and voltage output.
- 2. A generator converts mechanical energy to electrical by:
 - a) electro magnetic spring action.
 - b) electro magnetic induction.
 - c) electrostatic induction.
 - d) electro dynamic induction.
- 3. In an aircraft electrical system which incorporates a voltmeter, the voltmeter indicates:
 - a) the flow in the electrical system before the battery cut-out contacts close.
 - b) the rate of flow at all times.
 - c) the pressure in the electrical system before and after the cut-out contacts close.
 - d) the flow in the electrical system after the battery cut-out contacts close.
- 4. If the generator warning light comes on in flight it indicates that:
 - a) the generator is feeding the battery bus bar.
 - b) the generator is not feeding the battery bus bar.
 - c) the battery has failed.
 - d) a rectifier is faulty.
- 5. A generator failure is usually indicated by:
 - a) the ammeter reading decreasing or showing a discharge and a red warning lamp lighting.
 - b) the voltmeter reading increasing, the ammeter reading showing discharge and a red lamp lighting.
 - c) the current consuming devices failing to operate.
 - d) the motor speed increasing.

AIRCRAFT ELECTRICAL POWER SYSTEMS

- 6. A generator warning light will be illuminated:
 - a) when the battery voltage exceeds that of the generator and the cut-out has opened.
 - b) at night only.
 - c) when the generator is supplying current to a fully charged battery, and no electrical loads are switched on.
 - d) when the battery charge current is lower than required to maintain its fully charged state.
- 7. If a generator fails in flight:
 - a) the voltmeter will read maximum.
 - b) the ammeter reading will decrease.
 - c) load sharing circuits will operate.
 - d) the watt metre will show a increase.
- 8. If one generator fails you should:
 - a) switch off the good generator.
 - b) stop and feather the engine concerned.
 - c) switch off the failed generator and continue normal use of the electrical system.
 - d) switch off the failed generator, and cut down on the electrical services being used.
- 9. A generator is brought 'on the line' when it is:
 - a) connected in series with other generators.
 - b) switched into the electrical circuit in parallel with the other generators.
 - c) connected with the ground batteries for starting.
 - d) connected to a phase reducer.
- 10. In a twin engine aircraft, fitted with two generators, if one should fail:
 - a) the failed generator must be isolated.
 - b) cut down the air supply to reduce five risks.
 - c) the failed generator must be stopped.
 - d) both generators must be switched off.

GENERATOR CIRCUIT 2

- 1. A generator is brought 'on line' via the battery cut-out by an increase in:
 - a) the battery voltage.
 - b) the radio by pass switch.
 - c) the generator voltage.
 - d) the generator field voltage.
- 2. Generator failure is indicted by:
 - a) load sharing circuits connecting.
 - b) a decrease or discharge in ammeter readings and generator warning light on.
 - c) an increase in voltmeter readings, a discharge in ammeter reading and generator warning light on.
 - d) failure of electrically driven instruments.
- 3. In a twin engine aircraft, with a generator fitted to both engines, the starboard generator fails. Will:
 - a) the starboard engine cut.
 - b) the port engine cut.
 - c) both engines run normally.
 - d) the engine with the failed generator will automatically feather.
- 4. Loads on a bus bar are:
 - a) in series with the generator so that the voltage can be reduced.
 - b) in parallel so the voltage can be varied.
 - c) in parallel so the current can be reduced.
 - d) determined by the cross sectional area of the lead cable.
- 5. When the battery master switch is switched off in flight:
 - a) the generators are disconnected from the bus bar.
 - b) the battery is isolated from the bus bar.
 - c) the battery is discharged through the bonding circuit diodes.
 - d) the battery may overheat.

AIRCRAFT ELECTRICAL POWER SYSTEMS

- 6. A generator is taken 'off' line by:
 - a) the battery switch.
 - b) operation of the field switch.
 - c) opening of the cut-out.
 - d) removing of all loads.
- 7. If the ammeter reads plus 5 amp after engine shut down:
 - a) some switches have been left 'on'.
 - b) the battery is charging.
 - c) the generator field switch is 'on'.
 - d) the ammeter is defective.
- 8. If the ammeter shows 'no' charge, yet the battery remains charged. Would you look for:
 - a) loose battery connections.
 - b) defective voltage regulator.
 - c) defective C/B.
 - d) defective ammeter.
- 9. A field switch in the generator circuit is:
 - a) kept in the 'on' position.
 - b) connected in the armature circuit.
 - c) to 'shut off' the generator field.
 - d) to disconnect the battery.
- 10. During flight a malfunction of the generator cut-out would be indicated by:
 - a) overheating of the battery.
 - b) the ammeter.
 - c) lights going out.
 - d) the current limiter.

D.C. ELECTRICS

AIRCRAFT ELECTRICAL POWER SYSTEMS

DISTRIBUTION

- 1. A short circuit in a 'single pole' electrical circuit would be caused:
 - a) by a broken conductor between the source of supply and an item of equipment.
 - b) by an open circuit between loads in parallel.
 - c) when wiring between the source of supply and an item of equipment goes down to earth.
 - d) by an open circuit between an item of equipment and earth.
- 2. In a '2 pole' electrical circuit, a short of the conductors would result in:
 - a) an item of equipment operating automatically without switches.
 - b) the component not working.
 - c) an increase in voltage.
 - d) an item of equipment burning out because of a large current flow.
- 3. The indicating range of an ammeter can be increased by fitting;
 - a) A shunt fitted in parallel with the instrument.
 - b) A shunt fitted in parallel with the load
 - c) A shunt fitted in series with the instrument
 - d) A multiplier fitted in parallel with the instrument
- 4. An electrical system which uses the aircraft structure as a return path for current, is known as:
 - a) a diode pole circuit.
 - b) an earth return circuit.
 - c) a single phase circuit.
 - d) a dipole circuit.
- 5. On a single pole circuit, if the positive conductor is shorted to the aircraft structure:
 - a) the electrical component will operate.
 - b) the fuse will blow.
 - c) the circuit will be under loaded.
 - d) the load will only operate at half speed.

AIRCRAFT ELECTRICAL POWER SYSTEMS

- 6. In a double pole circuit:
 - a) the systems polarity will change.
 - b) the current is supplied by one wire and the current is returned through the aircraft bonding system.
 - c) the current passes out through one wire and is returned through a second wire.
 - d) the current passes out through one wire and is returned via the aircraft's immune circuit.
- 7. In a earth return circuit if the conductor is open circuited:
 - a) the fuse will blow.
 - b) the bus bars will overheat.
 - c) the load will not operate.
 - d) the generator will burn out.
- 8. A 'hot bus' is:
 - a) the bus bar always connected to the battery
 - b) the bus bar that supplies the galley power
 - c) the bus bar that supplies the essential loads
 - d) the bus bar that supplies the nom-essential loads
- 9. The earth return system of aircraft wiring is that:
 - a) one lead from the battery and one lead from the component is connected to the aircraft structure.
 - b) one lead from the battery is earthed and both leads of the components are earthed.
 - c) the negative sides of the system are connected direct to the positive side of the battery.
 - d) rectifiers are cross connected.
- 10. A dipole circuit is one where:
 - a) diode valves are used.
 - b) three conductors are used.
 - c) the aircraft structure is used for the earth return.
 - d) two conductor wires are used.

CHAPTER EIGHT

Contents

		Page
8.1	BONDING	1.8 - 1
8.2	THE STATIC DISCHARGE SYSTEM OR STATIC WICKS	1.8 - 1
8.3	DISCHARGE OF STATIC ON TOUCH DOWN	1.8 - 1
8.4	SCREENING	1.8 - 2
	SELF ASSESSMENT QUESTIONS	1.8 - 3

8.1 BONDING

An aircraft in flight will pick up, or become charged with, static electricity from the atmosphere. Bonding will prevent any part of the aircraft from building up a potential so great that it will create a spark and generate a fire risk.

Each piece of the metal structure of the aircraft, and each component on the aircraft, is joined to the other by flexible wire strips. All strips must be clean and free from any insulating coatings such as anodizing, paint, grease and oxides to prevent electrolytic corrosion occurring which would introduce resistance.

This process is called **bonding**, and it provides an easy path for the electrons from one part of the aircraft to another.

Bonding can also act as part of the earth return system in a uni pole circuit and will also help to prevent radio interference due to static discharges.

8.2 THE STATIC DISCHARGE SYSTEM OR STATIC WICKS

The **static discharge systems**, or **static wicks**, are fitted to reduce static build up on the airframe. They were originally made of cotton of about the thickness of a cigarette.

They are fitted to the trailing edge of the aircraft control surfaces, and the tips of wings, or stabilisers. Static electricity is dispersed from them into the atmosphere.

The free end of the wick becomes 'teased' (spread out) and a brush discharge action takes place. Modern wicks are like miniature barbed antenna, small wire brushes, or alternatively are straight metal wicks.

8.3 DISCHARGE OF STATIC ON TOUCH DOWN

To ensure that no static electrical charge, with its possible fire risk, remains on the aircraft after landing, the main bond must be brought into instantaneous contact with the ground as the aircraft touches down.

This is achieved by fitting nose, tail or main wheel tyres which contain a high proportion of carbon in the rubber.

The tyre is in contact with the main bond via the wheel bearing and any static charge is dissipated to earth on touch-down.

8.4 SCREENING.

Screening is designed to prevent radio interference by absorbing electrical energy.

Static electrical charges, produced by the operation of certain electrical equipment, create interference on radio circuits.

This interference is overcome by fitting interference suppressors in the cables connected to the source of interference, and by total enclosure of the cables in a continuous metal sheath.

Screening is required for ignition systems, DC generators and motors (commutator machines), slip ring machines operating at over 200 rpm and also for any electrical equipment operating by making and breaking a circuit at a frequency greater than 10 Hz.

SELF ASSESSMENT QUESTIONS - BONDING-SCREENING

ELECTRICS

- 1 Why are static wick dischargers fitted to aircraft:
 - a) to smooth the generator output.
 - b) to prevent tyres bursting on landing.
 - c) to minimise radio interference.
 - d) to act as an earth return in a single pole electrical system.
- 2 Bonding is used to protect the aircraft against fire from arcing of static electricity by:
 - a) providing an earth return.
 - b) shortening the negative strips.
 - c) maintaining different electrical potential throughout the structure.
 - d) ensuring the same electrical potential of all metal components.
- 3 Static electricity constitutes a fire hazard because:
 - a) metal components become very hot and ignite inflammable gases and materials.
 - b) sparks occur due to differences of potential and could ignite inflammable gases and materials.
 - c) of colour charged electrons.
 - d) aircraft tyres become heavily charged and may burst on landing.
- 4 Static electrical charges and currents in an aircraft structure are evened out by:
 - a) hardening
 - b) screening
 - c) bonding
 - d) anodising
- 6 The electrical components of aircraft systems are screened to:
 - a) bond the circuit to reduce risk of fire.
 - b) prevent them discharging.
 - c) prevent short circuits in radio equipment.
 - d) prevent them interfering with the function of radio equipment.

- 6 Bonding is a method of:
 - a) heat screening.
 - b) providing a positive reaction.
 - c) ensuring that the different parts of the aircraft are maintained at a different potential.
 - d) ensuring that the different parts of the aircraft are maintained at the same potential.
- When refuelling an aircraft:
 - a) the refuelling nozzle must be bonded to the fuel tank.
 - b) the bonding plug must be connected to the earth terminal.
 - c) the continuity between nozzle and hose must be infinity.
 - d) only use plastic nozzles.
- 8 The purpose of electrical bonding on an aircraft is:
 - a) to prevent compass malfunctioning and accumulation of local static charges.
 - b) to reduce the anodising effect.
 - c) to isolate all components electrically and therefore make static potential constant.
 - d) to provide a low resistance path for earth return circuits and safely dissipate local static charges and lightning strikes.

CHAPTER NINE - MORE SELF ASSESSMENT QUESTIONS

Contents

	Page
GENERAL NO. 1	1.0 1
GENERAL NO. 1	. 1.9 - 1
GENERAL NO. 2	. 1.9 - 4
MACTED ANGWED CHEET	10 5

DC ELECTRICS GENERAL NO. 1

- 1 Spare fuses are carried:
 - a) at the operators's discretion.
 - b) for generators only.
 - c) by law with a stated minimum number required.
 - d) by the first officer.
- When selecting a fuse for a circuit the governing factor is:
 - a) the voltage of the circuit.
 - b) the fuse length and diameter.
 - c) the resistance of the circuit.
 - d) the power requirement of the circuit.
- 3 Differential cut-outs close when a differential voltage exists between the:
 - a) generator bus and battery bus-bar.
 - b) generator bus-bar and earth.
 - c) batteries.
 - d) battery bus-bar and earth.
- 4 Circulating current is the term used to describe:
 - a) back EMF.
 - b) current necessary to excite the generator.
 - c) current passing between two paralleled generators of differing voltage.
 - d) current passing between AC and DC systems.
- 5 A megohm is:
 - a) 10 000 ohms
 - b) 1000 ohms
 - c) 1 000 000 ohms
 - d) 1 000 000 000 ohms
- 6 Load shedding is:
 - a) transferring the loads between generators.
 - b) reducing the load voltage.
 - c) overall reduction of electrical load on the system.
 - d) overall reduction of generator voltages.

- 7 the formula for calculating power is
 - a) $\frac{V^2}{R}$ or $I^2 \times R$ or $I \times V$
 - b) $\frac{V^2}{R}$ or I x R or I x V
 - c) $\frac{V}{R^2}$ or $I^2 \times R$ or $I^2 \times V$
 - d) \underline{V} or I x R² or I x V
- When a generator is on line and its associated ammeter reads 10 amps, this is an indication of:
 - a) BTB's being energised.
 - b) battery charge rate.
 - c) battery discharge rate.
 - d) generator load.
- Assuming a 5 amp circuit has failed during flight and investigation has shown that the fuse is open circuit, the action to be taken is to:
 - a) to switch the circuit off immediately.
 - b) switch off replace the fuse with another of the correct rating for the circuit and repeat this action as often as necessary.
 - c) leave the switch on, replace the failed fuse with one of increased rating.
 - d) switch off, replace the failed fuse with one of the correct rating once only.
- If the voltage in a circuit is doubled the current will:
 - a) double
 - b) increase only if the battery is in circuit.
 - c) remain the same.
 - d) decrease.
- A simple electrical circuit has a current flow of 4 amperes and its resistance is 5 ohms. How much power (watts) is used:
 - a) 20 watts
 - b) 45 watts
 - c) 80 watts
 - d) 100 watts

DC ELECTRICS SPECIMEN QUESTIONS

- 12 A lead acid battery voltage should be checked:
 - a) on open circuit with a voltmeter.
 - b) on load with a voltmeter.
 - c) on no load with a voltmeter.
 - d) only if a fault is suspected.
- 13 Connecting two batteries in series will:
 - a) increase the voltage and capacity.
 - b) have no effect.
 - c) decrease the voltage and the capacity.
 - d) increase the voltage, the capacity will remain the same.
- An aircraft has a battery with a capacity of 60 A/H. Assuming that it will provide its nominal capacity and is discharged at the 10 hour rate:
 - a) it will pass 60 amperes for 10 hurs.
 - b) it will pass 10 amperes for 6 hours.
 - c) it will pass 6 amperes for 10 hours.
 - d) it will pass 60 amperes for 1 hour.
- 15 A NICAD battery shows a high temperature after engine start, this could be an indication of:
 - a) thermal runaway.
 - b) it is not connected to the battery bus-bar.
 - c) normal temperature during charging.
 - d) depends upon the outside air temperature.
- When generators are connected in parallel their output voltage must be:
 - a) divided by the circuit resistance.
 - b) the same.
 - c) added together.
 - d) controlled by one generator.

DC ELECTRICS GENERAL NO. 2

- In a direct current generating system the voltage regulator controls the system voltage within prescribed limits:
 - a) regardless of varying engine RPM and electrical load by inserting a variable resistance in the generator field winding.
 - b) by means of a relay which closes contacts in the output circuit when a prescribed voltage is reached.
 - c) of the generator rotor speed.
 - d) by a variable resistance which limits the voltage given by the battery.
- 2 A generator or battery cut-out is fitted:
 - a) to isolate the battery on touch down.
 - b) to prevent the battery from being overcharged.
 - c) to allow the generator to be isolated in a crash.
 - d) to prevent the battery feeding back into the generator when its voltage is above the generator voltage.
- A generator or battery cut-out contacts will close:
 - a) with an increase in battery voltage.
 - b) with an increase in generator voltage.
 - c) at flight idle only.
 - d) with an increase in generator current.
- 4 Failure of an aircraft generator is indicated by:
 - a) a red warning light lighting and the ammeter showing zero or discharge.
 - b) a red warning light going out and the ammeter showing a discharge.
 - c) a current limiter tripping.
 - d) a circuit fuse blowing.
- On a twin engined aircraft with a generator fitted to each engine, if the starboard generator fails, will:
 - a) the fuel crossfeed cocks close.
 - b) the starboard engine cut (stop).
 - c) the port engine will cut.
 - d) both engines will run normally.

DC ELECTRICS SPECIMEN QUESTIONS

- 6 On an earth return aircraft wiring circuit:
 - a) the negative pole is connected to the aircraft structure.
 - b) the positive pole is connected to the aircraft structure.
 - c) the negative pole is connected to the positive pole.
 - d) two fused are needed.
- 7 In a dipole aircraft wiring circuit if the conductors are bridged:
 - a) an item of electrical equipment would be burned out.
 - b) no immediate action is necessary.
 - c) the item of electrical equipment would operate normally.
 - d) the fuse or circuit breaker in that circuit will blow.
- 8 A circuit breaker that has tripped due to overload:
 - a) cannot be reset unless the circuit has returned to normal.
 - b) will not be able to be reset in the air.
 - c) will reset itself when the circuit returns to normal.
 - d) must be replaced.
- 9 When changing a blown fuse:
 - a) it is changed with one of a lower rating.
 - b) the press to reset button is operated.
 - c) leave circuit switched on.
 - d) it is changed with one of the correct rating.
- 10 Is this a:
 - a) faulty switch.
 - b) double pole switch.
 - c) quadruple switch.
 - d) single pole switch.
- 11 As the speed of an electric motor increases the back EMF will:
 - a) remain the same.
 - b) fluctuate.
 - c) increase.
 - d) decrease.

- 12 The output of a shunt wound generator:
 - a) will rise gradually as load is applied.
 - b) will remain constant as load is applied.
 - c) will vary with generator speed.
 - d) will fall gradually as load is applied.
- 13 Load shedding is:
 - a) increasing circuit resistance.
 - b) transferring the loads between generators.
 - c) reducing the load voltage.
 - d) overall reductions of the loads on the system.
- An inertia switch on an aircraft will operate:
 - a) when selected by the pilot or flight engineer.
 - b) automatically in flight.
 - c) during an emergency or crash landing.
 - d) in flight only.
- 15 The purpose of electrical bonding on aircraft is:
 - a) to directly earth the positive lead.
 - b) to prevent compass malfunctioning and to gather local static charges.
 - c) to isolate all components electrically and therefore make the static potential constant.
 - d) to provide a low resistance path for earth return circuits and safely dissipate local static charges and lightning strikes.
- 16 Electrical components of aircraft systems are screened to:
 - a) bond the circuit to reduce risk of fire.
 - b) prevent them interfering with the function of radio equipment.
 - c) prevent short circuits interfering with aircraft equipment.
 - d) prevent engine malfunctions.

DC ELECTRICS SPECIMEN QUESTIONS

ANSWERS TO SELF ASSESSMENT QUESTIONS

THE	ORY ((1.1-1	1)		UNITS 1 (1.1-13)						UNITS 2(1.1-15)						
	A	В	C	D		A	В	C	D			A	В	C	D		
1				*	1				*		1	*					
2	*				2	*					2		*				
3	*				3			*			3			*			
4			*		4	*					4			*			
5	*				5				*		5		*				
6		*			6			*			6		*				
7			*		7		*				7			*			
8			*		8				*		8		*				
9			*		9	*					9				*		
10		*			10				*		10				*		

	BA	TTE	RIES 1	1	BATTERIES 2							BATTERIES 3					
	A	В	C	D		A	В	C	D			A	В	C	D		
1		*			1	*					1			*			
2				*	2				*		2	*					
3	*				3				*		3				*		
4			*		4			*			4				*		
5				*	5				*		5		*				
6			*		6			*			6	*					
7			*		7			*			7	*					
8				*	8			*			8				*		
9		*			9		*				9			*			
10			*		10				*		10	*					

DC ELECTRICS

SPECIMEN QUESTIONS

MAG	NET	ISM				(GEN THEORY					GEN CONTROL					
	A	В	C	D			A	В	C	D			A	В	C	D	
1				*		1				*		1			*		
2		*				2		*				2			*		
3	*					3		*				3	*				
4			*		400 34	4	*					4			*		
5			*			5				*		5	*				
6		*				6	*				11.7	6			*		
7				*		7		*			210	7		*			
8		*				8	*					8		*			
9	*					9		*				9	*				
10						10		*				10		*			

GEN	CUT	OUT				GEN CIRCUIT 1							GEN CIRCUIT 2					
	A	В	C	D			A	В	C	D			A	В	C	D		
1	*				e Plant and	1	*					1			*			
2				*		2		*				2		*				
3				*		3			*			3			*			
4	*					4		*				4			*			
5		*				5	*					5		*				
6				*		6	*					6			*			
7	*					7		*				7				*		
8				*		8				*		8				*		
9				*		9		*	,			9			*			
10		*				10	*					10		*				

мот	ORS	& A(CTUA	TORS	5]					
	A	В	C	D			A	В	C	D	
1			*			1			*		
2		*				2				*	
3	*					3		*			
4		*				4			*		
5		*				5				*	
6	*					6				*	
7	*					7	*				
8		1	*			8				*	
9	*					9					
10	*					10					

	DISTRIBUTION							CIRCUIT BKRS						FUSES			
	A	В	C	D			A	В	C	D			A	В	C	D	
1			*		ull le	1	*					1			*		
2		*				2				*		2		*			
3	*					3		*				3				*	
4		*				4	*					4			*		
5		*				5	*				41	5			*		
6			*			6		*				6				*	
7			*		i d	7	*					7				*	
8	*					8				*		8	*				
9	*					9	*					9				*	
10				*	441	10	*					10			*		

GENERAL 1 & GENERAL 2

	A	В	C	D			A	В	C	D			A	В	С	D
1			*		-	13				*		7				*
2				*		14		:	*			8	*			
3	*					15	*					9				*
4			*			16		*				10		*		
5			*			17						11			*	
6			*			18						12				*
7	*					1	*				100	13				*
8				*		2				*		14			*	:
9				*		3		*				15				*
10	*					4	*					16		*		
11			*			5				*		17				
12		*				6	*					18				

JOINT AVIATION AUTHORITIES AIRLINE TRANSPORT PILOT'S LICENCE Theoretical Knowledge Manual

AIRCRAFT GENERAL KNOWLEDGE 2

021 02 02 ALTERNATING CURRENT

Second Edition, First Impression.







SUBJECT 2 - ALTERNATING CURRENT ELECTRICS

TABLE OF CONTENTS

CHAPTER 01	INTRODUCTION
CHAPTER 02	ALTERNATORS
CHAPTER 03	PRACTICAL AIRCRAFT SYSTEMS
CHAPTER 04	TRANSFORMERS
CHAPTER 05	A C MOTORS
CHAPTER 06	BASIC COMPUTERS

CHAPTER 07 SEMI CONDUCTORS

CHAPTER ONE - INTRODUCTION

Contents

	Pag
1.1	INTRODUCTION. 2.1 -
1.2	THE NATURE OF ALTERNATING CURRENT 2.1 -
1.3	TERMS 2.1 -
1.4	RELATIONSHIP OF CURRENT AND VOLTAGE IN AN AC CIRCUIT 2.1 -
1.5	RESISTANCE IN AC CIRCUITS
1.6	INDUCTANCE IN AC CIRCUITS
1.7	INDUCTIVE REACTANCE
1.8	CAPACITANCE IN AC CIRCUITS
1. 9	CAPACITIVE REACTANCE
1.10	IMPEDANCE
1.11	RESONANT CIRCUITS
1.12	POWER IN AC CIRCUITS
1.13	POWER IN A PURELY RESISTIVE CIRCUIT 2.1 - 1
1.14	POWER IN A PURELY INDUCTIVE CIRCUIT 2.1 - 1
1.15	POWER IN A CAPACITIVE CIRCUIT 2.1 - 1
1.16	POWER IN A PRACTICAL AC CIRCUIT 2.1 - 1
1.17	POWER FACTOR 2.1 - 2
1.18	POWER FACTOR RESUME

1.1 INTRODUCTION.

Alternating current (AC) is used in most large modern transport aircraft because of the following advantages that it holds over direct current (DC) supplies:-

- a) AC generators are simpler and more robust in construction than DC machines.
- b) The power to weight ratio of AC machines is better than comparable DC machines.
- c) The supply voltage can be converted to a higher or lower value with almost 100% efficiency using transformers.
- d) Any required DC voltage can be obtained simply and efficiently using transformer rectifier units. (T.R.U.s)
- e) Three phase AC motors which are simpler, more robust and more efficient than DC motors, can be operated from a constant frequency source, (AC generators).
- f) AC machines do not suffer from the commutation problems associated with DC machines and consequently are more reliable, especially at high altitude.
- g) High voltage AC systems require less cable weight than comparable power low voltage DC systems.

1.2 THE NATURE OF ALTERNATING CURRENT.

If the electrons flowing in a circuit move backwards and forwards about a mean position then the current produced is known as alternating current (AC). The simple AC generator shown in Figure 1.1 shows that a loop of wire (armature) rotated in a magnetic field experiences continuously changing flux through it so that a voltage will be induced as long as rotation continues.

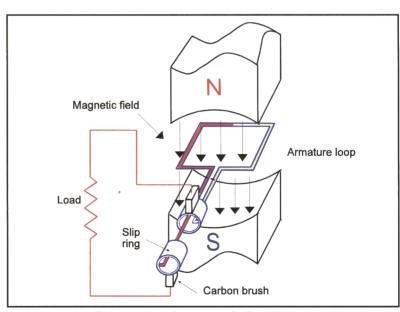


Figure 1.1 Simple AC Generator

The magnitude of the voltage depends on the speed of rotation and the field strength (ie. rate of change of flux).

When an armature is connected to a load (resistor) in a closed circuit through slip rings and carbon brushes a current will flow around the circuit in proportion to the induced voltage. If this armature is rotated as in Figure 1.2 then the flux is constantly changing. In positions 1,3 and 5 the two sides of the loop are moving parallel to the field and so there is no voltage induced as there is no rate of change of flux. In positions 2 and 4 the two sides of the armature are moving at right angles to the field and the maximum voltage is induced as there is maximum rate of change of flux. In between these positions the induced voltage is between maximum and zero.

The polarity of the induced voltage changes as it passes through zero because the direction that each side of the armature moves through the field is reversed. If the polarity reverses then so must the current through the external circuit, current flowing backwards and forwards about a mean position is alternating current. The direction of current flow through each side of the armature at any point can be determined by using Fleming's Right Hand Rule for generators.

Figure 1.2 shows one complete revolution of the generator armature and the associated rise and fall of induced voltage

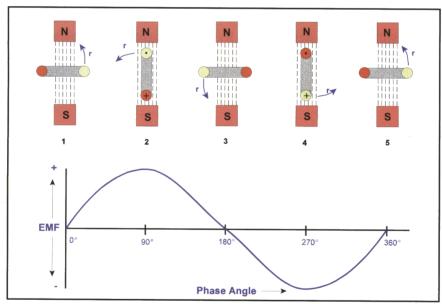


Figure 1.2 Production of AC

Figure 1.3 illustrates the production of AC The blue vector arrow OP represents one half of the coil of the generator, pivoted at O and rotating in an anti-clockwise direction. The E.M.F. induced in the coil is proportional to the ordinate ON, or can be calculated by multiplying the Max value by the sine of the Phase Angle at that point.

Successive ordinates plotted to a time scale corresponding to the rate of rotation of OP produce a sine wave which represents an alternating current or voltage.

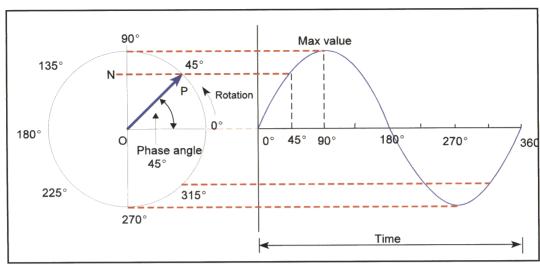


Figure 1.3 Production of A Sinewave

1.3 TERMS

Several terms are used to describe alternating current, illustrated in Figure 1.4 some of these terms are explained below:-

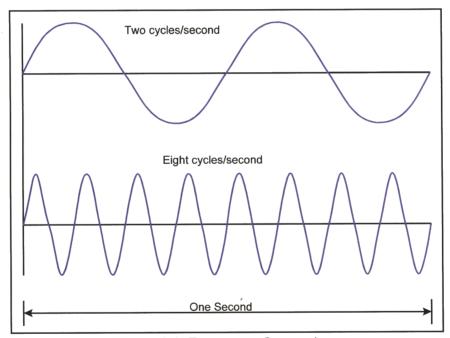


Figure 1.4. Frequency Comparison

- a) Cycle. A cycle is one complete series of values, e.g. the graph of Figure 1.4.
- b) Phase. A sine wave can be given an angular notation called phase. One cycle represents from 0° 360° of phase.

Frequency. The number of cycles occurring each second is the frequency of the supply. The frequency is measured in Hertz (Hz). One cycle per second is equal to one Hertz. Constant frequency AC supply systems usually have a frequency of 400 Hz. Frequency is dependent upon the number of times a North and a South pole pass the armature in a given time period.

To determine the frequency of a generator output, the following formula can be used:-

Number of Poles
$$\frac{R.P.M.}{2}$$
 = Frequency in hertz 60 (secs)

The number of poles is the total of North and South poles making up the field of the generator and the RPM is the speed of rotation in revolutions per minute.

For example, an 8 pole generator rotating at 6,000 R.P.M. will have an output frequency of :-

$$\frac{8}{2}$$
 6.000 = 400 Hertz

d) **Period.** The period is the time it takes for one cycle to occur. It is the reciprocal of the frequency:-

Period (T)
$$= 1/f$$
 seconds

- e) **Amplitude or Peak Value**. The amplitude of a sine wave is the maximum value it attains in one cycle, see Figure 1.5
- f) **Root Mean Square Value.(r.m.s)**. The effective value of an alternating current is calculated by comparing it with **Direct Current**. The comparison is based on the amount of heat produced by each current under identical conditions.

ie. A DC current of 1 amp will make a resistor hotter than AC with peak value of 1 amp. So to make the resistor as hot with an AC current its peak value must be higher so that its effective value can be 1 amp.

The effective value is termed the **Root Mean Square**, which is found by taking a number of instantaneous values of voltage or current (whichever is required) during a half cycle.

These values are squared and their mean (average) value determined. Obtaining the square root of the mean value gives the Root of the Mean of the Squares, **the r.m.s. value.**

Another way of looking at it is that the voltage (or current) rises from zero to maximum in 90° of phase angle, the average value must occur at the midway point of 45°. As the values follow a sine curve as previously described then the value at 45° is a product of the **Peak value** multiplied by the **Sine of 45° (0.707).**

Therefore the r.m.s. value of alternating current (or voltage) is related to its **amplitude or peak** value. For a sine wave, the relationship is given by the formula:-

r.m.s. =
$$\underbrace{\text{PEAK VALUE}}_{\sqrt{2}}$$
 Or r.m.s. = 0.707 X PEAK VALUE

Most AC supply values are given in r.m.s. terms. In general terms, ammeters and voltmeters are calibrated in r.m.s. values also.

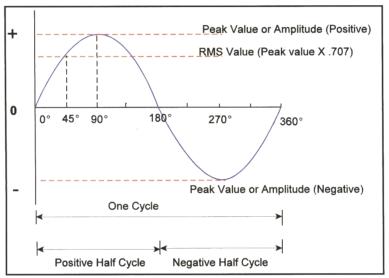


Figure 1.5 AC Terminology

1.4 THE RELATIONSHIP OF CURRENT AND VOLTAGE IN AN AC CIRCUIT.

Current and voltage in an AC circuit have the same frequency and the wave form (the shape of the cycle) is similar, i.e. if the voltage waveform is sinusoidal then the current waveform is also sinusoidal.

In a DC circuit the current flow was directly affected by the applied voltage and circuit resistance, in the relationship formulated by OHMS law (I=E/R). ie. The current is directly proportional to

the voltage and inversely proportional to the resistance.

There are very few AC circuits in which the current is affected solely by the applied voltage and resistance such that both the current and the voltage pass through zero and reach their peaks in the same direction simultaneously. In such circuits voltage and current are said to be **in phase** and the circuit is said to be **resistive.**

In most circuits however because of the ever changing values of voltage and current, the current flow is influenced by the **magnetic and electrostatic** effects of **inductance and capacitance** respectively, which causes the current and voltage to be **out of phase**. This means that although they are at the same frequency, the voltage and current **do not pass through zero at the same time**. The difference between corresponding points on the waveforms is known as **phase difference or phase angle**. Inductive and Capacitive circuits will be studied later in this text.

1.5 RESISTANCE IN AC CIRCUITS.

There is no such thing as a 'pure resistance' when considering an AC circuit. All resistors, even a piece of wire, have 'inductance' as well as resistance, but for the purpose of studying AC theory in this chapter we have to assume that we can build separate circuits having only resistance, inductance or capacitance.

In the resistive circuit, then, we are assuming 'pure resistance'

The voltage and current waveforms when AC is applied across a pure resistive circuit are sine waves. Both waveforms are **in phase** as shown in Figure 1.6, and Ohms Law applies as in DC circuits, remembering that values quoted will be r.m.s. values.

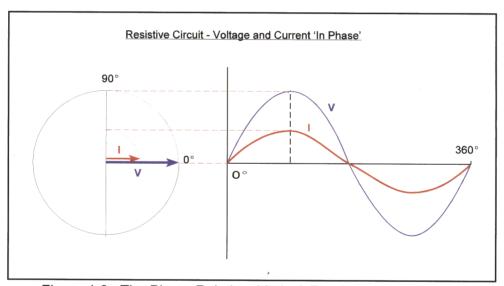


Figure 1.6. The Phase Relationship in A Purely Resistive Circuit

INTENTIONALLY

BLANK

1.6 INDUCTANCE IN AC CIRCUITS

In section 1.2, in a simple generator a change of flux through a conductor **induced** a voltage in that conductor, by rotating the conductor relative to the magnetic field. A different kind of generator uses a **rotating magnetic field** and a stationary **conductor**. Both rely on the physical movement of conductor or field.

A change of flux in a coil can be achieved without physical motion, by varying a current flow, thereby changing the magnetic field relative to a coil. Figure 1.7 shows how voltages can be induced in this manner.

Figure 1.7a shows a DC circuit containing a coil, controlled by a switch, this is the **primary circuit**, with no current flow there is no magnetic field created in the coil. Alongside the primary circuit is another circuit containing a coil and an ammeter, this is the **secondary circuit**. As there is no current flow in the primary circuit there will be nothing happening.

In Figure 1.7b the switch has been made and a magnetic field is produced by the current flow through the coil which expands while the current is increasing. This magnetic field 'cuts' the coil in the secondary circuit as it is expanding, thereby inducing a voltage and current flow which will show by a deflection of the ammeter. When the current is stable at its maximum the magnetic field will be stable and there will be no induced voltage. Therefore the meter in the circuit will kick sharply as the switch is closed and return to zero when the magnetic field becomes static.

In Figure 1.7c the switch has been opened and there is a rapid collapse of the magnetic field because the current flow has ceased, inducing a voltage in the secondary circuit. The meter will kick in the opposite direction as the field collapses to zero.

Figure 1.7d and e show an AC circuit, With an ever changing and alternating current flow in the circuit the magnetic field will be constantly changing therefore there will be a continually induced voltage and current flow proportional to the AC waveform. This will be indicated by the ammeter needle swinging alternately left and right. The greatest voltage will be induced when the current is changing at its greatest rate ie when it is changing polarity.

This is called **mutual induction** and is the principle of operation of transformers. The magnitude of the induced voltage is dependent on the rate of change of magnetic field which is proportional to the frequency of the supply.

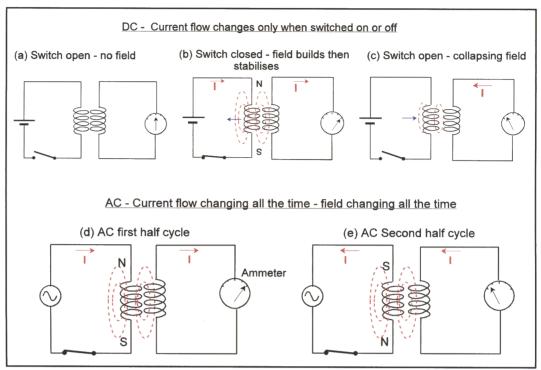


Figure 1.7 Inductance

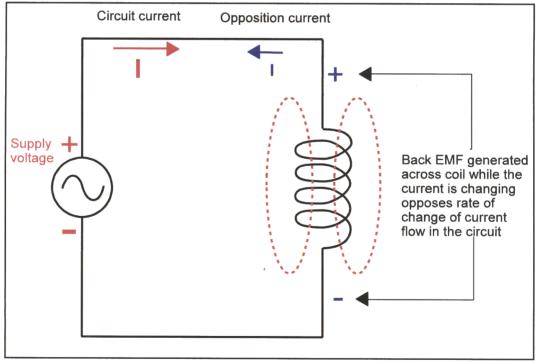


Figure 1.8 Self Induction

Referring to Figure 1.8, the secondary circuit has been removed, but the AC supply still generates an ever changing magnetic field which has the effect of inducing a voltage in the coil itself. This is called **self induction** and according to **Lenz's law** the voltage induced will oppose any change of current in the circuit. This self induced voltage is often referred to as the Back EMF.

The amount of inductance in any circuit can be measured by the size of the induced voltage. A number of factors affect induced voltage.

- a) The **number of turns** in the coil (stronger magnetic field)
- b) The addition of a **soft iron core** in the coil (stronger magnetic field)
- c) An increase in the rate of change of current (increase in frequency)

Items a and b refer to the construction of the coil itself and determine the value of the self

inductance for a given frequency. This is referred to as the **Inductance** of the coil and is a measure of its ability to produce a back emf. A coil with a high value of inductance will produce a greater back emf than one with a small value for the same supply frequency.

Any device having inductance can be referred to as an **inductor**. The unit of inductance is the **Henry** and its symbol is a capital **L.** Inductance is usually expressed in milli-Henries or micro-Henries as the Henry is too large a unit for practical use. A circuit has an inductance of **one Henry** if a current change of **one ampere per second** induces a **Back e.m.f. of one volt.**

The effect of inductance in an AC circuit is to cause the voltage and current to be out of phase, because of the opposition to the current flow the rise in current is held back behind the rise in voltage ie. **current lags voltage**.

In a circuit having only inductance the current lags the voltage by 90°. This is illustrated in Figure 1.9.

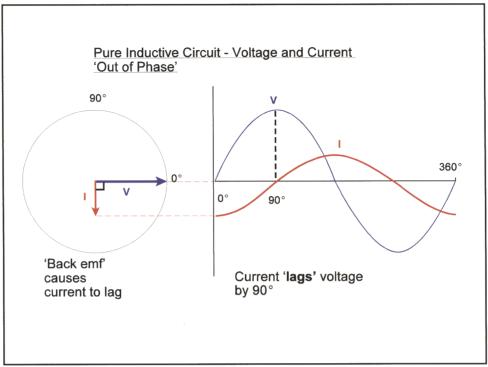


Figure 1.9 The Phase Relationship in A Purely Inductive Circuit

1.7 INDUCTIVE REACTANCE

The opposition to current flow in this circuit is called the **Inductive Reactance**.

It is called reactance rather than resistance because the effects of inductance depend on the frequency of the supply as well as the value of the inductance.

Inductive reactance is measured in **Ohms** and is given the symbol X_L .

To determine inductive reactance the following formula can be used.

$$X_L = 2 \pi f L$$

Where π is a constant, f is the frequency, L is the inductance

From this formula it can be seen that as **frequency increases the value of inductive reactance increases** so the circuit current would decrease. Conversely, and more importantly, as the circuit frequency decreases the inductive reactance decreases and the circuit current increases.

1.8 CAPACITANCE IN AC CIRCUITS

Capacitance is the ability of a circuit to store an electrical charge. A device used to introduce capacitance into a circuit is known as a **Capacitor**. A capacitor consists of two plates separated by a Dielectric, see Figure 1.10. Dielectrics can be, amongst other things, air, mica or waxed paper.

Three factors affect the amount of charge a capacitor can hold.

They are;-

- a) The area of the plates.
- b) The distance between the plates.
- c) The material used to separate the plates, the dielectric.

The capacitor will store an electric charge, much like a hydraulic accumulator stores fluid under pressure, but first it needs to be charged.

When connected to the battery as shown in Figure 1.10 electrons will be removed from the plate connected to the positive terminal of the battery and added to the plate connected to the negative terminal, conventional current flow will be from positive to negative. This process will continue until the plates become saturated and no more current will flow.

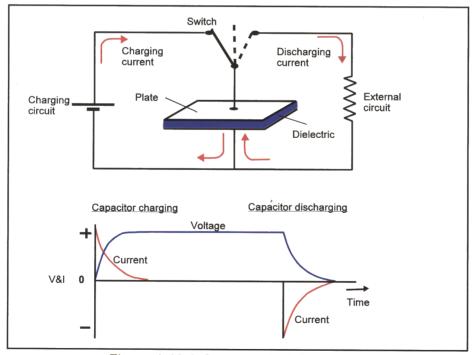


Figure 1.10 A Capacitor in A DC Circuit

The potential difference between the plates is at its maximum and the capacitor is now fully charged, its voltage being equal to the battery voltage.

If the switch is now moved to a mid position the charging circuit is disconnected and the capacitor will hold its charge indefinitely, in a similar fashion to an accumulator. (In practice there will be some leakage which allows the capacitor to discharge over a period of time).

Using the switch to connect the capacitor to the external circuit will allow the capacitor to discharge and current will flow around the circuit in the opposite direction until the potential difference across the plates has equalised. Notice that the capacitor has discharged in the opposite direction to which it was charged. Note also that electrons do **not** pass between the plates through the dielectric

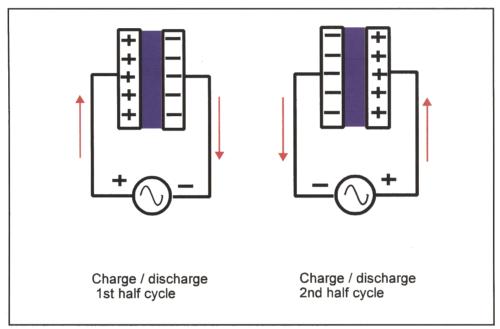


Figure 1.11 Capacitor in An AC Circuit

When fitted in an AC circuit as shown in Figure 1.11 the capacitor will be constantly charging and discharging as the applied voltage and current flow are constantly reversing polarity and direction. As the applied voltage falls the capacitor discharges current back into the circuit in the opposite direction and its voltage falls.

This has the effect of shifting the voltage out of phase with the current, and in a purely capacitive circuit the **current will lead the voltage by 90°** see Figure 1.12.

The unit of capacitance is the **Farad**, and a capacitor is given the symbol **C**. If a current of lampere flowing for 1 second creates a potential difference of 1 volt between the plates of a capacitor then it is a 1 Farad capacitor. Because of the values involved a 1 Farad capacitor is not a practical size, a more common unit is the micro-farad or pico farad.

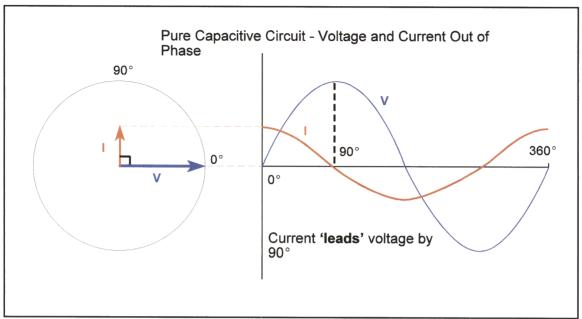


Figure 1.12. Phase Relationship in A Purely Capacitive Circuit

1.9 CAPACITIVE REACTANCE

The opposition to current flow in this circuit is called **Capacitive Reactance**. As in the inductive circuit the amount of reactance is dependent upon frequency and the value of the capacitor in Farads. Capacitive reactance is measured in **Ohms** and is given the symbol X_C . It can be calculated by using the following formula:-


$$X_C = \underline{} 1$$
 $2 \pi f C$

From this formula it can be seen that as **frequency increases the value of capacitive reactance decreases** so the circuit current will increase. Conversely if frequency decreases capacitive reactance increases and circuit current will decrease.

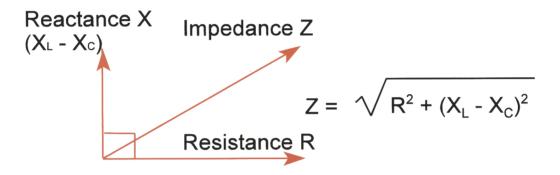1.10 IMPEDANCE

The total opposition to current flow in an AC circuit is a combination of Resistance, Inductive reactance and Capacitive reactance. But because in each circuit there is a different phase relationship between the voltage and current they cannot simply be added together.

Inductive reactance can be thought of as having the opposite effect to capacitive reactance as in one circuit the current lags the voltage by 90° and in the other the current leads the voltage by 90° , so they are 180° apart and the total reactance can be found by subtracting one from the other. Impedance is the vector sum of the resistance and total reactance and represents the total opposition to current flow measured in Ohms and given the symbol Z



Pictorially this can be shown as vectors in an impedance triangle, from which it can be seen that resistance is out of phase with reactance by 90°:-

Mathematically the vector sum of the two can be expressed using Pythagoras' Theorem.

1.11 RESONANT CIRCUITS

Changes of supply frequency in a circuit will have the opposite effect on capacitance and inductance. An increase of supply frequency will increase the inductive reactance (XL) and decrease the capacitive reactance (XC). Increasing XL will cause the current in the circuit to decrease and decreasing the XC will cause the current to increase.

The manner in which the inductance and capacitance react in an opposite fashion to changes of supply frequency means that there will be one specific frequency for each circuit at which their values will be equal.

When the Capacitive Reactance and the Inductive Reactance in a circuit are Equal the circuit is said to be Resonant.

If a capacitor and an inductance are placed in series each other, at the resonant frequency the current flowing in the circuit will be maximum. If on the other hand the capacitor and inductance are placed in parallel with each other, the current flowing in the circuit at resonant frequency will be minimum.


SUMMARY SO FAR

a) The Voltage and Current phase relationship in reactive circuits can be remembered using the following mnemonic:-

C I V I L

In a Capacitive circuit, I current leads Voltage leads I current in an L inductive circuit.

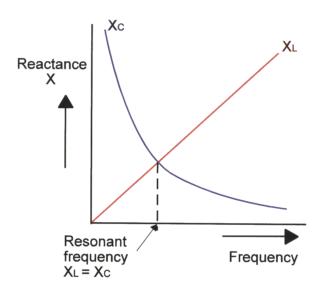b) The effect of frequency variation on inductive and capacitive reactance is shown in the following graph.



1.12 POWER IN AC CIRCUITS

The power absorbed in a DC circuit, according to OHMS law is the product of the Voltage and the Current. So it is in AC circuits. However due to the change in phase relationship between voltage and current in reactive circuits the actual power absorbed is not necessarily the same as the power apparently supplied.

Once again the Resistive, Inductive and Capacitive circuits need to be examined separately and then a practical circuit having a combination of all three is considered.

1.13 POWER IN A PURELY RESISTIVE CIRCUIT

The power in a resistive circuit is the average value of all of the instantaneous values of power for a complete cycle. The instantaneous power value is found by multiplying the instantaneous values of current and voltage. If this process is carried out over a full cycle it will give the power curve shown in Figure 1.13.

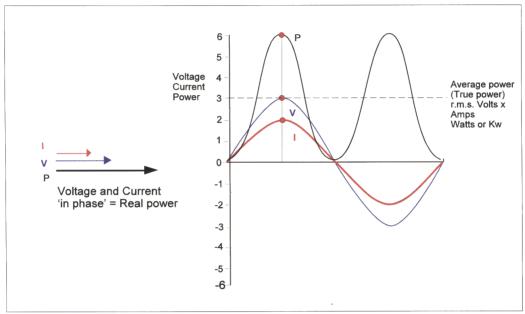


Figure 1.13 Power in A Purely Resistive Circuit

Notice that the Power curve is **always positive** because the voltage and current are **in phase** and its frequency is twice that of the voltage and current.

This positive power is known as the **True Power**, **Real Power or Wattfull Power** and its value is the product of the r.m.s. current and the r.m.s. voltage. It is measured in **Watts or Kilowatts** (KW).

The average power over a complete cycle is the average value of the power curve and can be represented by a line drawn halfway between the minimum and maximum values

1.14 POWER IN A PURELY INDUCTIVE CIRCUIT.

Figure 1.14 shows a purely inductive circuit where the current 'lags' the voltage by 90° . It can be seen that by plotting instantaneous values of current times voltage we can obtain the waveform of instantaneous power.

The axis of that power waveform is the same as that of the voltage and current but its frequency is double.

If the axis of all the waveforms is the same, then the **positive power is equal to the negative power**. The positive cycle represents power given to the circuit to generate the magnetic field, and the negative cycle is power given back by the circuit in generating the back EMF.

Thus in a circuit that contains only inductance, **the true power is zero** and only the power required that is necessary to overcome the inductive reactance is absorbed. This called **reactive power** and is the product of the voltage and current that is 90° out of phase. It is measured as Volts x Amps Reactive **VAR or KVAR**.

The product of the r.m.s. voltage and the r.m.s. current in this circuit is known as the **apparent power** and is measured in **VA** or **KVA**.

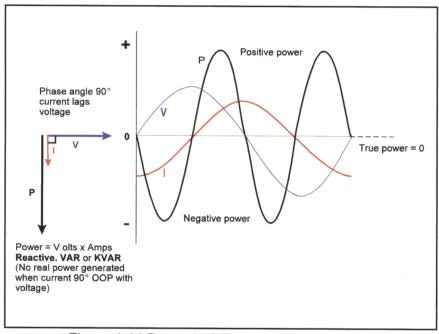


Figure 1.14 Power in A Purely Inductive Circuit

1.15 POWER IN A CAPACITIVE CIRCUIT

Power in a purely capacitive circuit is very similar to the inductive circuit, because the current is also out of phase with the voltage, but this time leading Refer to Figure 1.15, once again the positive power is equal to the negative power thus no real power is absorbed. The power required is only overcoming the capacitive reactance. When the voltage and current are 90° out of phase the power required is all **reactive power (VAR or KVAR).**

As before the r.m.s. volts x r.m.s. amps is apparent power (VA or KVA).

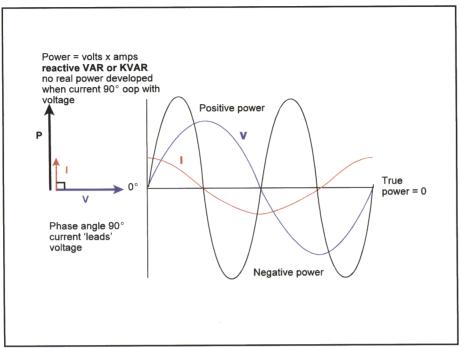


Figure 1.15 Power in A Purely Capacitive Circuit

1.16 POWER IN A PRACTICAL AC CIRCUIT

A practical AC circuit will always have some resistance and some inductance, the amounts of each will depend on the construction of that circuit. An AC circuit may also have capacitance if capacitors are fitted.

Calculating power therefore depends on the ratio of resistance in a circuit to the inductance or capacitance (remember that inductance has the opposite effect to capacitance so if both are present in a circuit the effects of one will cancel out some of the other leaving the circuit more inductive or capacitive depending on which one is more dominant, the resistance will always be there)

Figure 1.16 shows a circuit having equal resistance and inductance, notice the phase angle is 45° and that the amounts of positive power and negative power are **not** equal.

A line dividing the power curve into two equal areas would show the average power consumed in that circuit. The "average power" in a circuit with both resistance and inductance is the **true** power (KW) consumed in that circuit.

The **apparent power (KVA)** is the r.m.s. volts x amps and the **reactive power (KVAR)** is the amount of power required to overcome the inductive reactance.

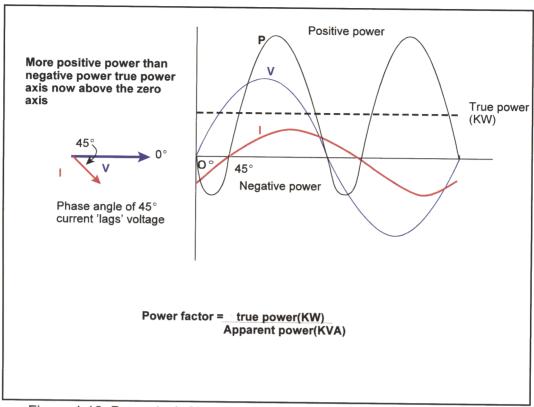


Figure 1.16 Power in A Circuit Having Equal Amounts of Resistance and Inductance

1.17 POWER FACTOR

There is a definite relationship between the apparent power and the true power, the value of each will change with the ratio of resistance to inductance (or capacitance) and therefore with the **phase angle.**

The greater the phase angle the greater will be the apparent power compared with the true power, and vice versa. This relationship is called the **power factor** and can be calculated as the **ratio between True Power and Apparent power**

In a purely inductive (or capacitive) circuit the True power would be Zero and the phase angle will be 90° so from the formula we can deduce that the Power Factor must also be Zero, its minimum value.

Decreasing the phase angle increases the True Power and increases the Power Factor.

In a purely resistive circuit the phase angle will be zero and the true power will equal the apparent power so the power factor will be its maximum or 1.

The power factor can also be calculated as the cosine of the phase angle

ie. As every good pilot should know, $\cos 0^{\circ} = 1$, $\cos 90^{\circ} = 0$

1.18 POWER FACTOR RESUME.

Below is a list of facts relating to the Power Factor. It may be of use when revising the subject so far.

- a) Apparent Power = the product of r.m.s. voltage and current in one half cycle.
- b) Apparent Power can also be called the Theoretical Power or Rated Power. It is measured in VAs or KVAs.
- c) True Power = Apparent Power, but only if the voltage and the current are in phase.
- d) True Power = Zero, but only if the voltage and the current are 90° out of phase.
- e) True Power can also be called the Real Power, the Effective Power, the Wattful Power or the Working Power consumed in the circuit.
- f) True Power is measured in Watts or Kilowatts.
- g) Real Power = the voltage * the current * the power factor.
- h) **Reactive Power** is measured in **KVAR**'s.
- i) <u>TRUE POWER</u> = POWER FACTOR APPARENT POWER

CHAPTER TWO - ALTERNATORS

Contents

	Page
2.1	INTRODUCTION TO AIRCRAFT POWER SUPPLIES 2.2 - 1
2.2	GENERATORS /ALTERNATORS 2.2 - 1
2.3	ROTATING ARMATURE ALTERNATOR 2.2 - 1
2.4	ROTATING FIELD ALTERNATOR
2.5	ALTERNATOR OUTPUT RATING 2.2 - 2
2.6	A SINGLE PHASE ALTERNATOR
2.7	POLYPHASE CIRCUITS
2.8	THREE PHASE ALTERNATOR CONNECTIONS 2.2 - 4
2.9	THE FOUR WIRE STAR CONNECTION 2.2 - 5
2.10	DELTA CONNECTED ALTERNATOR 2.2 - 7
2.11	PRACTICAL AC GENERATORS
2.12	BRUSHED ALTERNATORS
2.13	BRUSHLESS ALTERNATORS
2.14	FREQUENCY WILD ALTERNATORS
2.15	OBTAINING A CONSTANT FREQUENCY SUPPLY FROM A FREQUENCY WILD SYSTEM
2.16	CONSTANT FREQUENCY ALTERNATORS
2.17	CONSTANT SPEED GENERATOR DRIVE SYSTEMS 2.2 - 11
2.18	CSDU FAULT INDICATIONS IN THE COCKPIT 2.2 - 12
2.19	THE DRIVE DISCONNECT UNIT
2.20	VARIABLE SPEED CONSTANT FREQUENCY POWER SYSTEMS (VSCF)2.2-13
2.21	SELF EXCITED GENERATORS
2.22	LOAD SHARING OR PARALLELLING OF CONSTANT FREQUENCY
	ALTERNATORS
2.23	REAL LOAD
2.24	REACTIVE LOAD. 2.2 - 14
2.25	PARALLEL CONNECTION
2.26	BEFORE CONNECTING IN PARALLEL. 2.2 - 15
2.27	LAYOUT OF A PARALLELLED SYSTEM
2.28	REAL LOAD SHARING 2.2 - 17
2.29	REACTIVE LOAD SHARING 2.2 - 18

2.30	LOAD SHARING GENERAL 2.2 -	- 19
2.31	ALTERNATOR COOLING	- 20
2.32	GENERATOR FAULT PROTECTION 2.2 -	- 20
2.33	BUS TIE BREAKERS (BTB)	- 20
2.34	DISCRIMINATORY CIRCUITS 2.2 -	- 21
2.35	DIFFERENTIAL FAULT PROTECTION 2.2 -	- 21
2.36	SYNCHRONISING UNITS	- 21
2.37	GENERATOR FAILURE WARNING LIGHT	- 22
2.38	LOAD METERS	- 22
2.39	VOLTAGE AND FREQUENCY METERS 2.2 -	- 22
2.40	GENERATOR CONTROL UNIT	- 22
2.41	EMERGENCY SUPPLIES 2.2 -	23
2.42	RAM AIR TURBINE (RAT)	23
2.43	AUXILIARY POWER UNIT (APU) 2.2 -	23
2.44	STATIC INVERTER	23
2.45	GROUND POWER CONSTANT FREQUENCY SUPPLY SYSTEM 2.2 -	- 24
2 46	TYPICAL CONTROLS AND INDICATIONS 2.2	25

2.1 INTRODUCTION TO AIRCRAFT POWER SUPPLIES.

The requirement for more power to operate larger pieces of electrical equipment as passenger aircraft grew in size now means that most large commercial aircraft use alternating current distribution systems.

The industry standard that has evolved for constant frequency aircraft is:

115/200v AC, 3 phase, 400 Hz.

And the requirement for DC is satisfied by converting AC to 28v DC using transformer rectifier units (TRU's), while retaining the battery for emergency use.

The distribution system is laid out in a similar fashion to the DC aircraft using a system of Busbars having a distinct hierarchy, the emphasis being placed on the ability of the system to cope with failure with the minimum loss of electrical services.

As in a DC system the AC generators can be operated in parallel if the designer requires.

This chapter will explain different types of AC generator, their operation, control and protection and some typical aircraft AC systems.

2.2 GENERATORS / ALTERNATORS.

In a DC generator the rotating part is always the armature. In an AC generator this is not generally true.

Another name for an AC generator is Alternator.

There are two types of alternator:-

- a) Rotating Armature.
- b) Rotating Field.

2.3 ROTATING ARMATURE ALTERNATOR.

The rotating armature alternator is similar in construction to a DC generator, the **armature rotates** in a **stationary magnetic field**. As it does so, an e.m.f. is induced into it, and this e.m.f., rather than being converted to DC as it is in the commutator of a DC machine, is taken out as AC through **Slip Rings**.

The rotating armature is only used in very small output alternators and are not generally used for supplying AC systems.

2.4 ROTATING FIELD ALTERNATOR.

Most practical alternators are designed with a **rotating field** and a **stationary armature** so that the rotor, the moving part, carries the field windings. The field can either be energised by a **permanent magnet or by DC from a separate source**.

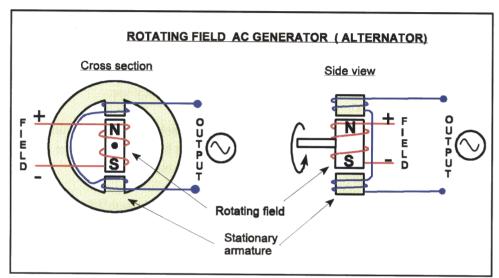


Figure 2.1. Rotating Field Alternator

N.B The field MUST be energised by DC to keep the correct polarity in the rotor.

One advantage of a rotating field alternator is that only a low current is fed through slip rings to the field windings.

The **output** is taken from the stationary armature windings, which means that problems associated with arcing from the brush gear are greatly reduced. Figure 2.1 illustrates a simple rotating field alternator.

2.5 ALTERNATOR OUTPUT RATING.

The maximum output current from an alternator depends on the amount of heating loss which can be sustained in the armature. This power loss heats up the conductors and can, in extreme cases, destroy the insulation of the windings. Alternators are rated in terms of this armature current as well as by their voltage output. Thus every alternator is **rated** in **Volt Amperes (VA)** or **Kilo Volt Amperes(KVA)**, the Apparent Power.

2.6 A SINGLE PHASE ALTERNATOR.

A single phase alternator has its stator windings connected in series to supply the output. The stator windings (coils) are connected so as to be series-aiding, so that the induced voltages in them are **in phase**. The rotor consists of two poles of opposite polarity. This is illustrated in Figure 2.2.

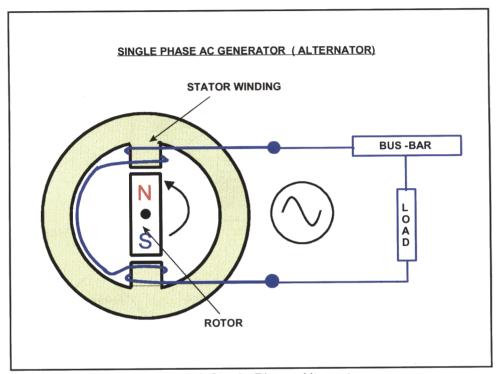


Figure 2.2 Single Phase Alternator

The output of this type of machine will rise to a maximum in one direction, then fall to zero, rise to a maximum in the other direction and then fall to zero again.

2.7 POLYPHASE CIRCUITS.

Polyphase or "multi-phase" alternators have **two or more single phase windings** symmetrically spaced around the stator.

The number of separate stator windings determines the number of phases present in the supply. The currents and voltages generated in this type of machine will have the same the same frequency but be out of phase with each other.

Corresponding values of voltage or current will be separated by an equal number of degrees. The most common polyphase alternator is the **three phase alternator** which has become the standard AC distribution system for aircraft. This is illustrated in Figure 2.3.

Note that the phase windings are **mechanically** arranged to be at 120° to each other in the sequence A,B,C so that the outputs are **electrically** separated by 120° as shown in the diagram. It can be seen that "A" phase reaches a peak going positive before "B" phase reaches a peak going positive before "C" phase reaches a peak going positive. This is the **phase sequence ABC**

The peak values of the voltages induced in the three single phase windings of the three phase alternator shown in Figure 2.3 are 120° displaced from each other. The three phases are independent of each other.

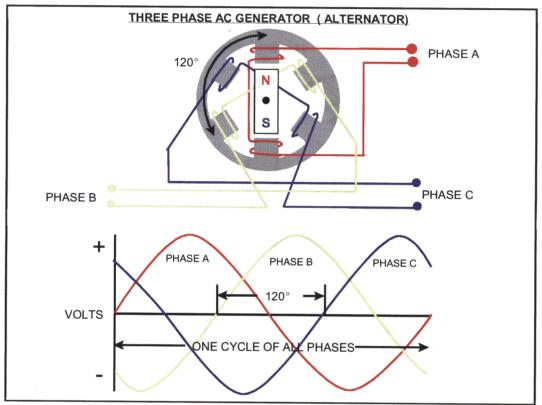


Figure 2.3 Three Phase Alternator

The advantages of a three phase system are:-

- a) They have a greater power / weight ratio.
- b) They are easier to work in parallel.

2.8 THREE PHASE ALTERNATOR CONNECTIONS.

The outputs of a three phase alternator can be connected by either the "Star" or "Delta" method. These connections are shown in Figure 2.4.

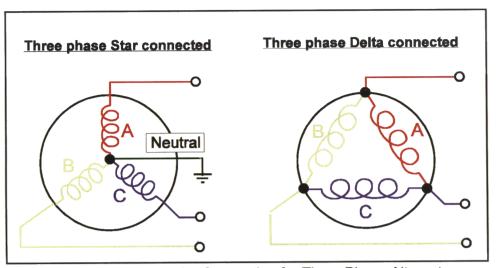


Figure 2.4 Star and Delta Connection for Three Phase Alternators

2.9 THE FOUR WIRE STAR CONNECTION.

A star connected three phase alternator has the three phases joined at one end to form a fourth connection known as the neutral point. Refer to Figure 2.5.

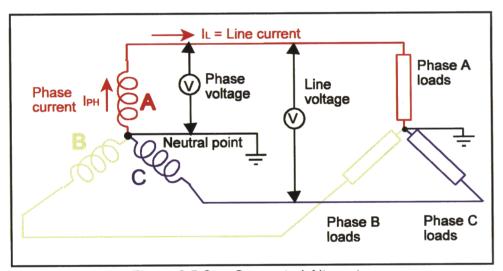


Figure 2.5 Star Connected Alternator

The **neutral point** is normally **grounded** and used as the **earth return** in modern aircraft. The neutral line will carry any out of balance current. This means that if there is an earth fault on one phase, the neutral will carry an exceptionally high load.

This is the type of alternator that will be fitted to a typical aircraft distribution system because it can cope with different loads on each bus bar, the delta connection can not.

The connection at the opposite end of the phase from the neutral is called **the line connection**. A voltmeter measuring the **potential difference between** the **neutral** and the **line lead** would read **phase voltage**. A voltmeter measuring the **potential difference** between **two line connections** would read **line voltage**.

In this type of alternator the **phase** voltage and **line** voltage are different because phase voltage is measured across **one phase** whereas line voltage is measures across **two phases** and is the vector sum of the two.

Given one or the other of these values, the following formula will enable the student to establish the missing criterion:-

LINE VOLTAGE = 1.73 **★** PHASE VOLTAGE

Note :- $(1.73 = \sqrt{3})$

The line voltage of a typical aircraft supply system would be 200 volts, from the formula above it can be seen that the phase voltage would be;-

To be more specific, a modern aircraft power supply would be 115/200 volts, 3 (phase), 400 Hz.

While the **voltages** of line and phase differ in the "star" connected system, because the windings form only one path for current flow between phases:-

LINE CURRENT = PHASE CURRENT

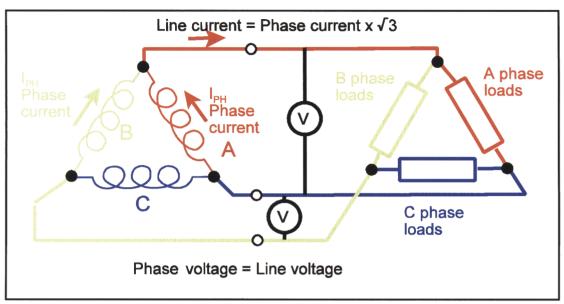


Figure 2.6 Delta Connected Alternator

2.10 DELTA CONNECTED ALTERNATOR.

As can be seen from Figure 2.6, in this system the ends of the phases are joined together to form a closed mesh and the loads are connected in a similar fashion.

Logically, because the potential measured across the phase is measured between two lines, then:-

LINE VOLTAGE <u>IS</u> PHASE VOLTAGE

BUT

LINE CURRENT = PHASE CURRENT $X\sqrt{3}$

This type of connection will not be used in a practical distribution system because it cannot cope with unbalanced loads as there is no neutral point. However they may be used for specific purposes eg. speed sensors or tacho generators.

2.11 PRACTICAL AC GENERATORS.

Rotating Armature alternators suffer from various disadvantages :-

- a) The rotating coils are heavy and centrifugal forces are high
- b) Efficient insulation of the rotating coils is difficult.
- c) The resistance across the brushes to the sliprings is high.
- d) The rotating coils are difficult to cool.
- e) They have a poor power to weight ratio.

Rotating Field alternators make up the majority in use. From the previous sections it will be seen that in this type of alternator the field is in the rotor and the phase windings form the stator.

There are two types of rotating field alternator in use on aircraft:-

- a) Brushed alternators.
- b) Brushless alternators.

2.12 BRUSHED ALTERNATORS.

The current supply for the excitation of the rotor field can be provided initially from the aircraft DC bus bar (battery) and then subsequently by rectified AC The DC current is directed through brushes and slip rings to the rotating field.

Control of the excitation current is by the **voltage regulator** which samples the alternator output (115v AC) and adjusts the excitation current to maintain the correct voltage irrespective of the alternator speed.

The voltage regulator in its simplest form is a variable resistance connected in series with the field coil (the principle of the carbon pile regulator in the DC book).

Fig 2.7 shows a block diagram of a Brushed Alternator.

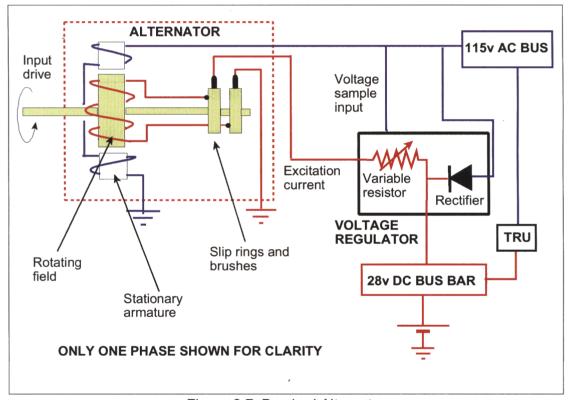


Figure 2.7 Brushed Alternator

2.13 BRUSHLESS ALTERNATORS

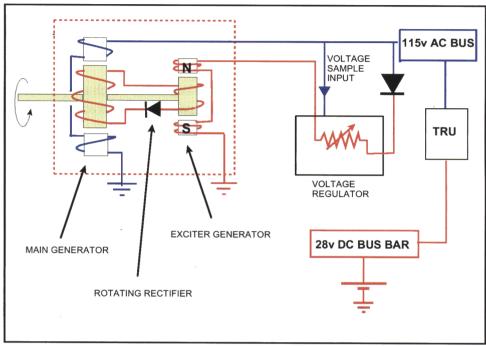


Figure 2.8 Brushless Alternator

A brushless alternator incorporates an exciter generator mounted on the same shaft as the main generator. The purpose of the exciter generator is to provide a current for the main generator rotating field. The rotating rectifier converts the AC produced in the exciter armature to DC required for the main rotor field supply.

Voltage regulation is effected by controlling the Exciter field strength and thereby the current strength at the main rotor field coil.

Brushless alternators have some advantages over brushed alternators

- a) They are very reliable.
- b) There are no brush wear problems.
- c) They have a high power to weight ratio.

Modern brushless alternators may have a third generator on the same shaft called a Permanent Magnet Generator (PMG) which provides excitation current for its exciter generator.

Alternator output is usually 200 (line) / 115 (phase) volts @ 400 Hz. There are two basic types of brushless alternator:-

- a) Externally excited. (No residual magnetism in the exciter)
- b) Self excited. (Some residual magnetism in the exciter)

2.14 FREQUENCY WILD ALTERNATORS

If an alternator is driven directly from the engine gearbox, then its speed, and therefore the frequency of its output will vary directly with engine speed. An output from such a generator is said to be **Frequency Wild**.

NB. The connection of two frequency wild generators in parallel is not possible.

Frequency wild alternators are usually used on aircraft to power the electrical de-icing systems, where the resistances that make up the heater mats are not affected by changing frequencies.

2.15 OBTAINING A CONSTANT FREQUENCY SUPPLY FROM A FREQUENCY WILD SYSTEM.

Inverters can be used to give a constant frequency output from a frequency wild supply. The frequency wild AC is rectified to DC which is used to power either a **Rotary** or **Static Inverter** which then converts DC to constant frequency AC.

2.16 CONSTANT FREQUENCY ALTERNATORS

If an alternator can be driven at a constant speed, then the output frequency will be constant. Driving the engine at a constant speed is not a practical proposition so a device is required to keep the speed of the alternator constant irrespective of the engine speed.

2.17 CONSTANT SPEED GENERATOR DRIVE SYSTEMS.

The Constant Speed Drive Unit (C.S.D.U) consists of an engine driven hydraulic pump, the output of which drives a hydraulic motor which itself in turn drives the alternator.

The oil which forms the medium through which the mechanism operates and also facilitates lubrication and cooling, is contained within a reservoir, entirely separate from the engine oil system.

The output of the hydraulic pump, and therefore the speed of the hydraulic motor, depends on the angle of a swashplate within the pump. The angle of the swashplate is controlled by a device called a **speed governor**. The speed governor is controlled by the **load controller** which senses the output frequency of the alternator and is responsible for increasing or decreasing the torque output of the C.S.D.U. to the alternator drive.

Most C.S.D.U.s are capable of maintaining the alternator output frequency within 5% of 400 Hz (380 - 420 Hz).

In the event of a mechanical failure in the alternator the C.S.D.U. is protected by a **Quill Drive**, this is the equivalent of a weak link which will break before any major damage can be caused.

The CSDU operates in one of three modes overdrive, straight through drive or underdrive.

- a) overdrive = engine speed less than generator speed
- b) straight through drive = engine speed same as generator speed
- c) underdrive = engine speed greater than generator speed

Some constant frequency generators have their CSDU and generator combined in one unit called an Integrated Drive Unit (IDU) or Integrated Drive Generator (IDG)

2.18 C.S.D.U. FAULT INDICATIONS IN THE COCKPIT.

There are several indications in the cockpit associated with the Constant Speed Drive Unit and the problems which might occur with it. The two main ones are:-

- a) **Low Oil Pressure Warning Lights**. These will illuminate when the oil pressure drops below a predetermined minimum value.
- b) **High Oil Temperature warning.** Monitors the CSDU oil outlet temperature.

2.19 THE DRIVE DISCONNECT UNIT (DOG CLUTCH DISCONNECT).

In the unlikely event of a malfunction in the C.S.D.U. or the alternator, the engine input drive to the C.S.D.U. can be disconnected. This will allow both the drive unit and the alternator to become stationary, thus eliminating any chance that the malfunction will affect engine performance.

The disconnection can be carried out at any time the engine is running, although reconnecting may only be done "manually" on the ground following shut down of the engine.

Figure 2.9 illustrates a CSDU and drive disconnect mechanism. The disconnect unit is operated by the selection of a momentary action 'Drive Disconnect' switch by the pilot. This operates a solenoid which causes a mechanical separation of the input drive from the engine to the constant speed unit. Exceptionally some aircraft may allow automatic disconnection of the generator drive by a generator control unit (GCU) under certain fault conditions.

Modern units can have the CSDU and generator in one unit. These are called **Integrated Drive** Units (IDU's) or Integrated Drive Generators (IDG's).

Some IDG's are known as as **Permanent Magnet Generators (PMG's)**. The generator has three separate generators on the same shaft, a **permanent magnet generator** which provides for initial excitation of the **exciter generator** which controls the **main generator** field. This type of generator is invariably controlled by a Generator Control Unit (GCU) paragraph 2.40

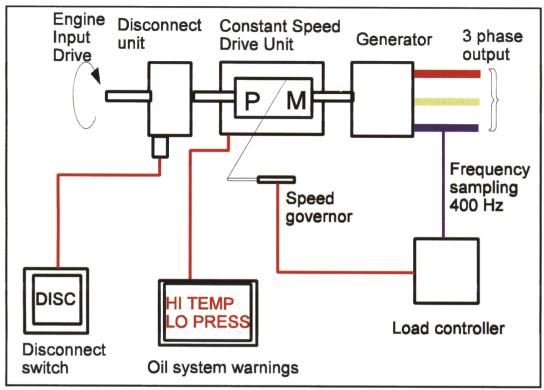


Figure 2.9.

2.20 VARIABLE-SPEED CONSTANT FREQUENCY POWER SYSTEMS (VSCF)

A variable speed constant frequency system (VSCF) utilises a frequency wild generator driven by the engine and the variable frequency out put is electronically converted into a constant frequency 400 Hz supply. The conversion is achieved by a generator converter control unit (GCCU) which first passes the variable frequency supply through a full wave rectifier where it is rectified and filtered and then to an inverter where it is formed into a 3 phase 400 HZ AC supply. This of course eliminates the need for a hydro mechanical CSDU and all its associated controlling mechanisms. This improves reliability and flexibility on the installation as the electronic circuit does not necessarily have to be located in the engine compartment with the generator. VSCF systems are currently fitted to Boeing 737 aircraft and several military aircraft. The VSCF also incorporates a built in test facility which can provide fault isolation information to the ground engineer.

2.21 SELF EXCITED GENERATORS.

A self excited generator is one which has some **permanent magnetism** in its exciter generator. On initial rotation, the flux from these **Stationary Permanent Magnets** causes an induced AC voltage an therefore current to flow in its rotor. The rotor output is then fed directly to a rotating rectifier which in turn supplies the rotating field coils of the main generator with a DC supply.

The output of the main generator stator is tapped to provide a regulated supply to the exciter field so enabling the voltage to be controlled.

2.22 LOAD SHARING OR PARALLELLING OF CONSTANT FREQUENCY ALTERNATORS.

When running two or more constant frequency alternators in parallel they must be controlled in order that each one takes a fair and equal share of the load.

This "load sharing" or "parallelling" requires that two parameters are regulated :-

- a) Real Load.
- b) Reactive Load.

2.23 REAL LOAD.

Real Load is the actual working load output available for supplying the various electrical services and it is measured in Kilowatts (real power or true power see 1.16).

Real Load is directly related to the mechanical power or torque which is being supplied to the alternator drive by its prime mover, i.e. the engine or CSDU.

Real Load Sharing is achieved by controlling the Constant Speed Drive Unit (C.S.D.U.) and adjusting the torque at its output shaft so that if the torque of the two or more CSDU's is equal then the real load taken by each generator is the same.

2.24 REACTIVE LOAD.

Reactive Load is the so-called Wattless Load which is the vector sum of inductive and capacitive currents and voltages **expressed in KVARs** (Kilo Volt-Amperes Reactive again see 1.16).

Reactive Load Sharing is achieved by controlling the Voltage Output (Exciter Field Current) of each generator that is connected in parallel. If their voltages are identical then the reactive load on each generator will be the same.

2.25 PARALLEL CONNECTION.

To control the real and reactive load when two or more generators are paralleled there are two separate load sharing circuits, one to detect and control real load and one to detect and control reactive load.

N.B. It must be emphasised that until a generator is connected in parallel with one or more others it will **not** be connected into the load sharing circuits. While constant frequency alternators are operating as individual units, such as at engine start when only one alternator may be on line, their **Real Load and Reactive Load sharing circuits are not connected**.

2.26 BEFORE CONNECTING IN PARALLEL.

AC generators, or alternators, are **synchronous machines** which will lock frequencies when they are operated in parallel. The system frequency thus becomes that of the alternator with the highest load.

However if the two alternators are at different frequencies before they are connected in parallel then damage can occur as one generator tries to slow down and the other tries to speed up, so they must be at the **same frequency before paralleling.**

As well as being at the same frequency they must also be of the same **phase sequence**, ie at any point in time phase A,B and C on the first generator must be identical to phase A, B and C on the second generator.

The **Voltage** of each generator being paralleled must also be the same.

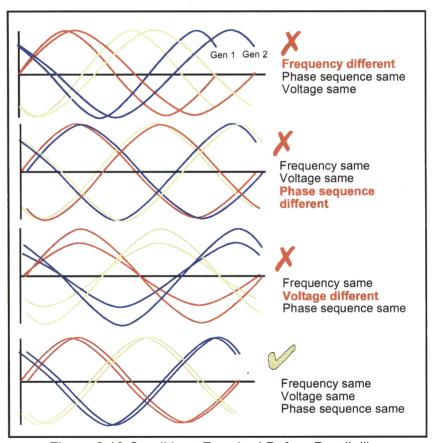


Figure 2.10 Conditions Required Before Parallelling

2.27 LAYOUT OF A PARALLELLED SYSTEM

Figure 2.11 shows a diagrammatic layout of a three generator parallelled system. Notice that for each of the three phases of the output there is a separate bus bar, for example the No1 generator bus bar (Gen Bus1) is made up of three separate bus bars A, B and C for phases A, B and C. The generator is connected to its own bus bar through a 3 phase circuit breaker called the Generator Circuit Breaker (GCB), operated automatically or controlled from the flight deck. All the electrical loads of the aircraft are shared between the three generator bus bars.

To operate the generators in parallel they are connected through their respective generator bus bars to a **synchronising bus bar** via a **Bus Tie Breaker (BTB)**. A Bus Tie Breaker is another 3 phase circuit breaker controlled automatically or manually from the flight deck.

The synchronising bus bar takes no electrical loads at all, it is only there to allow the engine driven generators to be operated in parallel. Ground power or power from the APU generator can be connected into the synchronising bus and from there can be fed to the load bus bars through the BTB's when the engine generators are not operating and the GCB's are open.

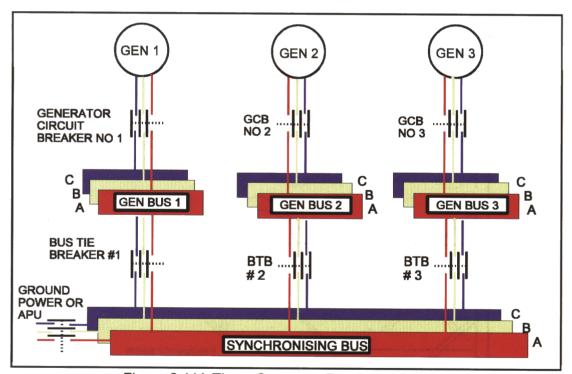


Figure 2.11A Three Generator Parallelled System

2.28 REAL LOAD SHARING

The **Load Controller** controls the basic frequency of the AC generator (400Hz).

After parallelling the load controllers work as a team to evenly share the real load by increasing the torque input to the lower speeding alternators drive and decreasing the torque input to the higher speeding alternators to ensure each alternator takes an equal share of the load.

Current transformers sense the **Real Load** distribution at the output of each of the parallelled alternators.

When current flows through these transformers voltage is induced in them and a current flows in the **Load Sharing Loop**. Each of the current transformers, which are connected in series with each other in the loop, has an **Error Detector** wired in parallel with it.

If it is assumed initially in Figure 2.12 that conditions of balanced load have been attained, then the current output of each current transformer can also be assumed to be 5 amperes and no current will flow through the error detectors.

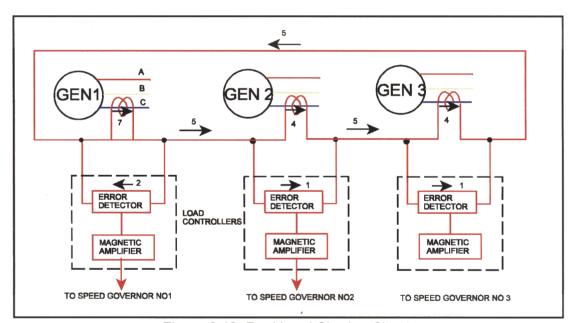


Figure 2.12 Real Load Sharing Circuit

Now imagine that the drive unit of the N° 1 alternator increases its torque output, it will take a bigger share of the load than the other two alternators which will decrease by a proportional amount.

The output of the N° 1 alternator current transformer has increased to 6 amperes for arguments sake, this will mean that the output of the No2 and 3 transformer will decrease to 4 amps so that the average current flowing in the circuit is still 5 amperes.

According to Kirchoff's first law the difference between each current transformer and the average current will be pushed through the error detectors in opposite directions. This signal, when amplified, will be sent to the speed governors to tell the CSDU for the No 1 Gen to reduce torqueand the CSDU's for the No 2 and 3 Gen to increase torque until the current in each transformer is once again equal and the real load is once again balanced.

Real load sharing is controlled by matching CSDU speed (torque).

2.29 REACTIVE LOAD SHARING.

The **reactive load** sharing circuit shown below looks very similar to the real load sharing circuit. It works in a similar fashion but it is a completely separate circuit.

The sensing of out of balance loads by the current transformers is the same but this time the error detector needs to know the difference between the **reactive loads** carried by each generator. The mutual reactor is a phase shifting transformer which ensures that the error detector only detects that part of the current which is 90° out of phase with the voltage (reactive load). The error signal is then amplified and correcting signals are sent to the **generator field circuit** to increase the voltage on the low voltage generator and reduce the voltage of the higher voltage generator to balance the reactive load.

Reactive load sharing is controlled by the Voltage Regulators matching voltage outputs (field excitation).

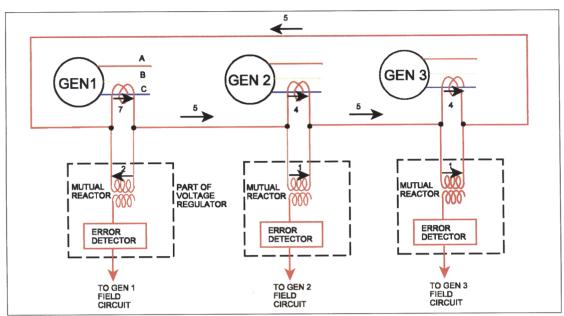


Figure 2.13 Reactive Load Sharing Circuit

2.30 LOAD SHARING GENERAL

It is typical to run three and four generator systems in parallel but most modern twin engined aircraft wih two generators run the generators in isolation (Split Bus System).

In those three and four generator systems the load sharing circuits operate as shown above but are extended to cater for the required number of generators.

If any generator in a parallel sytem is not connected in parallel then it will not be connected to the load sharing circuits either.

REMEMBER:

Real load sharing - Reactive load sharing -

speed, torque (CSDU) excitation, field current (Voltage Regulator)

2.31 ALTERNATOR COOLING.

The heat generated in the alternator stator windings due to the current flow through them means that some form of cooling system is required. Those systems with frequency wild generators or constant frequency generators with separate CSDU's typically use **ram air cooling** in flight and some means to induce an airflow on the ground.

IDG's or IDU's use their oil to cool the stators which is then cooled in its own oil cooler.

2.32 GENERATOR FAULT PROTECTION.

When constant frequency alternators are paralleled, then the requirement for other Control and Protection devices becomes apparent.

There follows a non-exhaustive list of some of those devices:-

- a) Bus Tie Breakers (B.T.B.s)
- b) Discriminatory circuits.
- c) Differential Fault Protection circuits.
- d) Synchronising Units.
- e) Failure Warning systems.
- f) Load meters.
- g) Voltage and Frequency meters.
- h) Generator Control Units (GCU)

2.33 BUS TIE BREAKERS (B.T.B.s).

A bus tie breaker connects two bus bars together. In a paralleled system it connects an alternator to the **synchronising bus bar**. The synchronising bus bar allows two or more alternators to be connected in parallel with each other while the B.T.B.s are closed. Control of the B.T.B. can be automatic or manual dependent on the type of aircraft. Correct signals from a **Synchronising Unit** (monitoring voltage, frequency and phase sequence) must be available before the B.T.B. will close and put the alternator in parallel with another. In a parallelled system the BTB's are normally closed and open under fault conditions. In a Split Bus system (non parallelled) the BTB is normally open and closes under fault conditions.

Visual indication of the position of the B.T.B.s is given by indicators on the electrical control panel or the electronic display panel.

2.34 DISCRIMINATORY CIRCUITS.

When alternators are paralleled, **Discrimination Circuitry** is required to ensure that in the event of a failure, **only the faulty system is disconnected** from the appropriate bus bar. This is achieved by selective switching of the GCB's and BTB's.

2.35 DIFFERENTIAL FAULT PROTECTION.

Control and protection devices must be included within the power supply circuits. These will monitor system performance and **appropriately operate** the relevant circuit breakers, G.C.B.s BTB's etc. This may be achieved by a component known as a **bus power control unit (BPCU)** which monitors the system by current transformers placed at each generator and at each bus bar. It will isolate a defective generator or faulty bus bar and reconfigure the electrical system to maintain the maximum usage.

Protection is provided for ;-

- a) Over / Under Voltage.
- b) Over / Under Frequency.
- c) Over / Under Excitation.
- d) Differential Current Faults, (short circuits between bus bars or bus bar to ground, or open circuit faults unbalancing phase outputs).

2.36 SYNCHRONISING UNITS.

Before the alternator can be connected to a bus bar which is common to another alternator its **voltages**, **frequency and phase sequence** must be within very strict limits and in the same order. The **Synchronising Unit** ensures that these values are within limits before it will allow connection to a common bus bar. There are two methods in use:-

- a) Automatic Control.
- b) Manual (Dark Lamp) Method.

Automatic control will not allow the B.T.B. or GCB to close and parallel the generators until the voltage, frequency and phase sequence of the oncoming generator is within limits This may be achieved by circuitry within a bus bar protection control unit or in the Generator Control Units (GCU's) of a modern IDG system.

The Manual (Dark Lamp) method is a much older method but remains in use on a few aircraft. Synchronising Lights on the alternator control panel will show when there are differences between phases of two supplies. Synchronisation is indicated when the lamps are "dark" and then the BTB. or GCB can be closed by means of the manual switch.

2.37 GENERATOR FAILURE WARNING LIGHT.

A Generator Failure Warning Light will illuminate when its associated G.C.B. is tripped. The Centralised Warning System will operate simultaneously with the Generator Warning Light and in some aircraft Aural Warnings are generated.

Aircraft with electronic systems management display units will show the failure and the associated schematic display.

2.38 LOAD METERS.

KW/KVAR Meters are used in paralleled alternator systems to indicate the Real Power (KW) or the Reactive Power (KVAR) output Only one meter may be used to indicate both parameters, selection of a switch will determine which of the two is shown. Typically the switch is selected so that the KW output is normally displayed.

The Real Load is the part of the alternator output which is available to do work at the bus bar.

The **Reactive Load** is the part of the alternator output which is used to create electromagnetic and electrostaticeffects in the circuits. It is the so-called Wattless Load which is the vector sum of the Inductive and capacitive Currents and voltages.

Load meters on modern electronic display units may only show a percentage of the maximum power being taken.

2.39 VOLTAGE AND FREQUENCY METERS.

Voltage and frequency indications are also provided for each generator. Typically only one voltmeter and one frequency meter is provided in systems with several alternators in circuit. The voltage or frequency of any alternator can be selected by a **Multi-position Switch**. The switch can usually be positioned to show not only the supply frequency and voltage of the engine driven alternators, but also that of the auxiliary power unit, the ground power unit or the Emergency Ram Air Turbine, if provided.

2.40 GENERATOR CONTROL UNIT (GCU)

In a modern generator control system a Generator Control Unit (GCU) houses circuitry to provide many functions of power control and protection. A typical GCU will monitor generator output and provide voltage regulation by controlling the exciter field current. Protection circuitry will monitor for over voltage and over current, frequency, phase sequence and differential current protection. A GCU will be provided for each generator and they may work as a team with the BPCU (para 2.35) in controlling fault isolation switching.

The GCU may also house an Exciter Control Relay otherwise known as a Generator Control Relay or Generator Field relay. The exciter control relay controls the exciter field current supply to the generator field. In the event of a dangerous fault occurring (over excitation or over voltage) the fault protection circuit will open the exciter control relay which will cause the generator output to fall to a residual value making it safe. The GCU will also open the generator circuit breaker (GCB) to disconnect the generator from its bus bar. (In a parallelled system power would be maintained to the generator bus bar from the other generators through the BTB).

2.41 EMERGENCY SUPPLIES.

In the unlikely event of some or all of the engine driven AC power generation systems on the aircraft failing, alternative methods of supply must be made available. Some alternative means of providing AC are listed below;

- a) Ram Air Turbine (R.A.T)
- b) Auxiliary Power Unit (A.P.U.)
- c) Static Inverter.
- d) Hydraulic Motor driven generator.

2.42 THE RAM AIR TURBINE (R.A.T.)

The Ram Air Turbine (R.A.T. or E.L.R.A.T.), when lowered into the slipstream of an aircraft in flight will produce an emergency source of AC power. The output is controlled at a nominal 200 / 115 volts, three phase 400 Hz. It will give limited operation only of Flight Instrument and Radio services in the event of Total Alternator Failure. (RAT's driving an electrical generator have been largely superceded by RAT's driving a hydraulic pump, as modern aircraft are more dependent on hydraulic power)

2.43 THE AUXILIARY POWER UNIT (A.P.U).

The Auxiliary Power Unit (A.P.U.) is usually a small gas turbine engine mounted in the aircraft tailcone. This engine runs at a constant speed and has its own protection devices in the event of a Fire, Low Oil Pressure, High Oil Temperature, Overspeed or Overheat.

It can be used, among other things, to drive a 200 / 115 volt, three phase alternator for ground servicing supplies, or, in some aircraft, for emergency supplies in the air.

The A.P.U. alternator cannot normally be paralleled with the engine driven alternators, and will usually only supply power to the bus bars when no other source is feeding them.

2.44 THE STATIC INVERTER.

A Static Inverter is a Solid State Device capable of supplying the aircraft with 115 volts at 400 Hz for the limited operation of instrument and radio services.

It is powered by the aircraft batteries or from an essential DC Bus Bar.

2.45 GROUND POWER CONSTANT FREQUENCY SUPPLY SYSTEM.

The standard modern **Ground Power Unit** output is 200 / 115 volts, three phase at 400 Hz.

When plugged into the aircraft it can be used to supply all the aircraft electrical services. The ground power unit circuitry must embody automatic protection systems which ensure that ground power;-

- a) cannot be connected to the aircraft distribution system if the system is already being supplied by its own alternators.
- b) cannot be connected if the phase sequence of the supply is incorrect.
- c) will be rejected and switched off at source if over voltage occurs.

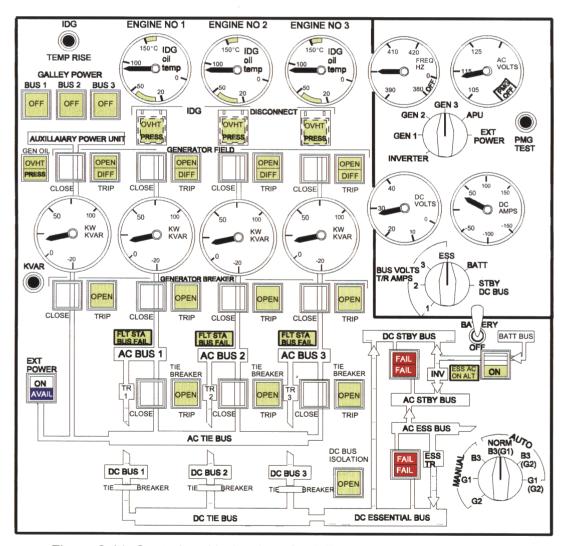


Figure 2.14 Control and Indications for A Three Engine Parallel System

2.46 TYPICAL CONTROLS AND INDICATIONS

Figure 2.14 shows typical controls and indications for a three engine parallelled system. This type of panel uses "switchlights". these are a combination switch and indicator, either having a momentary or alternate action eg. push once to activate (Gen disconnect switch) or push once to switch "on", then push a second time to switch "off" (Galley power on/off). The indicator shows switch position or system status.

Each engine drives a constant frequency generator (Integrated Drive Generator or IDG). Oil temp indications are shown along with overheat and low pressure warning lamps in the disconnect switch. The disconnect switch is guarded to prevent inadvertant operation.

The APU also drives a generator but this one does not need a constant speed unit because the APU runs at a constant speed.

The generator field switchlights control the field excitation circuit (exciter control relay), the "flowbar" in the "close" switchlight illuminates to indicate the generator field is complete and the voltage and frequency can be checked by selecting the required generator on the rotary switch and reading off the voltmeter and frequency meter in the upper right corner of the panel .The "trip" switchlight opens the field circuit to reduce the generator voltage to zero.

The Generator Circuit Breaker (GCB) is controlled by the GCB switchlights (close/trip) which connect or disconnect the generator to it's own AC bus bar or the APU to the AC Tie Bus. The load on each generator can be monitored by the Real/Reactive load indicator showing KW or KVAR. The gauge normally shows KW but KVAR can be shown by pressing and holding the KVAR button to the left of the gauges.

The BTB's are controlled in the same manner to connect the generator busses to the AC tie bus for parallel operation, all three generators are normally connected in parallel to share the total aircraft electrical load.

Each AC bus feeds a TRU which converts 200v/115v AC to 28v DC to power the individual DC busses, these too are normally parallelled through tie breakers which are all controlled by the DC Bus Isolation switch.

The DC part of the system can also be checked for Voltage and Current by use of the other rotary selector and meters for DC Volts and Amps

The Standby bus bars can be fed from the normal electrical supply (AC and DC) or from the battery in the event of a total supply failure. The Red fail lights indicate no voltage on the essential or Standby busses.

CHAPTER THREE - PRACTICAL AIRCRAFT SYSTEMS

Contents

		Page
3.1	POWER DISTRIBUTION	2.3 - 1
3.2	THE SPLIT BUS SYSTEM	2.3 - 1
3.3	THE PARALLELLED BUSBAR SYSTEM	2.3 - 4

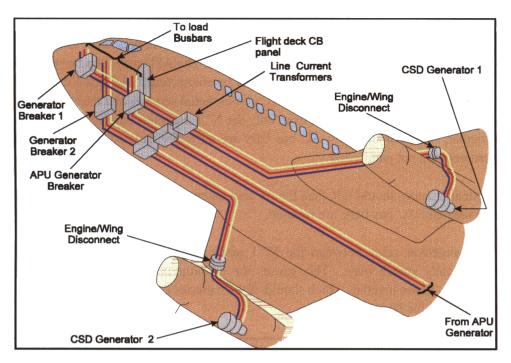


Figure 3.1. Generator Feeder Lines.

3.1 POWER DISTRIBUTION.

In a very basic form, Figure 3 shows the general layout of an electrical distribution system for a twin jet aircraft. One generator is driven by and mounted on each engine and one generator is mounted on the APU (not shown). The feeder cables from each generator are routed through the aircraft wings and fuselage to meet at a central distribution compartment usually beneath the flight deck or cabin floor. This distribution compartment will house many of the components already described: GCB's, BTB's, GCU's or Voltage regulators, current transformers, main busbars and busbar protection circuitry, battery and battery charger. Busbars and busbar extensions may be found on the flight deck behind the rear, side and overhead circuit breaker panels.

A schematic diagram for this type of system is shown at fig.3.2

3.2 THE SPLIT BUS SYSTEM.

The Split Bus Bar System uses 115/200v 3 phase constant frequency alternators as the primary power source. They are not designed to run in parallel and therefore do not require complex parallelling and load sharing circuits. A 28v DC supply is provided by two Transformer Rectifier Units (T.R.U.s) convert 115v AC to 28v DC from the two separate AC bus bars. A battery is provided which will provide power to start the APU and limited emergency power to the essential busbars.

If, in the circuit shown in Figure 3.2, either alternator should fail, then the main bus bars are automatically connected by the Bus Tie Breaker and they will now serve as one bus bar. Power supplies to all the bus bars are thereby maintained. The APU may then be started in flight and its generator can be used to restore full power by connecting to AC bus 1 or bus 2. While each alternator separately supplies its own AC non-essential services and the associated T.R.U., the essential AC loads are supplied from only the No 1 main bus bar via a changeover relay. In particular, note that the main AC bus bars are normally isolated from one another, i.e. the alternators are not parallelled

If both alternators should fail, then the AC non-essential services, which are normally supplied from the main AC bus bars, are isolated.

The changeover relay between the No 1 main bus bar and the essential AC bus bar will automatically switch over. This causes the essential AC bus bar to be connected to an Emergency Static Inverter, which should, if the batteries are in a fully charged state, supply the essential AC for 30 minutes.

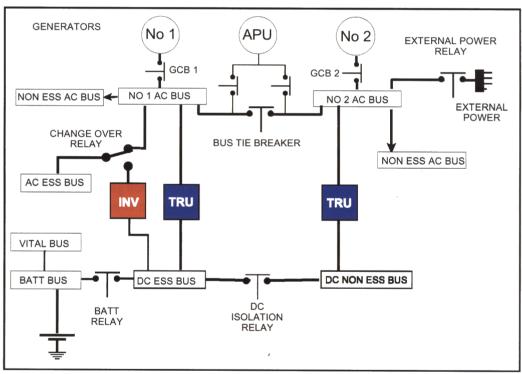


Figure 3.2 Split Bus System

Under normal conditions, the DC supply in Figure 3.2 is obtained from the two independent T.R.U.s. and batteries.

The N° 1 T.R.U. supplies essential DC loads and the N° 2 T.R.U. supplies non-essential DC loads.

In normal operation the two bus bars supplying the essential and non-essential DC loads are connected together by the Isolation Relay. The batteries are connected directly to the Battery Bus Bar, and through the Battery Relay they feed the essential DC bus bar.

If one alternator fails then both T.R.U.,s are still supplied through the now closed contacts of the bus-tie breaker, and will still supply all of the DC consumers.

If however both alternators fail, the DC Isolation Relay will open and sepatare the essential and non-essential bus bars.

Non-essential loads will now no longer be powered, but the AC and DC essential loads will be fed from the battery bus bar, (the AC loads from the static inverter).

External power or supplies from the A.P.U. can be used to feed all electrical services in the aircraft on the ground, but the APU generator may only be capable of supplying one bus bar in flight.

Figure 3.3 and 3.4 show the control panel and ECAM display screen for an Airbus A320, a typical Split System type layout.

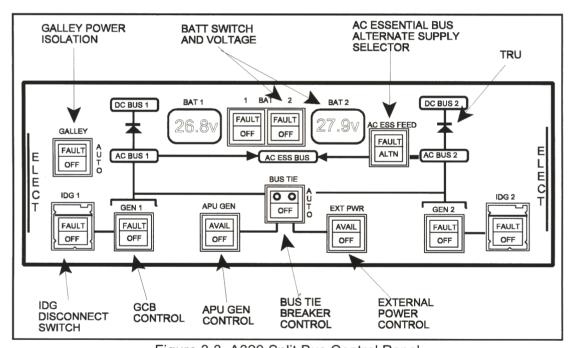


Figure 3.3 A320 Split Bus Control Panel

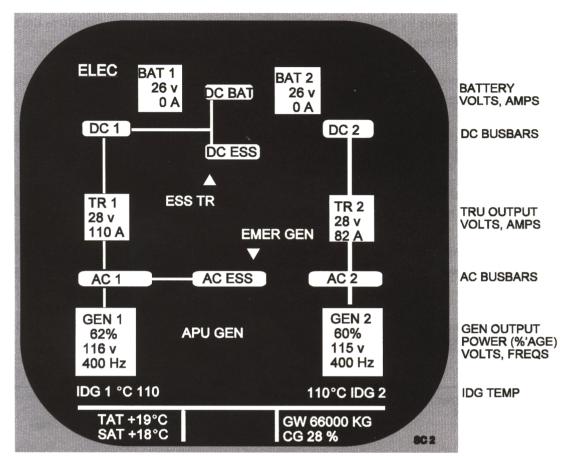


Figure 3.4m A320 ECAM Display

3.3 PARALLEL BUSBAR SYSTEM

Figure 3.5 illustrates a four generator parallelled system. This system allows various combinations of alternator operation. Operation of the system begins with the excitation of the alternator field which will bring its output within the limits required before operation of the G.C.B. can occur.

When the G.C.B. closes it connects its associated alternator to its Load Bus Bar. Once the G.C.B. has closed it will remain closed during all normal circuit functioning.

The Bus Tie Breakers are normally closed so that the closure of the G.C.B. effectively connects the alternator to the Synchronising Bus Bar. If the other one of a pair of alternators (1 & 2) or (3 & 4) now comes "on line" it too will be joined in parallel to the synchronising bus bar, but only once the voltage, frequency and phase sequence have been satisfied allowing its GCB to close.

In the system described there are two synchronising bus bars which can be combined or isolated by the Split System Breaker (S.S.B.) depending on the flight phase or other system requirement. Keeping the synchronising bus bars isolated from each other will allow the alternators to operate as two parallelled pairs which would be a requirement for example during an dual autopilot autoland to enable the two autopilots to have totally separate power supplies.

If a single alternator failure occurs with a system similar to that shown in Figure 3.5, then opening of the associated G.C.B. will allow its paired alternator to feed the loads of both of them. However, this would place a larger load upon that alternator than is being carried by the pair on the other synchronising bus bar.

Closure of the S.S.B. would bring all three alternators into parallel operation, thus sharing the total aircraft load between them. Failures are not always that simple however, if there was an earth fault on a load bus bar for instance, opening of the associated G.C.B. would do little to help, the other alternator/s would now be attempting to feed the earth fault. Operation of the B.T.B. associated with the faulty bus bar would prevent the serviceable alternators being affected by the fault, and then the earth fault could be totally isolated by opening the G.C.B. of the alternator feeding it.

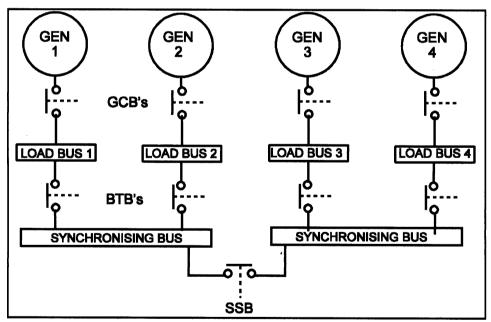


Figure 3.5 Parallel Alternator Operation

An example of an aircraft with this type of parallelled system is the Boeing 747 - 400. Shown below in Figures 3.6. and 3.7. are the control panel and the EICAS display for the electrical system.

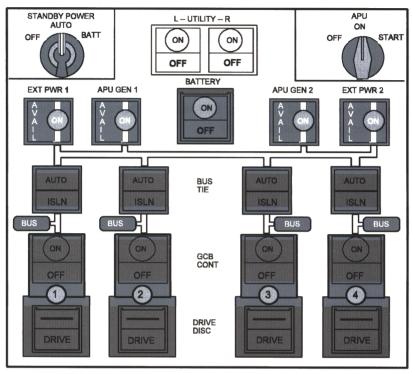


Figure 3.6 747 - 400 Electrical Control Panel

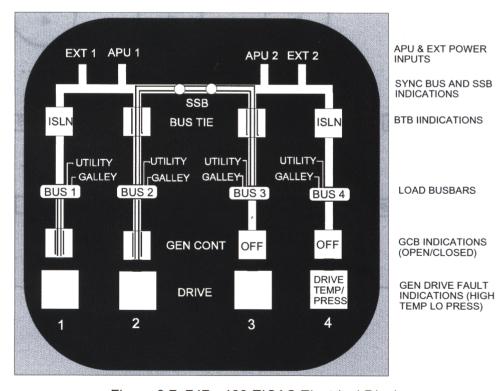


Figure 3.7 747 - 400 EICAS Electrical Display

CHAPTER FOUR - TRANSFORMERS

Contents

		Page
4.1	TRANSFORMERS	2.4 - 1
4.2	TRANSFORMATION RATIO	2.4 - 1
4.3	POWER IN A TRANSFORMER	2.4 - 2
4.4	THREE PHASE TRANSFORMERS	2.4 - 2
4.5	AUTO TRANSFORMERS	2.4 - 2
4.6	RECTIFICATION OF ALTERNATING CURRENT	2.4 - 3
4.7	HALF WAVE RECTIFICATION.	2.4 - 4
4.8	FULL WAVE RECTIFICATION	2.4 - 4
4.9	THREE PHASE RECTIFIERS	2.4 - 5
4 .10	TRANSFORMER RECTIFIER UNITS (TRU'S)	2.4 - 6
4.11	INVERTERS	2.4 - 6

4.1 TRANSFORMERS.

One of the biggest advantages that an AC supply has over a DC supply is the ease with which the value of alternating voltage can be raised or lowered with extreme efficiency by the use of Transformers.

A simple transformer would consist of two electrically separate coils wound over iron laminations to form a common core. This forms a completely closed magnetic circuit. See Figure 4.1.

The Primary winding is connected to the AC supply and the output is taken from the Secondary winding.

The alternating voltage and current in the primary winding creates an alternating flux which links across to the secondary winding.

The alternating flux in the secondary winding sets up an e.m.f. of mutual inductance which is available as the output voltage. The out put voltage will be 180° out of phase with the input voltage. If a load is placed across the terminals of the secondary winding then a current will flow in the circuit.

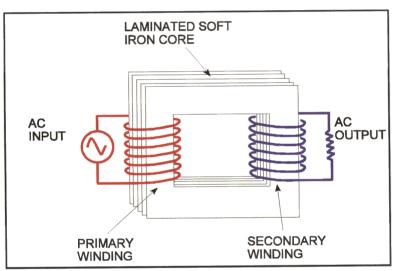


Figure 4.1 A Simple Transformer

4.2 TRANSFORMATION RATIO.

The Transformation Ratio of a transformer is the ratio of the number of turns of wire on the secondary winding (N2) to the number of turns of wire on the primary winding (N1). The transformation ratio will also allow the determination of input and output voltages by using the formula:-

TRANSFORMATION RATIO (r) =
$$\frac{N2}{N1}$$
 = $\frac{E2}{E1}$

If the transformation ratio is greater than one, then the transformer is a Step Up transformer. If the ratio is less than one, then the transformer is a Step Down transformer. See Figure 4.2.

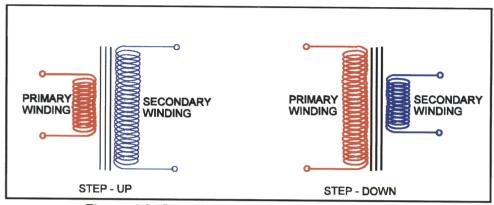


Figure 4.2 Step Up and Step Down Transformers

4.3 POWER IN A TRANSFORMER.

If we ignore the very small losses that do occur in a transformer, then we can say that the power that goes into a transformer equals the power that comes out of it. The power in either the primary winding or the secondary winding is equal to the product of the voltage times the current in either winding.

4.4 THREE PHASE TRANSFORMERS.

The output of a three phase alternator can be transformed by either ;-

a) 3 SINGLE PHASE TRANSFORMERS

or

b) 1 THREE PHASE TRANSFORMER

A three phase transformer consists of the primary and secondary windings of each phase wound on one of three laminated iron limbs.

4.5 AUTO TRANSFORMERS.

Where AC is required for the operation of instruments on the aircraft, an Auto Transformer can be utilised to either step down, or sometimes even step up, the source supply, the supply usually required for instruments is 26 volts AC

An auto transformer is a single winding on a laminated core to form a closed magnetic circuit. Figure 4.3. illustrates the relationship between the primary and secondary in an auto transformer.

It should be noted that part of the winding carries both the primary and secondary current because it is common to both windings.

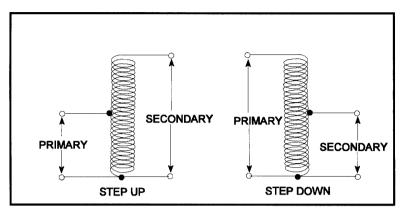


Figure 4.3 Auto Transformers

Auto transformers are less expensive than two coil transformers because they use less wire, however, they do not electrically isolate the primary and secondary windings and so cannot be used in many circuits for this reason.

4.6 RECTIFICATION OF ALTERNATING CURRENT.

A Rectifier is a device which will convert Alternating Current into Direct Current. The operation of the Diode Rectifier is described in the Semiconductor chapter and is a very common device in modern aircraft solid state circuits. It can be used to convert AC to DC or as a "Blocking Diode" (electrical non return valve) to prevent reverse current flow in a DC system.

A diode has a high resistance in one direction and a low resistance in the other. The accepted symbol for a diode rectifier and the direction of conventional current flow is shown in Figure 4.4.

4.7 HALF WAVE RECTIFICATION.

A diode inserted in the secondary circuit of a transformer will allow current to flow through the load in one direction only. This is termed Half Wave Rectification. The bottom half of the AC waveform is blocked and the frequency of the output is the same as the input, as shown in Figure 4.4.

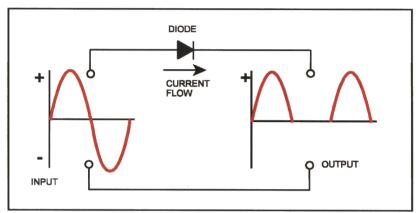


Figure 4.4 Single Phase, Half Wave Rectification

4.8 FULL WAVE RECTIFICATION.

To fill in the gaps between pulses that have been left from half wave rectification a Bridge Rectifier can be used. As can be seen from Figure 4.5, when one half of the bridge circuit is presenting a high resistance to current flow, the other half is allowing it to flow relatively easily. This arrangement is specifically designed to allow the output of the bridge to be of a single polarity. The output can be smoothed to some extent by the addition of a capacitor placed across it

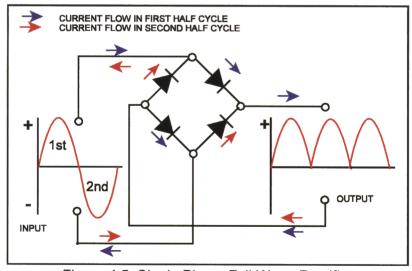


Figure 4.5 Single Phase Full Wave Rectifier

4.9 THREE PHASE RECTIFIERS.

The rectification of a three phase supply can be effected by using a formation of six rectifiers in a bridge circuit.

This is shown in Figure 4.6. The output of a Three Phase Rectifier is essentially a steady output.

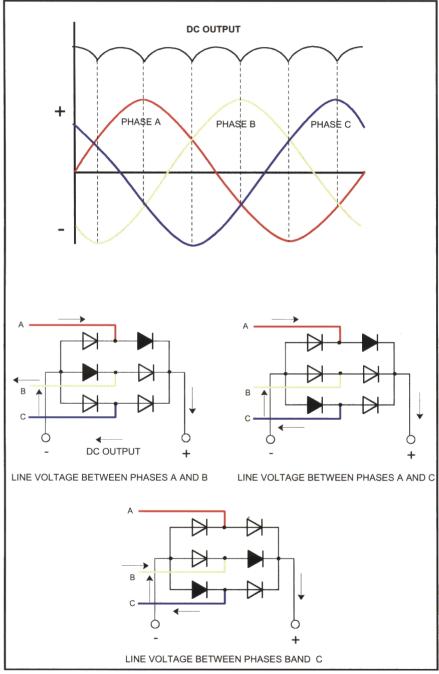


Figure 4.6 Three Phase Full Wave Rectifier

4.10 TRANSFORMER RECTIFIER UNITS (TRU's)

TRU's convert AC at one voltage to DC at another voltage by combining the tranformer and rectifier in one unit (usually 115/200vAC to 28vDC) to supply the DC needs of an AC distribution system.

TRU's are invariably multi phase units to achieve a smooth DC output. Indications of TRU output (amps) can be shown on the main electrical panel on the flight deck.

Cooling is achieved by drawing air through the unit which may be monitored for temperature with an overheat warning supplied.

4.11 INVERTERS

An inverter converts DC to AC.

The inverter in an constant frequency AC equipped aircraft is used as a source of emergency supply if the AC generators fail, then the inverter is powered by the battery.

Inverters are invariably "solid state" static inverters, (transistorised), in modern aircraft providing constant frequency AC for operation of flight instruments and other essential AC consumers. Rotary and Static inverters are described in the DC section.

Aircraft which have a frequency wild distribution systems (British Aerospace ATP, ATR 42) use inverters to supply their normal constant frequency requirements.

Inverter output can be monitored for voltage and frequency in the same manner as the main generators.

Cooling is accomplished in the same manner as the TRU.

CHAPTER FIVE - AC MOTORS

Contents

		Page
5.1	ALTERNATING CURRENT MOTORS	2.5 - 1
5.2	THE PRINCIPLE OF OPERATION OF AC MOTORS	2.5 - 1
5.3	THE SYNCHRONOUS MOTOR	2.5 - 1
5.4	THE INDUCTION MOTOR	2.5 - 3
5.5	THE SQUIRREL CAGE ROTOR	2.5 - 4
5.6	THE INDUCTION MOTOR STATOR	2.5 - 4
5.7	SLIP SPEED	2.5 - 4
5.8	STARTING SINGLE PHASE INDUCTION MOTORS	2.5 - 4
5.9	FAULT OPERATION	2.5 - 5
AC EL	ECTRICS SELF ASSESSMENT QUESTIONS PAPER 1-13	2.5 - 7

5.1 ALTERNATING CURRENT MOTORS

Alternating current motors can, in most cases, duplicate the operation of DC motors and are less troublesome to operate. DC motors have a great deal of trouble with their commutation, high altitude flight causing particular difficulty because of the associated arcing that occurs.

The brush equipment is another weak link, the heat generated at the brushes causing them to stick in the holders and as a consequence the resistance between them and the commutator increases, often to the point of becoming an open circuit, when of course the motor stops.

Synchronous AC motors do in fact use brush gear, their rotors are fed by relatively low current DC through sliprings, but these in general are less troublesome.

Alternating current motors are particularly suited for constant speed applications since their speed is determined by the frequency of the applied power supply.

Alternating current motors can be operated from either single or multi-phase power supplies.

5.2 THE PRINCIPLE OF OPERATION OF AC MOTORS.

Whether the AC motor is single or multi-phase, the principle of operation is the same, alternating current applied to the motor stator generates a rotating magnetic field which causes the rotor to turn.

The majority of motors used in aircraft can be divided into two types :-

- a) **Synchronous Motors**. These are basically alternators operated as motors. Alternating current is applied to the stator but the rotor has a Direct Current power source.
- b) Induction Motors. This type has alternating current applied to the stator but the rotor has no power source.

5.3 THE SYNCHRONOUS MOTOR.

The synchronous motor gets its name because the rotation of the rotor is synchronised with the rotating field set up in the stator. Its construction is basically the same as the rotating field alternator.

As illustrated in Figure 5.1, the application of a three phase supply to the stator causes a rotating magnetic field to be set up around the rotor. If a bar magnet was suspended in the field it would rotate synchronously with it (at the same speed as the rotating field).

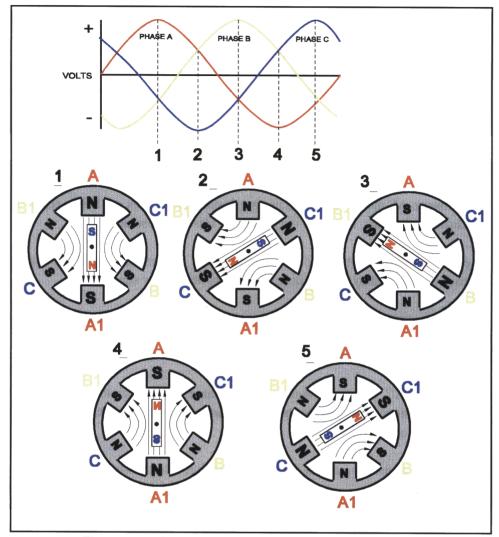


Figure 5.1 Generation of A Rotating Magnetic Field

In the same way, the rotor of a synchronous motor, which is energised with DC, acts like a magnet. It lines up with the field created by the stator and if the field turns, the rotor turns with it.

Synchronous motors are in fact single speed motors, the speed of rotation depending upon the frequency of the supply. Since in most cases the supply frequency is constant, then so is the motor speed. A synchronous motor will rotate at the same speed as the alternator that is supplying it providing it has the same number of poles. ie. if a synchronous motor with 4 poles is supplied with a constant frequency 400 Hz supply it will rotate at a constant 12,000 Rpm.

One disadvantage of the synchronous motor is that it is not self starting. To obtain the initial rotation some induction windings have to be added to the rotor to assist in bringing it up to synchronous speed.

Synchronous motors are used on aircraft to indicate engine rpm. A small three phase alternator (tacho-generator) is driven by the engine so that the frequency of the supply will be directly proportional to engine speed. The electrical output is connected to a synchronous motor in the rpm indicator. The indicator needle is coupled to the synchronous motor via a permanent magnet and a 'drag cup'. As the synchronous motor rotates it 'drags' the drag cup around with it, the faster the motor goes the further the drag cup moves and the further around the scale the needle moves. So the movement of the needle will be in proportion to engine rpm.

5.4 THE INDUCTION MOTOR

The induction motor gets its name from the fact that an alternating current is induced in the rotor by the rotating magnetic field in the stator.

It is the most commonly used because of its simplicity, its robustness and because it is relatively cheap to produce.

This relative cheapness is mainly because of the fact that the rotor is a self contained unit and not connected to the supply.

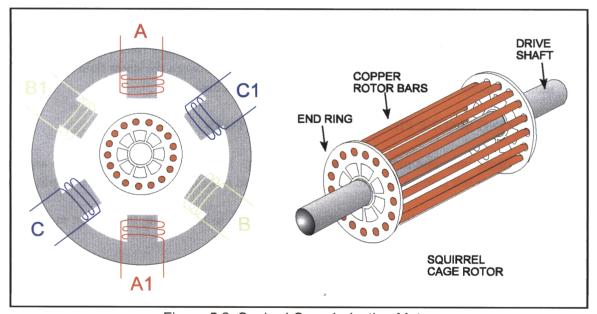


Figure 5.2 Squirrel Cage Induction Motor

5.5 THE SQUIRREL CAGE ROTOR

The rotor consists of a cylindrical laminated iron core which has a number of longitudinal bars of copper or aluminium evenly spaced around the circumference. These bars are joined at either end by rings of the same material to form a composite structure called a Squirrel Cage. The rotor bars are of very low resistance material so that a large current can flow through them.

5.6 THE INDUCTION MOTOR STATOR

The stator consists of windings, the number of which is related to the number of poles and also to the number of phases of the power supply. The rotating magnetic field produce in the stator cuts through the bars of the rotor which is basically a closed circuit of low resistance.

The resultant induced voltage creates a relatively large current flow in the squirrel cage. This current flow sets up its own magnetic field which interacts with the rotating field of the stator to produce a torque. If a three phase motor has two phases of its supply reversed, then its direction of rotation will be reversed also.

5.7 SLIP SPEED

The speed of the motor is determined by the frequency of the supply and the load on the motor. The rotor never quite reaches true synchronous speed, if it did then the squirrel cage bars would not be cut by any lines of force and thus would not produce the induced voltage. The difference between synchronous speed and rotor speed is called the slip speed or rotor slip. A typical value of slip would be 5%. Because of the difference in speed between the stator field and rotor the induction motor is sometimes referred to as being **asynchronous**.

5.8 STARTING SINGLE PHASE INDUCTION MOTORS

Single phase induction motors are not self starting. Different methods are used to assist in making them self starting. The most common method is the use of what is called a Split Phase Winding.

If the current in the split phase winding can be made to lead or lag the current in the main winding by 90° then a rotating field can be produced.

The lead or lag can be produced by the following methods;-

- a) Resistance starting.
- b) Inductance starting.
- c) Resistance / inductance starting.
- d) Capacitance starting.

The application of each method depends on the power output of the motor, e.g. capacitance started motors are usually of less than 2 H.P. output.

5.9 FAULT OPERATION

Occasionally the failure of one phase of the supply to a three phase induction motor does happen. If the motor is lightly loaded then it will probably continue to run at about half of its normal speed. This will create a humming noise in the motor which, because of the usually remote locations in which the motors are mounted, will probably not make itself apparent. The fault usually becomes apparent the next time an attempt is made to run the motor, it will not start.

1.	The i	mpedance of a circuit :-
	a)	is the AC inductive load.
	b)	is the DC inductive load.
	c)	is the total resistance in an AC circuit.
	d)	is the highest resistance of a rectifier.
2.	The r	ratio of true power to apparent power is known as:-
	a)	Ohms.
	b)	the power factor.
	c)	kVAs.
	d)	the r.m.s. value.
3.	In a c	constant frequency AC supply system, the frequency is determined by :-
	a)	the generator drive speed and the number of poles.
	b)	engine drive speed and the power factor.
	c)	the capacitive reactance.
	d)	the impedance.
4.	The a	amount of electrical power output for a given generator weight is :-
	a)	dependent on the aircrafts power requirements.
	b)	greater for a DC generator.
	c)	greater for an AC generator.
	d)	determined by the size of the aircraft.
5.	The f	requency of a supply is quoted in :-
	a)	cycles or Hertz.
	b)	watts.
	c)	megacycles.
	d)	cycles / minute.

- 6. Instrument transformers normally:
 - a) convert 14 volts DC to 26 volts AC
 - b) reduce the A.C supply to 26 volts for some instruments.
 - c) change 115 volts to 200 volts for engine instruments.
 - d) convert 28 volts DC to 28 volts AC

- 7. One advantage that AC has over DC is :
 - a) that T.R.U.s are not required.
 - b) that the generators require less cooling.
 - c) that the cables require less insulation.
 - d) the ease with which the voltage can be stepped up or down with almost 100% efficiency.
- 8. The voltage output of an AC generator will rise to a maximum value :
 - a) in one direction, fall to zero and rise in the same direction.
 - b) in one direction and remain there.
 - c) in one direction, fall to zero and rise to a maximum value in the opposite direction.
 - d) in one direction only.
- 9. If the frequency in a circuit is less than it was designed for, then current consumption will:
 - a) decrease.
 - b) remain the same.
 - c) fluctuate.
 - d) increase.
- 10. In a capacitive circuit, if the frequency increases:
 - a) current decreases.
 - b) current increases.
 - c) current flow is unaffected by frequency change.
 - d) the voltage fluctuates.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

- 1. An auto-transformer:
 - a) varies its turns ratio automatically to maintain a constant output voltage with varying input voltage.
 - b) has only one coil which is used as both primary and secondary.
 - c) will maintain a constant output frequency with a varying supply frequency.
 - d) requires an inductive supply.
- 2. The line voltage of a typical aircraft constant frequency paralleled AC system is:
 - a) 115
 - b) 208
 - c) 200
 - d) 400
- 3. A 400 Hz supply has :
 - a) an output capacity of 400,000 watts.
 - b) an impedance of 400 ohms.
 - c) a frequency of 400 cycles per second.
 - d) a frequency of 400 cycles per minute.
- 4. In an AC circuit which is mainly inductive :
 - a) current will lead voltage.
 - b) current and voltage will be in phase.
 - c) current will lag voltage.
 - d) the power factor will be negative.
- 5. If the frequency is increased in an inductive circuit:
 - a) impedance will increase.
 - b) impedance will decrease.
 - c) impedance will remain constant.
 - d) the heating effect will increase.

- 6. The r.m.s. value of alternating current is :
 - a) the mean current value for one half cycle.
 - b) 1.73 times the peak value.
 - c) equal to the square root of the peak value.
 - d) .707 times the peak value.

7. An alternator is :-

- a) a reversing input switch.
- b) an AC generator.
- c) a DC generator.
- d) a static inverter.

8. A diode:-

- a) has a high resistance in one direction and a low resistance in the other.
- b) has a high inductance in one direction and a low resistance in the other.
- c) has a low resistance in both directions.
- d) has a high resistance in both directions.
- 9. The number of separate stator windings in an AC generator determines:
 - a) the output voltage of the supply.
 - b) the output frequency of the supply.
 - c) the power factor.
 - d) the number of phases present in the supply.
- 10. AC generators usually have a rotating field and a fixed armature to :
 - a) reduce the overall diameter of the of the generator.
 - b) allow the output to be taken from the stator.
 - c) reduce the weight of the generator.
 - d) prevent arcing at the commutator.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

- 1. kVAR is a measure of :
 - a) the resistive load on the alternator.
 - b) the reactive load on the alternator.
 - c) the total load on the alternator.
 - d) the total circuit impedance.
- 2. In a Star wound three phase system:
 - a) line voltage equals phase voltage and line current equals .707 times phase current.
 - b) line current and voltage are 1.73 times phase current and voltage.
 - c) line current equals phase current and line voltage equals .707 times phase voltage.
 - d) line current equals phase current and line voltage equals 1.73 times phase voltage.
- 3. Instruments measuring AC are calibrated in :
 - a) r.m.s. values.
 - b) average values.
 - c) peak values.
 - d) mean values.
- 4. The output of an AC generator is taken from :
 - a) the exciter windings.
 - b) the field coils.
 - c) the stator windings.
 - d) the rotor coils.
- 5. Impedance is the :
 - a) vector sum of the resistance and the reactance.
 - b) sum of the resistance and capacitive reactance.
 - c) sum of the capacitive reactance and the inductive reactance.
 - d) sum of the resistance, inductive reactance and the capacitive reactance.
- 6. If an alternator is run at below normal frequency, then:
 - a) electric motors will stop.
 - b) inductive devices will overheat.
 - c) lights will become dim.
 - d) lights will become brighter.

- 7. The moving part of an alternator is:
 - a) the rotor.
 - b) the megacycle.
 - c) the stator.
 - d) the frequency.
- 8. The power factor is:
 - a) <u>kVA</u> kW
 - b) <u>kW</u> kVAR
 - c) <u>kW</u> kVA
 - d) <u>kVAR</u> kW
- 9. When reactance is present in a circuit:
 - a) the power factor will be unity.
 - b) the power factor will be negative.
 - c) the power factor will be greater than unity.
 - d) the power factor will be less than one.
- 10. Generator output frequency is decreased by decreasing the :
 - a) generator field rotation speed.
 - b) generator field voltage.
 - c) generator field current.
 - d) generator field impedance.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

- 1. A step-up transformer is one in which the number of turns on the secondary winding is:
 - a) the same as the primary if the cable diameter is the same.
 - b) greater than that on the primary.
 - c) less than on the primary.
 - d) always the same as on the primary.
- 2. The r.m.s. value of AC is:
 - a) 1.73 times the peak value.
 - b) the peak value times the power factor.
 - c) the peak value which would provide the same heating effect as DC
 - d) the value of DC which would provide the same heating effect.
- 3. In a reactive circuit:
 - a) the voltage and current will be out of phase.
 - b) the voltage and current will be in phase opposition.
 - c) the voltage will always be led by the current.
 - d) the voltage and current will be in phase.
- 4. A transformer which halves the voltage will have :
 - a) twice as many turns on the secondary as on the primary.
 - b) half as many turns on the secondary as on the primary.
 - c) half as much current flowing in the secondary as in the primary.
 - d) four times as many turns on the secondary as on the primary.
- 5. The power output of a transformer is:
 - a) in proportion to the transformation ratio.
 - b) in inverse proportion to the transformation ratio.
 - c) the same as the power input.
 - d) increased in a step up transformer.
- 6. A capacitor consists of two metal plates:
 - a) separated by a diabetic.
 - b) which have current flowing between them.
 - c) which will not allow a potential difference between them.
 - d) separated by waxed paper or mica.

- 7. In a DC circuit, an inductance:
 - a) never has any effect on the voltage.
 - b) only affects the voltage upon switching on.
 - c) offers opposition to the flow while switching on and off.
 - d) will always increase the voltage.
- 8. The basic unit of inductance is:
 - a) the Henry.
 - b) the Ohm.
 - c) the Farad.
 - d) the Coulomb.
- 9. With no load across the output terminals of a transformer:
 - a) the current flow will be maximum.
 - b) the current flow will be negligible.
 - c) the current will be in phase with the voltage.
 - d) the voltage in the primary will be always greater than the secondary.
- 10. A Bridge Rectifier:
 - a) will allow full wave rectification.
 - b) will give half wave rectification.
 - c) has a high resistance in both directions.
 - d) has an output with every other half wave chopped off.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

1.	A fre	equency wild alternator must be :-
	a)	paralleled.
	b)	a rotating magnet type.
	c)	self exciting.
	d)	unparalleled.
2.	In a 3	3 phase AC generator circuit, the phase voltage is :-
	a)	greater than line voltage.
	b)	10% higher than line voltage.
	c)	less than line voltage.
	d)	equal to line voltage.
3.		e voltage induced in the secondary windings is greater than that in the primary then the former is:-
	a)	an autotransformer.
	b)	a step up.
	c)	a step down.
	d)	a magnetic amplifier.
4.	If an	alternator output is frequency wild, it would normally be used for :-
	a)	flight instruments.
	b)	charging a battery.
	c)	all AC equipment.
	d)	prop and engine de-icing systems.
5.	The	generator output voltage is increased by :-
	a)	putting more load on it.
	b)	the frequency controller.
	c)	decreasing the generator field voltage.
	d)	increasing the generator field current.

- 6. A constant frequency AC supply in an aircraft with only frequency wild generators is provided by:
 - a) an inverter.
 - b) a diode.
 - c) an auto-transformer.
 - d) a rectifier.
- 7. An alternator normally used to supply an aircrafts power system would be :
 - a) single phase.
 - b) three phase.
 - c) two phase.
 - d) frequency wild.
- 8. A permanent magnet in a rotating field generator:
 - a) provides for initial excitation of the field.
 - b) controls the amount of excitation in the stator windings.
 - c) provides the initial excitation in the voltage regulator.
 - d) can be flashed by the application of alternating current.
- 9 Voltage control of an alternator output is achieved by varying the :
 - a) excitation of the rotating commutator.
 - b) load current.
 - c) excitation of the rotating field.
 - d) power factor.
- 10. Frequency wild AC is produced when:
 - a) a transformer winding open circuits.
 - b) the voltage regulator is malfunctioning.
 - c) the rotational speed of the generator varies.
 - d) the alternator becomes angry.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

AC ELECTRICS 6

- 1. In a star connected supply system:
 - a) line and phase current are equal.
 - b) line current is greater than phase current.
 - c) line current is less than phase current.
 - d) phase current is 0.707 times line current.
- 2. In a 3 phase supply system, line voltage would be sensed between the :
 - a) phases only.
 - b) phase and earth.
 - c) phase and neutral.
 - d) phases and earth.
- 3. In an inductive circuit:
 - a) current leads the voltage.
 - b) current lags the voltage.
 - c) the voltage is in phase with the current.
 - d) only the r.m.s. values vary.
- 4. In a capacitive circuit, if the frequency increases then:
 - a) current flow is unaffected.
 - b) the voltage varies.
 - c) current flow decreases.
 - d) current flow increases.
- 5. The power factor is:
 - a) <u>WATTFUL POWER</u>

REAL POWER

- b) <u>RATED POWER</u> APPARENT POWER
- c) <u>APPARENT POWER</u> TRUE POWER
- d) <u>REAL POWER</u> APPARENT POWER

- 6. One advantage of three phase generation over single phase generation is that:
 - a) most aircraft services require a three phase supply.
 - b) it can be more easily transformed into DC
 - c) it gives more compact generators and allows lower cable weights.
 - d) the power factor is much lower.
- 7. In a typical aircraft constant frequency supply system, the phase voltage is:
 - a) 200.
 - b) 115.
 - c) 208.
 - d) 400.
- 8. An alternator with its output taken from its stationary armature, has:
 - a) a stationary field.
 - b) its field excitation fed directly to the armature.
 - c) AC excitation.
 - d) a rotating field.
- 9. The phase voltage in a star wound three phase system is measured between :
 - a) phase and neutral.
 - b) two phases.
 - c) two lines.
 - d) neutral and earth.
- 10. If one phase of a star wound three phase system becomes earthed, it will:
 - a) earth all three phases.
 - b) cause a large current to flow in the neutral.
 - c) have no effect on the other phases.
 - d) cause a reduction in the frequency of the supply.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

- 1. The output of the bridge rectifier mounted between the main generator and the excitation generator in a brushless self excited alternator is:
 - a) DC for the excitation of the exciter field.
 - b) AC for the excitation of the main field.
 - c) AC for the excitation of the exciter field.
 - d) DC for the excitation of the main field.
- 2. The alternators fitted in an aircrafts main power supply system would normally be:
 - a) brushed self excited machines.
 - b) frequency wild.
 - c) self excited.
 - d) externally excited.
- 3. Transferring electrical energy by means of a magnetic field is called:
 - a) electrostatic induction.
 - b) electromolecular induction.
 - c) electromagnetic induction.
 - d) electromolecular amplification.
- 4. A voltage regulator works by :
 - a) sensing the battery voltage.
 - b) assessing the impedance of the circuit.
 - c) varying the circuit voltage.
 - d) varying the rotating field strength.
- 5. To ensure correct load sharing on paralleled alternators:
 - a) both real and reactive loads should be balanced.
 - b) actual loads should be the same.
 - c) reactive loads should be the same.
 - d) the load impedance should be constant.

- 6. Reactive load sharing is achieved by :
 - a) altering the loads on the bus bars.
 - b) varying the generator rotational speed.
 - c) varying the generator field current.
 - d) altering the C.S.D.U. output torque.
- 7. Real load sharing is achieved by :
 - a) varying the alternator rotational speed.
 - b) varying the generator field current.
 - c) altering the loads on the bus bar.
 - d) the voltage regulator.
- 8. The phase relationship of paralleled generators should be ;
 - a) unimportant.
 - b) 180° apart.
 - c) synchronous.
 - d) 120° apart.
- 9. In a constant speed parallel operation alternator system :
 - a) each alternator has its own constant speed drive unit.
 - b) all engines are run at the same speed.
 - c) all alternators are driven by the same engine.
 - d) engine speed is governed by the constant speed drive unit.
- 10. An aircrafts constant frequency supply is maintained at :
 - a) between 350 450 Hz.
 - b) between 380 420 Hz.
 - c) between 115 200 Hz.
 - d) between 395 495 Hz.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

- 1. For a modern aircraft powered by an AC system, the ground power unit must supply:
 - a) 28 volts AC only.
 - b) 200 volts.
 - c) 115 volts, three phase.
 - d) 200 volts, three phase, 400 Hz.
- 2. Oil for the operation of a C.S.D.U. is :
 - a) supplied from the engine oil system.
 - b) a separate self contained supply.
 - c) drawn from a common tank for all C.S.D.U.s.
 - d) only required for lubrication purposes.
- 3. Malfunction of a C.S.D.U. requires :
 - a) automatic electrical disconnection of the drive at any time in flight.
 - b) that the input drive will shear on the ground only.
 - c) operation of the drive disconnect switch at any time in flight.
 - d) operation of the drive disconnect switch on the ground only.
- 4. Before two constant frequency AC generators can be connected in parallel:
 - a) their frequency, phase, phase sequence and voltage must match, and a means of automatic real and reactive load sharing must be available.
 - b) real and reactive loads must match. Frequency, phase and voltage must be within limits.
 - c) the synchronisation lights on the alternator control panel must be fully bright.
 - d) suitable control arrangements must exist for the sharing of real and reactive loads, these will correct any phase or frequency error existing at the time of connection.
- 5. The generator control relay (G.C.R) is :
 - a) in the excitation circuit.
 - b) between the alternator and its load bus bar.
 - c) in the stator circuit.
 - d) between the load bus bar and the synchronous bus bar.

- 6. The running excitation current for an alternator is:
 - a) AC
 - b) DC from the aircraft batteries.
 - c) DC from the static inverter.
 - d) DC which is rectified AC and could be from a separate excitation generator on the main rotor shaft.
- 7. If each phase of a three phase star wound system has a phase voltage of 115 volts, the voltage obtained by bridging two phase would be:
 - a) 200 volts AC
 - b) 173 volts DC
 - c) 28 volts DC
 - d) 173 volts AC
- 8. Protection from 'earth' faults and 'line to line' faults is given by :
 - a) a negative earth detector.
 - b) a fault protection system including a differential protection monitor.
 - c) the synchronisation unit.
 - d) reactive load sharing circuits.
- 9. Warnings of C.S.D.U. oil overheat are given in the cockpit by:
 - a) audio warning.
 - b) an 'oil overheat' warning light.
 - c) a 'low oil pressure' warning light.
 - d) a temperature gauge.
- 10. One disadvantage of parallel operation is that :
 - a) faults can propagate, and any error in supply can affect all services.
 - b) the system is less flexible due to the need for additional control and protection circuits.
 - c) the greater load on the C.S.D.U.s means that their power / weight ratio is much reduced.
 - d) there is a considerable increase in complexity compared with a non-paralleled system, due to the need for C.S.D.U.s and load sharing circuits.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

- 1. Alternators in parallel operation require the maintenance of constant frequency and phase synchronisation to:
 - a) balance the battery voltage when more than one battery is being used.
 - b) prevent recirculating currents.
 - c) control their voltage.
 - d) reduce their magnetic fields.
- 2. The A.P.U. generator can only be used when:
 - a) another generator is on line.
 - b) the aircraft is on the ground.
 - c) the bus bars are being fed from another source.
 - d) when no other power source is feeding the bus bar.
- 3. The purpose of the differential protection circuit in a three phase AC system is:
 - a) to compare alternator output current to bus bar current.
 - b) to compare on and off load currents.
 - c) to compare the alternators reactive load to its real load.
 - d) to compare the C.S.D.U. efficiency ratings.
- 4. An alternator driven by a C.S.D.U:
 - a) can never be paralleled.
 - b) will require a voltage controller.
 - c) will require a lubrication system separated from its drive oil system.
 - d) will not require a voltage controller.
- 5. The purpose of a synchronising bus bar is to :
 - a) enable interconnections to be made between generator bus bars.
 - b) supply essential services.
 - c) monitor on-load currents.
 - d) interconnect DC bus bars.

- 6. In the event of a mechanical malfunction of the alternator:
 - a) the drive disconnect unit will automatically separate the C.S.D.U. from the alternator.
 - b) the real load will be adjusted to compensate.
 - c) the quill drive will fracture.
 - d) the C.S.D.U. oil temperature will decrease.
- 7. The load meter, upon selection to "kVAR" would indicate:
 - a) total power available.
 - b) reactive loads.
 - c) active loads.
 - d) only DC resistive loads.
- 8. Disconnection of the C.S.D.U. in flight would be advisable if:
 - a) the frequency meter indicated a discrepancy of greater than 5 Hz between alternators.
 - b) there was an over or under voltage.
 - c) the oil temperature was high or the oil pressure was low.
 - d) the engine failed.
- 9. To increase the real load taken by a paralleled AC generator, the :
 - a) generator drive torque is increased.
 - b) generator excitation is increased.
 - c) generator drive torque and field excitation are increased.
 - d) generator voltage regulator adjusts the generator rotor torque.
- 10. Load sharing circuits are necessary whenever:
 - a) generators are operating in series.
 - b) generators are operating independently.
 - c) the ground power and the A.P.U. are serving the bus bars together.
 - d) generators are operating in parallel.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

- 1. Paralleled alternators will have :
 - a) one load meter which measures total system load.
 - b) one voltmeter for each alternator.
 - c) one load meter for each alternator.
 - d) one meter which indicates both voltage and frequency.
- 2. Frequency controlled generators are:
 - a) always paralleled.
 - b) not always paralleled.
 - c) never paralleled.
 - d) paralleled only when the DC is paralleled.
- 3. If the C.S.D.U. drive disconnect unit had been used, the drive can:
 - a) only be reconnected when the aircraft is on the ground.
 - b) be reinstated in flight from the electrical supply department.
 - c) be reinstated in flight from the flight deck.
 - d) be reinstated when necessary by using the Ram Air Turbine.
- 4. When selected to 'kW', the alternator load meter will indicate the:
 - a) total circuit load.
 - b) real load.
 - c) reactive load.
 - d) current flowing in the field.
- 5. An AC generator's I.D.U. oil system:
 - a) is self contained.
 - b) is common with the engine oil system.
 - c) is used only for cooling.
 - d) is used only for lubrication.

- 6. An alternator driven by a non-integrated constant speed drive unit, has windings that are cooled by:
 - a) water.
 - b) oil.
 - c) oil and water.
 - d) air and/or oil.
- 7 The load in a paralleled AC system is measured in :
 - a) kW & kVA.
 - b) kW & kV.
 - c) kV & kVAR.
 - d) kW & kVAR.
- 8. Paralleled generators must share real and reactive loads:
 - a) to prevent large current flows through the T.R.U.s.
 - b) to prevent out of balance forces being fed through the C.S.D.U.s to the engines.
 - c) to prevent large flows of current from one generator to another.
 - d) to prevent harmonic frequencies being created in the synchronous bus bars.
- 9. One advantage of running alternators in parallel is that :
 - a) the supply to all circuits is in phase.
 - b) a large capacity is available to absorb heavy transient loads when switching of heavy currents occurs.
 - c) the risk of overloading the system is reduced.
 - d) there is only a requirement for one C.S.D.U.
- 10. When an external AC supply is feeding the bus bars:
 - a) the internal bus bars are disconnected.
 - b) the aircraft generators are run in parallel with the external supply.
 - c) the aircraft generators are taken off line.
 - d) the synchronising unit will ensure that no frequency difference exists between the aircraft generators and the external supply.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

AC ELECTRICS 11

1	. Th	e outp	out of	an	alterna	tor is	rated	ın	:-
---	------	--------	--------	----	---------	--------	-------	----	----

- a) kVA.
- b) kVAR.
- c) kW.
- d) kw/kVAR.

2. A three phase AC system can be used to supply:-

- a) both one or three phase equipment.
- b) only three phase equipment.
- c) only single phase equipment.
- d) only inductive or capacitive loads.

3. In a frequency wild generation system:-

- a) generators can be run in parallel only when all engine r.p.m.s match.
- b) generators can never be run in parallel and there can be no duplication of supply.
- c) generators can never be run in parallel, but after rectification, the D,C, can be fed to a common bus bar to provide a redundancy of supply.
- d) capacitive and inductive loads can be fed with no problems of overheating.
- 4. A fault on one phase of a three phase AC star connected system would :
 - a) have no effect.
 - b) effect only the phase concerned.
 - c) cause inductive loads to overheat.
 - d) affect all three phases.

5. Fuses and circuit breakers are fitted:-

- a) in DC circuits only.
- b) in both AC and DC circuits.
- c) in AC circuits only.
- d) only to protect the wiring.

- 6. The purpose of an inverter is:
 - a) to change AC into DC
 - b) to change the frequency of the AC supply.
 - c) to act as a back up for the alternator.
 - d) to change DC into AC
- 7. A low reactive load on one generator is compensated for by:
 - a) altering the excitation current flowing in its field circuit.
 - b) increasing the rotor speed.
 - c) increasing the real load on the other generators.
 - d) overall load reduction.
- 8. In the event of a mechanical failure occurring in the generator, the C.S.D.U. is protected by:
 - a) a hydraulic clutch.
 - b) a universal joint.
 - c) a quill drive.
 - d) a feather drive.
- 9. To increase the real load which is being taken by a paralleled alternator:
 - a) the voltage regulator adjusts the generator rotor torque.
 - b) both its drive torque and its excitation are increased.
 - c) only its excitation is increased.
 - d) its drive torque is increased.
- 10. Where the aircraft's main electrical supply is A.C, DC requirements are met by:
 - a) batteries.
 - b) T.R.U.s.
 - c) inverters.
 - d) a static inverter.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

- 1. In a split bus system using non-paralleled constant frequency alternators as the primary power source:
 - a) essential AC loads are supplied directly from No 1 AC bus bar.
 - b) essential AC loads are supplied directly from N° 2 AC bus bar.
 - c) only non-essential AC loads are supplied from the AC bus bars.
 - d) essential AC loads are normally supplied from N° 1 AC bus bar via the changeover relay.
- 2. In a split bus system using non-paralleled constantfrequency alternators as the primary power source, if both alternators fail:
 - a) all non-essential services are lost.
 - b) all non- essential services will be supplied direct from the battery bus bar.
 - c) all non-essential services will be supplied from the static inverter.
 - d) essential DC consumers only will be supplied from the N°1 T.R.U., all other DC services will be lost.
- 3. In normal operation, the split bus bar AC system takes its DC supply from :
 - a) two T.R.U.s which are always isolated.
 - b) a battery which is supplied from N° 1 T.R.U. only.
 - c) two T.R.U.s which are connected together by the isolation relay.
 - d) the static inverter.
- 4. The static inverter in the split bus system supplies :
 - a) the essential DC consumers.
 - b) the essential AC consumers.
 - c) both essential and non-essential consumers.
 - d) the batteries.
- 5. In the split bus system, the AC bus bars :
 - a) are automatically connected via the isolation relay if one alternator fails.
 - b) are automatically connected via the bus tie breaker if one alternator fails.
 - c) can be connected together by switch selection if one alternator fails.
 - d) can never be connected together because there is no load sharing circuit.

- 6. With parallel generator operation:
 - a) there are two synchronising bus bars which are normally kept isolated.
 - b) the G.C.B.s connect the generators to the synchronising bus bar.
 - c) the B.T.B.s connect the synchronising bus bars together.
 - d) the G.C.R.s connect the generators to their load bus bars.
- 7. In a parallel alternator operation, should one alternator fail, then:
 - a) the other alternators can be selected to supply its load.
 - b) the failed alternators loads will not be supplied.
 - c) the G.C.B. of the failed alternator will remain closed to allow its loads to be supplied by the remaining alternators.
 - d) the S.S.B. will close allowing the three remaining alternators to share all of the load.
- 8. An earth fault on a bus bar of a parallel generator system:
 - a) would require that the appropriate G.C.B. should open.
 - b) would require that the appropriate B.T.B. should open.
 - c) would require that both the appropriate G.C.B. and B.T.B. should open.
 - d) would require that all alternators should operate independently.
- 9. To prevent high circulating currents between paralleled alternators, the following conditions should be met:
 - a) their voltage and frequency must be the same.
 - b) their frequencies must be identical and their phase sequence must be the same.
 - c) their voltage, frequency, phase and phase sequence must all be the same.
 - d) their inductive and capacitive reactances must match exactly.
- 10. If external power is plugged into an aircraft which utilises the split bus system of power distribution, then:
 - a) it will automatically parallel itself with any alternators already on line.
 - b) it will only supply non-essential AC consumers.
 - c) it will supply all the aircraft services.
 - d) essential AC consumers will be supplied from the static inverter.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

1.	Synchronous	motors are	usually	supplied	by:-
----	-------------	------------	---------	----------	------

- a) three phase AC
- b) single phase AC
- c) DC to the stator.
- d) DC to the stator and AC to the rotor.
- 2. Reversing two phases to a three phase motor will:
 - a) blow the phase fuses.
 - b) cause the motor to run in reverse.
 - c) overheat the stator windings.
 - d) stall the motor.
- 3. A synchronous motor runs at a speed that depends upon the supply:
 - a) voltage.
 - b) current.
 - c) reactance.
 - d) frequency.
- 4. If one phase of the supply to a three phase motor fails, then:
 - a) the motor will continue to run at the same speed.
 - b) will slow down and stop.
 - c) will stop immediately.
 - d) will run at about half speed but will not start on its next selection.
- 5. The basic principle of operation of a 3 phase induction motor is:
 - a) A rotating field created in the rotor.
 - b) A rotating field created in the stator.
 - c) A stationary field created in the stator.
 - d) A stationary field created in the rotor.

- 6. In an induction motor:
 - a) the rotor is star connected.
 - b) magnetic fields blend evenly with one another.
 - c) AC is induced in the rotor.
 - d) a DC supply produces DC in the rotor.
- 7. In a synchronous motor, the rotor is :
 - a) energised by DC and it lines up with the magnetic field in the stator.
 - b) wave wound.
 - c) both AC and DC energised.
 - d) impeded by the AC induced into it.
- 8. An induction motor has :
 - a) slip rings and brushes.
 - b) a commutator.
 - c) no slip ring or brushes.
 - d) slip rings but no brushes.
- 9. A squirrel cage rotor:
 - a) is not connected to the supply.
 - b) is expensive to produce.
 - c) rotates at exactly synchronous speed.
 - d) is a closed circuit of high resistance.
- 10. A starting circuit for a powerful single phase induction motor might be :
 - a) a capacitance starter.
 - b) a resistance / inductance starter.
 - c) a cartridge starter.
 - d) a bump starter.

QUE	1	2	3	4	5	6	7	8	9	0
ANS										
REF										

AC ELECTRICS WORKSHEET ANSWERS

AC#1

QUE	1	2	3	4	5	6	7	8	9	0
ANS	С	В	A	C	A	В	D	С	D	В
REF										

AC#2

QUE	1	2	3	4	5	6	7	8	9	0
ANS	В	C	C	C	A	D	В	A	D	В
REF										

AC#3

QUE	1	2	3	4	5	6	7	8	9	0
ANS	В	D	A	С	A	В	A	С	D	A
REF										

AC#4

QUE	1	2	3	4	5	6	7	8	9	0
ANS	В	D	A	В	С	D	С	A	В	A
REF										

AC#5

QUE	1	2	3	4	5	6	7	8	9	0
ANS	D	C	В	D	D	A	В	A	С	C
REF										

AC#6

QUE	1	2	3	4	5	6	7	8	9	0
ANS	A	A	В	D	D	C	В	D	A	В
REF										

AC#7

QUE	1	2	3	4	5	6	7	8	9	0
ANS	D	С	C	D	A	С	A	С	A	В
REF										

AC#8

QUE	1	2	3	4	5	6	7	8	9	0
ANS	D	В	С	A	A	D	A	В	D	D
REF										

AC#9

QUE	1	2	3	4	5	6	7	8	9	0
ANS	В	D	A	В	A	С	В	C	A	D
REF										

AC#10

QUE	1	2	3	4	5	6	7	8	9	0
ANS	C	В	A	В	A	D	D	C	В	C
REF										

AC#11

QUE	1	2	3	4	5	6	7	8	9	0
ANS	A	A	С	D	В	D	A	С	D	В
REF										

AC#12

QUE	1	2	3	4	5	6	7	8	9	0
ANS	D	A	C	В	В	A	D	C	C	С
REF										

AC#13

QUE	1	2	3	4	5	6	7	8	9	0
ANS	A	В	D	D	В	C	A	C	A	В
REF										

CHAPTER SIX - BASIC COMPUTERS

Contents

		Page
6.1	COMPUTERS	2.6 - 1
6.2	ANALOGUE COMPUTERS	2.6 - 1
6.3	DIGITAL COMPUTERS	2.6 - 1
6.4	BINARY NUMBER SYSTEM	2.6 - 2
6.5	CONVERTING DECIMAL NUMBERS TO BINARY NUMBERS: 2	2.6 - 3
6.6	OCTAL NOTATION SYSTEM:	2.6 - 6
6.7	HEXADECIMAL NUMBER SYSTEM:	2.6 - 7
6.8	DIGITAL COMPUTER COMPONENTS (HARDWARE):	2.6 - 7
6.9	CENTRAL PROCESSING UNIT (CPU):	2.6 - 8
6.10	INPUT OUTPUT DEVICES:	2.6 - 8
6.11	MEMORY:	2.6 - 9
6.12	AIRCRAFT SYSTEMS: 2.	6 - 10
SELF A	ASSESSMENT QUESTIONS	6 - 11
SELF A	ASSESSMENT QUESTION ANSWERS	6 - 16

6.1 COMPUTERS

A computer may be defined as: A device or set of devices that can store data and a program that operates on the data. A general purpose computer can be programmed to solve any reasonable problem expressed in logical and arithmetical terms.

The first fully operational general purpose computer, electromechanical and using binary digits was the Z3, built in Germany in 1941 by Konrad Zuse.

Basically there are two types of computer:

- a) Analogue
- b) Digital

By far the most common is the Digital Computer or Micro Processor which now plays a part in most aspects of everyday life.

6.2 ANALOGUE COMPUTERS

An analogue computer uses continuous physical variables such as voltage or pressure to represent and manipulate the measurements it handles.

Analogue computers are used as electronic models or **analogues** of mechanical or other systems in cases where conducting experiments on the system itself would be costly, time consuming or dangerous. For example when designing a bridge or aircraft wing or any structure where motion can occur, the engineer must know beforehand how it will react to various physical variables such as wind speed and temperature.

In recent years analogue computers have become less popular because it is now possible to program digital computers to simulate moving physical systems.

The remainder of this chapter will deal with digital computers and their use in aircraft.

6.3 DIGITAL COMPUTERS

Digital Computers use digital data (binary data) in their operations. This form of data has only two levels of voltage as opposed to the analogue systems continuous variables. The two levels correspond to **ON** or **OFF** ie switching circuits. Digital circuits are **two state** circuits. Normally when working on paper we count from zero to nine - the decimal number system. When the digital computer works it has to use the **ON** - **OFF**, two state or **BINARY** number system.

6.4 BINARY NUMBER SYSTEM

The binary number system represents different quantities using only two symbols, 1 and 0. If a quantity larger than 1 must be represented by binary numbers, the symbols systematically repeat. As in the decimal system, the binary system repeats by adding to the **left** of the first digit.

Therefore a binary number may be written: 101

How can the equivalent number be represented in the familiar decimal number system?

In the decimal system the least significant digit is on the right and the most significant digit on the left. The same applies in the binary system.

The 1 on the right represents 1 x 2 to the power 0 or 2^0 which is decimal 1.

The 0 in the middle tells us there is no value in the column 2¹ so the is no decimal 2.

The 1 on the left indicates there is 1 x 2 to the power 2 or 2² which is decimal 4

By adding the decimal one derived from the binary 1 on the left to the 4 derived from the binary 1 on the right we get decimal number 5.

Binary 101 = Decimal 5

The table below shows the specific value of a binary digit in positions of 1 to 10, with the least significant number on the right and the most significant number on the left.

BINARY DIGIT	10 th	9 th	8 th	7^{th}	6 th	5 th	4 th	3 rd	2 nd	1 st
POWER	29	28	27	2 ⁶	25	24	23	2^2	21	20
DECIMAL VALUE	512	256	128	64	32	16	8	4	2	1

Using the table it is easy to convert binary numbers in to their decimal equivalents, you simply place the binary number under the table, note the powers of two above the binary ones and add them together.

The table below shows another example in addition to the previous number conversion. Note that binary zeros are not counted.

ALTERNATING CURRENT

Convert binary 111011 to decimal:

Binary digit	6th	5th	4th	3rd	2nd	1 st	
Power	2 ⁵	24	2^3	2 ²	21	20	
Decimal value	32	16	8	4	2	1	
				1	0	1	4 + 1 =
	1	1	1	0	1	1	32 + 16

$$4 + 1 = 5$$

$$32 + 16 + 8 + 2 + 1 = 59$$

6.5 CONVERTING DECIMAL NUMBERS TO BINARY NUMBERS:

To change decimal numbers to binary numbers we simply progressively divide the decimal number by 2 and record the remainder, the remainder being the binary number:

Example 1: Convert decimal 96 to binary:

Quo	tient	Remainder
<u>96</u> 2	48	0 (last binary digit)
<u>48</u> 2	24	0
<u>24</u> 2	12	0
<u>12</u> 2	6	0
$\frac{6}{2}$	3	0
$\frac{3}{2}$	1	1
$\frac{1}{2}$	0	1 (first binary digit)

Decimal number 96 = binary number 1100000

Example 2: Convert decimal 18 to binary

Quoti	ient	Remainder
18/2	9	0
$\frac{9}{2}$	4	1
$\frac{4}{2}$	2	0
$\frac{2}{2}$	1	0
$\frac{1}{2}$	0	1

Decimal number = 18Binary number = 10010


Example 3: Convert decimal 69 to binary

Quot	ient	Remainder		
<u>69</u> 2	34	1		
$\frac{34}{2}$	17	0		
17 2	8	1		
$\frac{8}{2}$ $\frac{4}{2}$ $\frac{2}{2}$	4	0		
$\frac{4}{2}$	2	0		
$\frac{2}{2}$	1	0		
$\frac{1}{2}$	0	1		

Decimal number = 69 Binary number = 1000101

Positive Logic:

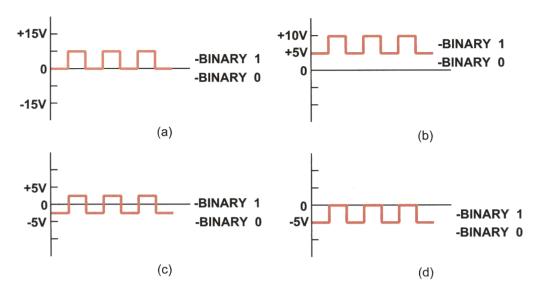Binary 1 is usually represented by a positive voltage +5v or +28v and binary 0 by zero volts (earth). This is known as positive logic.




Four examples of positive logic digital signals.

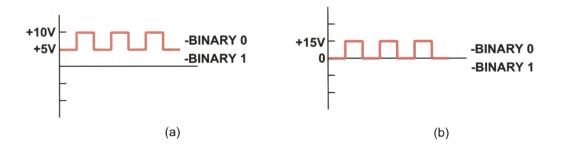- (a) Binary 1=+7.5 V, binary 0=0 V;
- (b) binary 1=+10 V, binary 0=+5 V;
- (c) binary 1=+2.5 V, binary 0=-2.5 V;(Bipolar binary) (d) binary 1=0 V, binary 0= -5 V.

Negative Logic:

When binary 1 is represented by a negative number and binary 0 by zero (earth). This is called negative logic and is less common.



Examples of negative logic digitals signals. (a) Binary 1=+5 V, binary 0=+10 V; (b) binary 1=0 V, binary 0 =+15 V.

As can be seen from the examples on the previous page, when counting in the binary system using just 0 and 1, many more columns are required. Successive columns from the right represent increasing powers of 2:

The term **BIT** may be used when referring to a **binary digit**. One bit is equal to one binary digit. A bit will always be a high or low logic level (+ voltage and 0 voltage for example).

Bits handled as a group are referred to as a **BYTE.** Therefore, an eight bit binary number is a byte containing eight bits.

A **WORD** is a grouping of bits that a computer uses as a standard information format. For example, many systems communicate using a 16 or 32 bit word. Each word for a particular system will conform to a specific format that enables the computer to understand it and decode it's message.

6.6 OCTAL NOTATION SYSTEM:

The octal number system is based on eight, 0 to 7. The octal notation system is the binary representation of an octal number. Octal notation is comprised of a series of three bit groups (TRIADS). Since the largest decimal number that can be represented by three bits is 7 (111), this is a base eight or octal system.

Octal notation is useful for certain programming techniques where large quantities of binary numbers must be manipulated. Octal is often used for the transmission of data by aircraft computers and their peripherals.

Triad group	4 th	3 rd	2 nd	1 st
3 - digit octal notation	001	010	100	001
Decimal equivalent of triad	1	2	4	1
Power of eight	8 ³	8 ²	8 ¹	80
Decimal value of base eight number	512	64	8	1
Decimal equivalent of octal groups	(1 x 512) 512	(2 x 64) 128	(4 x 8) 32	(1 x 1) 1

Sum the decimal equivalents of each octal group 512 + 128 + 32 + 1 = 673Octal notation $001\ 010\ 100\ 001 = decimal\ 673$

6.7 HEXADECIMAL NUMBER SYSTEM:

The hexadecimal (hex) system uses base 16. The main purpose of this system is to represent the very large numbers of **memory locations** used in micro controllers and microprocessors.

The hexadecimal system uses the **numbers 0 to 9** along with the **letters A to F** to make up the 16 symbols. The table below shows the relationship between hexadecimal, decimal and binary numbers:

Hexadecimal	Decimal	Binary
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
В	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

An important point to recognise about the hexadecimal system is that 4 binary digits represent a single hexadecimal digit. This is significant because a 16 bit binary code can be represented by a 4 digit hexadecimal number.

6.8 Digital Computer Components (Hardware):

Having discussed the language in which computers work, and remembering that **binary** is the basic language in which calculations are carried out and information is stored in memory, we shall now look at the construction of a basic computer.

All computers have the basic components shown in the diagram below:

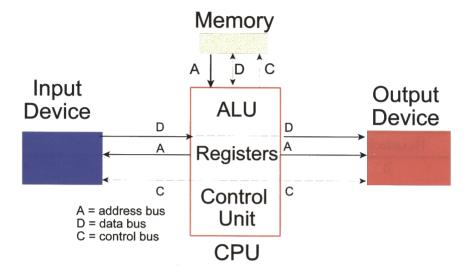


Figure 1 A Basic Digital Computer

6.9 Central Processing Unit (CPU):

The CPU performs, organises and controls all the operations the computer can carry out. It is really the **brain** of the computer. What the CPU can do is controlled by an **instruction set**. The current standard for high performance processors is Intel's Pentium II chip design. On two combined microprocessor **chips**, that are together less than a couple of square inches, the Pentium II holds 7.5 million transistors acting as tiny electronic switches.

The CPU itself consists of:

- **a. Arithmetic Logic Unit:** The ALU performs arithmetic calculations and logical operations in the binary number system.
- **b. Shift Registers:** The shift registers are temporary **stores**; one of them, called the **accumulator** contains the data actually being processed.
- **c. Control Unit**: The control unit contains the computer's **clock**. This is a crystal controlled oscillator which generates timing pulses at a fixed frequency, typically between 120 and 45MHz. This synchronises computer operations.

6.10 INPUT OUTPUT DEVICES:

The CPU accepts digital signals from the input devices, keyboard, mouse or modem, in the case of a PC, via its input port. In an aircraft these could be various sensors, Rad Alt, Baro Alt, TAS, fuel flow, etc.

After processing these are fed out via its output port to a Visual Display Unit (Monitor) or printer. In an aircraft the output may be fed to an EFIS Symbol Generator or the FMS Control Display Unit (CDU).

BIOS (Basic Input Output System) converts the input signals to a form the computer can work with and converts the outputs to a form the operator or another aircraft system can understand.

6.11 MEMORY:

a. Working Memory: A computer needs a working memory to run the programme of instructions (software) it has to execute. If the programme is fixed as in a computer controlled piece of equipment, the memory only has to be read. To do this a Read Only Memory (ROM) is used. This ROM is programmed by the manufacturer. A Programmable Read Only Memory (PROM), Erasable Programmable Read Only Memory (EPROM) would be used if the user wanted to construct or modify the programme himself and keep it permanently in the memory.

Memory that retains data when the power is switched off is called **NON VOLATILE MEMORY.** Memory that loses data in the event of a power failure or switch off is called **VOLATILE MEMORY**.

If the programme has to be changed during operation, then the memory must be able to be **written** to as well as **read**. To do this **Random Access Memory (RAM)** this allows instructions to be written in, read out and altered at will. A RAM is also required to store the data for processing as this also will change continually. **RAM is normally Volatile Memory**.

- b. Permanent Memory: As stated above RAM is volatile and work is lost when power is removed. Permanent storage for computer programmes and the work they generate is usually in the form of magnetic disks. Both floppy and hard disks are permanent stores of computer data. Their storage capacity is measured in megabytes or gigabytes. Hard disks are usually integral parts of the hardware. Floppy disks can be inserted and removed from drives and are transportable and securable.
- c. Electronically Alterable Read Only Memory (EAROM): This is a special type of ROM that can be electronically altered. It is used in the data base of the Flight Management System Computer. This contains a worldwide data base of all airfields, navigation aids, airways, etc. Of course, periodically, frequencies and airways change and the data base needs to be updated.

This is achieved on a 28 day cycle when Jeppeson issue an update floppy disk to their client airlines. The disk is inserted into the FMS Control Display Unit, powered up and the new data inserted and the old data cancelled.

- **6.12 AIRCRAFT SYSTEMS:** Systems which are computer controlled include:
 - a. Flight Management System (FMS)
 - b. Digital Flight Guidance System (DFGS)
 - c. Ground Proximity Warning System (GPWS)
 - d. Traffic Alert Collision Avoidance System (TCAS)

Of course Fly by Wire aircraft take computer control very much further, when the whole flight envelope is controlled by computer process with inputs from the crew when necessary.

Current design favours the use of dedicated computers for each separate system. In the future however we may see sharing of computer power in the form of an **Integrated Hazard Warning System (IHWS).** Here a powerful central processor, with appropriate back up, handles inputs from the stall warning system, windshear detection, GPWS, TCAS and even the Weather Radar, processes the information and prioritises warnings to the crew.

Analogue to Digital Conversion (A to D): Many aircraft sensors produce analogue information in the form of varying voltages, pressures, temperatures, etc. Of course digital computers use digital (binary) information and a device called an Analogue to Digital Converter is required in the interface between the sensor and the computer input device.

Digital to Analogue Conversion (D to A): When a digital computer has to pass information to an analogue device the process is reversed and a **Digital to Analogue Converter** is used.

SELF ASSESSMENT QUESTIONS

COMPUTERS

- 1. A basic digital computer consists of:
 - 1. input peripherals
 - 2. central processing unit
 - 3. inertial unit
 - 4. memory
 - 5. auto brightness control
 - 6. output peripherals
 - a. 1, 2, 3, 4 and 6
 - b. 1, 2, 4 and 6
 - c. 1, 4, 6 only
 - d. 2, 3, 4, and 6
- 2. The Central Processing Unit (CPU) consists of:
 - 1. input device
 - 2. output device
 - 3. Arithmetic Logic Unit (ALU)
 - 4. Shift Registers
 - 5. Control Unit
 - 6. Hard disk
 - a. 1, 2, 3, and five
 - b. 3, 4, and 6
 - c. 1, 2, 5, and 6
 - d. 3, 4, 5,
- 3. In computer terminology an input peripheral device would be:
 - a. a hard disk
 - b. a floppy disk
 - c. a keyboard
 - d. a screen display unit

4. The two types of binary logic a	are:
------------------------------------	------

- a. positive and negative
- b. variable and negative
- c. positive and reversible
- d. variable and reversible

5. In computer terminology an output peripheral device would be:

- a. a floppy disk
- b. a hard disk
- c. a screen display unit
- d. a keyboard
- 6. In computer terminology a memory which loses its data when power is removed is called:
 - a. non-volatile
 - b. non-permanent
 - c. non-retentive
 - d. volatile
- 7. In computer terminology a memory which retains its data when power is removed is called:
 - a. non-volatile
 - b. volatile
 - c. RAM
 - d. ROM

8. Examples of input peripheral devices are:

- 1. mouse
- 2. modem
- 3. printer
- 4. screen display unit
- 5. keyboard
- a. 2, 3, 4, 5.
- b. 1, 2, 5.
- c. 1, 5.
- d. 1, 2, 3.

- 9. In computer terminology "software" refers to:
 - a. the memory system floppy disks, hard disks, etc
 - b. the RAM and ROM capacity
 - c. the programme of instructions
 - d. the BIOS
- 10. In computer terminology "hardware" refers to:
 - a. the digital computer components, keyboard, monitor, CPU, etc
 - b. the permanent memory system and its capacity
 - c. the RAM capacity
 - d. the programme of instructions
- 11. Memory capacity in a digital computer is expressed in:
 - a. Bits (Mbits, Gbits)
 - b. Bytes (Mbytes, Gbytes)
 - c. ROM capacity
 - d. RAM capacity
- 12. The smallest information element in a digital system is:
 - a. byte
 - b. digit
 - c. electron
 - d. bit
- 13. A group of binary digits handled as a group is referred to as a:
 - a. byte
 - b. mega bit
 - c. giga bit
 - d. bits
- 14. Convert the decimal number 7 to its binary equivalent:
 - a. 1110
 - b. 111
 - c. 1101
 - d. 100

BASIC COMPUTERS

15.	Conv	Convert binary 1110 to its decimal equivalent:				
	a.	13				
	b.	14				
	c.	15				
	d.	16				
16.		computer language in which calculations are carried out and information is stored in ory is:				
	a.	decimal				
	b.	hexadecimal				
	c.	octal				
	d.	binary				
17.	The o	The computer language system which uses the base 16 is known as:				
	a.	septagesimal				
	b.	hectadecimal				
	c.	hexadecimal				
	d.	octal				
18.	The	The computer language system which uses the base 8 is called:				
	a.	decimal				
	b.	binary				
	c.	octal				
	d.	hexadecimal				
19.	The number system which uses the numbers 0 to 9 followed by the letters A to F is:					
	a.	alpha numeric				
	b.	hexadecimal				
	c.	octal				
	d.	numeric alpha				
20.		In a digital computer binary 1 is represented by +5 volts and Binary 0 by earth. This is an example of:				
	a.	negative logic				
	b.	bipolar logic				
	c.	positive logic				
	d.	analog system				

- 21. In a negative logic system:
 - a. binary 1 is a low level, binary 0 is a high level
 - b. binary 1 is a high level, binary 0 is a low level
 - c. binary 1 is positive, binary 0 is negative
 - d. binary 1 and binary 0 are equal levels above and below zero
- 22. The permanent memory of a digital computer usually takes the form of:
 - a. Integrated circuits rated in megabytes
 - b. shift registers whose capacity is rated in mega or gigabytes
 - c. floppy or hard disks whose capacity is measured in mega or gigabytes
 - d. Central Processing Unit
- 23. The purpose of the Arithmetic Logic Unit within the Central Processing Unit is to:
 - a. act as a temporary store for information being processed
 - b. perform calculations in the binary number system
 - c. perform calculations in the binary, octal or hexadecimal system
 - d. perform all clock functions based on the computer clock frequency (clock time)
- 24. Within the Central Processing Unit, the temporary stores and accumulator which handle the data during processing are called:
 - a. Arithmetic Logic Unit (ALU)
 - b. Shift Registers
 - c. Control Unit
 - d. BIOS
- 25. Aircraft data in analog form, before being processed by a computer must be passed through a:
 - a. digital to analog converter (D to A)
 - b. EPROM
 - c. EAROM
 - d. analog to digital converter (A to D)

COMPUTERS SAQ ANSWER SHEET.

No	A	В	С	D	REF
1		X			
2				X	
3			X		
4	X				
5			X		
6				X	
7	X				
8		X			
9			X		
10	X				
11		X			
12				X	
13	X				
14		X			
15		X			
16				X	
17			X		
18			X		
19		X			
20			X		
21	X				
22	:		X		
23		X			
24		X			
25				X	

CHAPTER SEVEN - SEMICONDUCTORS

Contents

	F	Page
7.1	AN INTRODUCTION TO SEMICONDUCTORS	7 - 1
7.2	CONDUCTORS AND INSULATORS	7 - 1
7.3	SEMICONDUCTORS	7 - 2
7.4	N-TYPE MATERIAL	7 - 3
7.5	P-TYPE MATERIAL	7 - 4
7.6	CURRENT FLOW	7 - 5
7.7	THE P-N JUNCTION. 2.	7 - 5
7.8	REVERSE BIAS	7 - 6
7.9	FORWARD BIAS	7 - 6
7.10	THE JUNCTION DIODE	7 - 7
7.11	THE BI-POLAR OR JUNCTION TRANSISTOR	7 - 8
7.12	SUMMARY	- 10
7.13	AN INTRODUCTION TO LOGIC GATES 2.7	- 10
7.14	BINARY LOGIC	- 10
7.15	TRUTH TABLES	- 10
7.16	GATE SYMBOLS	- 11
7.17	POSITIVE AND NEGATIVE LOGIC 2.7	- 11
7.18	THE 'AND' GATE	- 12
7.19	THE 'OR' GATE	- 13
7.20	THE 'INVERTER' OR 'NOT' GATE 2.7	- 14

7.1 AN INTRODUCTION TO SEMICONDUCTORS.

Most people own a some type of hand held or desktop calculator these days. The cost of these useful devices varies depending on sophistication, simple ones are given away free as advertising gimmicks, yet there is more computing power inside one of these tiny machines than took Neil Armstrong to the moon!!

Transistorisation and miniaturisation have enabled us to build ever more sophisticated electronics and package them in ever smaller units. Modern pilots rely heavily on the electronic flight systems incorporated in their aircraft and therefore must have an understanding of how transistors, or more specifically **semi-conductors**, work.

7.2 CONDUCTORS AND INSULATORS.

Before proceeding with the explanation about how semiconductors work, let us remind ourselves about the general atomic construction of conductors and insulators.

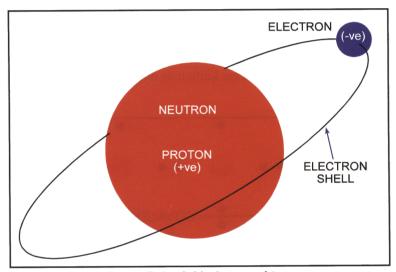


Figure 7.1. A Hydrogen Atom.

The most simple atom is the **Hydrogen** atom. It consists of a **nucleus**, containing one **proton** (positively charged) and one **neutron** (neutrally charged), and an **electron** (negatively charged) orbiting about the nucleus.

Conductors and insulators have more complex atoms with an increasing (equal) number of neutrons, protons and electrons with the latter orbiting the nucleus in multiple orbits or **shells**.

These atoms are held together by the bonds formed between the **valence** electrons in the outer shells and arrange themselves into a lattice type arrangement equidistant from each other. Electrons in the outer shells are less tightly bonded to their parent atom than those on the inner shells and are free to move from one atom to the next.

These electrons, known as **free electrons**, form the basis for current flow within the material. **Conductors**, formed by atoms held together by **electrovalent** bonds, possess large numbers of free electrons, this allows current to flow easily through the material or put another way; the material has **high conductivity** (**low resistivity**). Gold, silver and copper are all examples of good conductors.

Insulators, on the other hand, are formed by atoms held together by **covalent** bonds and possess few free electrons. This means that current flow is difficult; the material has **low conductivity** (high resistivity). Mica is one example of a good insulator.

7.3 SEMICONDUCTORS.

Semiconductors, as their name would imply, fall somewhere between a conductor and an insulator.

Both materials are formed by atoms with covalent bonds. Though each possess some free electrons at normal temperatures they are closer to being insulators than conductors. Thus an e.m.f. applied across the material would give rise to an intermediate current flow, higher than that in an insulator, but less than that in a conductor.

Conductivity can be improved by the controlled addition of impurities into the Silicon or Germanium material using a process known as **doping**.

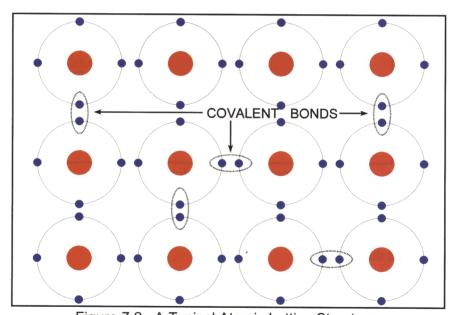


Figure 7.2. A Typical Atomic Lattice Structure.

7.4 N-TYPE MATERIAL.

By doping the Silicon or Germanium with **Arsenic** or **Antimony**, atoms which have 5 valance electrons in their outer shell are introduced into the lattice structure. The ratio of impurity atoms to original atoms (**doping ratio**) is in the order of 1:10⁸.

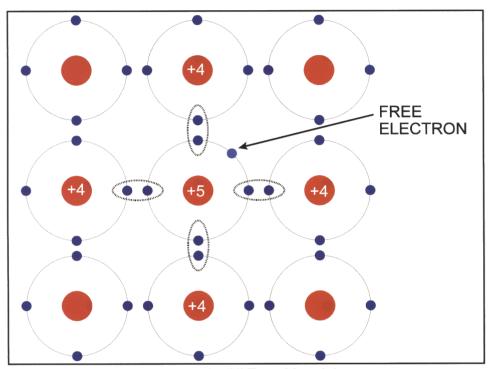


Figure 7.3. 'N' Type Material..

Four of the five electrons form covalent bonds with the surrounding atoms, the 5th electron, having no such ties, becomes a free electron. **Conductivity through the material is thus increased.**

We call this type of material **N-type** because of the surfeit of free electrons which are of course negatively charged. However, it should be noted that the material remains electrically neutral, for each free electron there is a fixed positive ion within the material.

7.5 P-TYPE MATERIAL.

By doping with impurities such **Aluminium** or **Idium**, again in the same doping ratio as above, atoms with only three valence electrons in their outer shell are introduced.

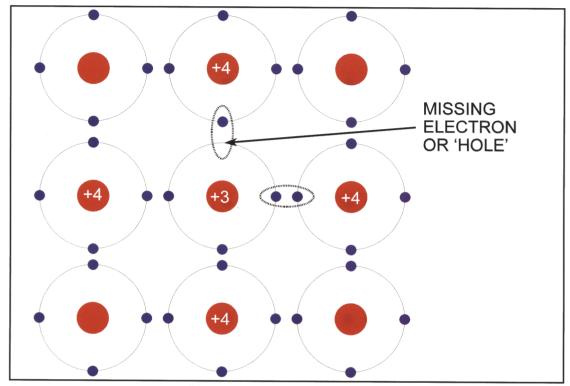


Figure 7.4. 'P' Type Material..

This time there are only 3 electrons to form the covalent bonds, one is missing. In other words there is a **hole** in the valent structure.

Electrons from adjacent atoms tend to move into these holes thus creating holes around the donor atoms which in turn 'steal' electrons from their neighbours moving the hole on further.

This apparent movement of holes increases the conductivity of the material.

Because of the shortage of electrons the material is classified as **P-type**.

Again, it should be noted, it possesses no electrical charge, there being an equal number of holes and fixed negative ions.

7.6 CURRENT FLOW.

Applying an e.m.f. across a piece of N-type material would cause the free electrons to migrate towards the positive terminal.

Any electrons leaving the material at the positive terminal are replaced by electrons entering at the negative terminal, thus the overall balance between free electrons fixed positive ions is maintained.

In P-type the situation is more complex, but in general, electrons are attracted into the positive terminal creating holes in this region.

The holes 'migrate' towards the negative terminal and are ultimately filled by an electron entering at that point.

Hence in P-type semiconductor material we can consider current flow as the drift of holes in the conventional direction, namely from the positive to the negative terminal.

Again, overall balance is maintained between electrons and fixed negative ions.

7.7 THE P-N JUNCTION.

If we **fuse** two small pieces of N and P-type materials together, by a process similar to **welding**, some free electrons from the N-type material **migrate** across the boundary into the P-type and similarly, holes migrate the other way.

This migration produces a charged region known as the **Depletion Layer** and creates a **Barrier Potential** restricting further electron/hole movement. This barrier potential may be represented as an imaginary battery, though it should be remembered, the regions of increased positive and negative charge exist only across the junction. **The material as a whole possess no electrical charge.**

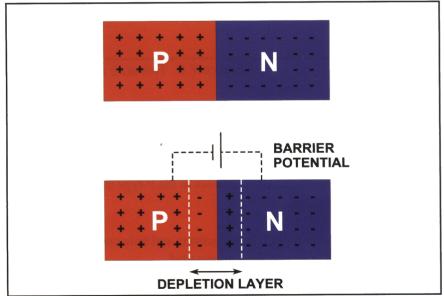


Figure 7.5. The P-N Junction.

7.8 REVERSE BIAS.

If we now connect an external e.m.f. across the P-N material, as shown in Figure. 7.6 A, more electrons are drawn across the barrier into the P-type material and more holes are drawn to the N-type.

This deepens the depletion layer and further electron/hole migration is prevented. Apart from a small leak current, in the order of μA , no significant current flows. The junction is said to be reverse biased.

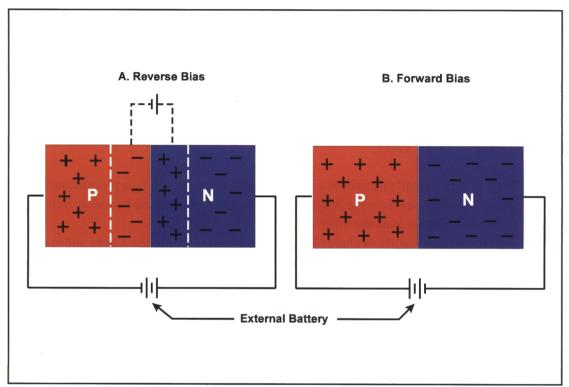


Figure 7.6. Reverse and Forward Bias.

7.9 FORWARD BIAS.

By applying the external e.m.f. as shown in Figure. 7.6 B, the direction of the electric field is such as to produce a drift of holes in the P-type material to the right, and of free electrons in the N-type to the left.

In the junction region, free electrons and hole combine, thus the barrier potential is overcome and current is free to flow unimpeded.

7.10 THE JUNCTION DIODE

It can be seen from Figure 7.7. that current can only flow in one direction through a semiconductor formed from P-N type material.

In other words the material acts as a **rectifier** and has similar conduction characteristics of a thermionic diode (valve).

It is therefore referred to as a **Junction Diode**.

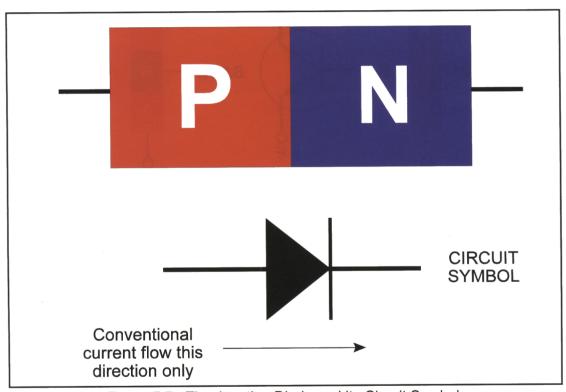


Figure 7.7. The Junction Diode and its Circuit Symbol.

7.11 THE BI-POLAR OR JUNCTION TRANSISTOR.

Construction: This is a combination of two junction diodes and consists of either a thin layer (typically 25 µm) of p-type semiconductor sandwiched between two n-type semiconductors (as shown in Figure 7.8 left) which is referred to as an n-p-n transistor, or a thin layer of n-type semiconductor sandwiched between two p-type semiconductors (as shown in Figure 7.8 right), which is referred to as a p-n-p transistor.

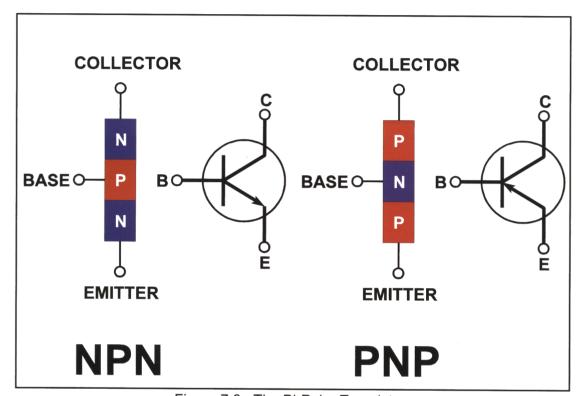


Figure 7.8. The Bi-Polar Transistor.

The three regions of either type of transistor are known respectively as **Collector**, **Base** and **Emitter**.

The circuit symbol for each transistor differs only in regard to the direction of the arrow between Base and Emitter.

The arrow always represents conventional current flow; thus for an N-P-N transistor it points from Base to Emitter, and for a P-N-P, from Emitter to Base.

Operation. N-P-N Transistor: If we apply an e.m.f. across the Collector - Emitter region, as shown in Figure. 7.9 left, no current flows.

AC ELECTRICS SEMICONDUCTORS

However, if we now add an e.m.f. between across the Base - Emitter region, as shown in Figure. 7.9 right, a large current flows from Emitter to Collector.

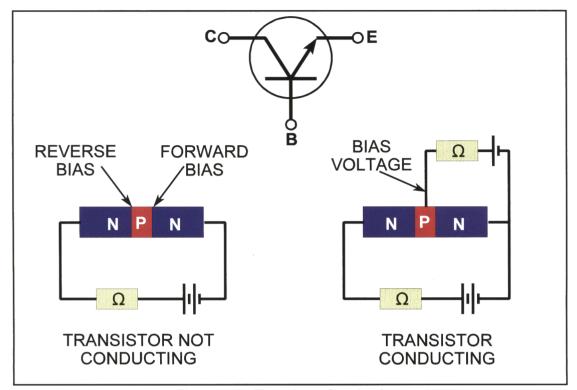


Figure 7.9. Transistor Conduction.

The theory governing the flow of current in a transistor is complex and generally beyond the scope of this course, but in simple terms here is what happens.

By applying an e.m.f., or **Bias voltage**, between Base and Emitter of an N-P-N transistor, the junction is forward biased and a large number of free electrons are attracted to the Base region.

However, in the relatively thin Base region, few holes are produced for these free electrons to combine with, so the surplus diffuse into the Collector region where they migrate towards the applied positive potential.

Holes that have combined with free electrons are replaced as an electron leaves the Base region for the positive terminal of the Bias supply.

Consequently, a relatively small Base - Emitter current flow produces a large Emitter - Collector flow.

Operation. P-N-P Transistor: A P-N-P transistor's operation is similar in all respects to that of an N-P-N transistor except that the applied e.m.f.s are reversed.

AC ELECTRICS SEMICONDUCTORS

7.12 SUMMARY.

The ability of a transistor to control a large Emitter - Collector current by means of a small Base - Emitter current means it can act as a **switch or amplifier**, by turning the Base - Emitter current on and off, or as an amplifier by superimposing a small alternating current signal on the Bias voltage. In conjunction with the Junction Diode and other electronic components, such as resistors, capacitors and inductors, the applications for the transistor are almost limitless.

Further more, the ability to control precisely those areas to which doping is applied, using **Photo-etching** techniques, means that all of the above components can be incorporated into a highly sophisticated and complex circuit within a single, small, piece of silicon. The ubiquitous **computer chip** is one such example.

For the future, as production techniques improve, faster, more powerful circuits will be contained in ever smaller packages, leading in turn to more sophisticated technology being incorporated in the modern airliner.

7.13 AN INTRODUCTION TO LOGIC GATES.

Logic gates, or gates, are a type of fundamental function performed by computers and related equipment. A single integrated circuit (IC) within a computer contains several gate circuits. Each gate may have several inputs and must have only one output.

There are six commonly used logic gates, the 'AND', the 'OR', the 'INVERT', the 'NOR', the 'NAND', and the 'EXCLUSIVE OR'. The name of each gate represents the function it performs.

7.14 BINARY LOGIC.

Logic gates are of a binary nature, i.e. the inputs and the outputs are in one of two states expressed by the digital notation '1' or '0'. Other corresponding expressions are also frequently used, they are:

- a) '1' on; true; high (H); closed; engaged.
- b) '0' off; false; low (L); open; disengaged.

7.15 TRUTH TABLES.

Truth Tables are a systematic means of displaying binary data. Truth tables illustrate the relationship between a logic gate's inputs and outputs. This type of data display can be used to describe the operation of a gate. For troubleshooting purposes, the truth table data is often reviewed in order to determine the correct output signal for a given set of inputs.

7.16 GATE SYMBOLS.

Each logic gate has a symbol of a specific shape. The symbols are designated to "point" in a given direction, that is, the inputs are always listed on the left of the symbol and the outputs on the right.

Since logic gate operate using digital data, all input and output signals will be comprised of '1's or '0's. Typically the symbol '1' represents 'ON' or voltage positive, and the symbol '0' represents 'OFF', or voltage negative. Voltage negative is often referred to as zero voltage or the circuit's ground.


7.17 POSITIVE AND NEGATIVE LOGIC.


As stated earlier, logic circuit input and output signals consist of two distinct levels. These levels are often referred to as 'binary 1' and 'binary 0'. The actual voltage levels required to achieve a 'binary 1' or 'binary 0' may vary between circuits.

- a. If positive logic is used in the digital circuit, a 'binary 1' equals a high voltage level and a 'binary 0' equals a low voltage level. The actual voltage values may be either both positive or both negative, or one positive and one negative. The only stipulation for positive logic is that a 'binary 1' is created by a greater positive voltage than a 'binary 0'. Each signal represents the greater positive voltage value as a 'binary 1', therefore each example employs the positive logic concept. Most digital systems employ positive logic throughout the entire computer and related component circuitry.
- b. The negative logic concept defines 'binary 1' as the lower voltage value and 'binary 0' as the higher voltage value (more positive). Although less popular, negative logic is used in some systems in order to meet certain design parameters.

7.18 THE 'AND' GATE.

The 'AND' gate is used to represent a situation where all inputs to the gate must be '1' (on) to produce a '1' (on) output. To be an 'AND' gate, input No. 1 and input No. 2 and input No. 3 etc, must be '1' to produce a '1' output. If any input is a '0' (off), the output will be '0' (off). The symbol and the truth table for a two-input AND gate are illustrated in Figure 7.10.

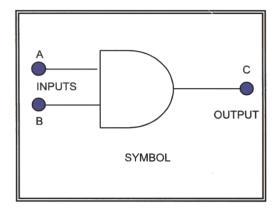

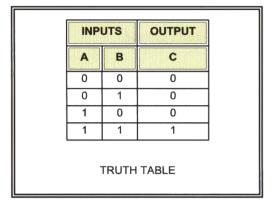

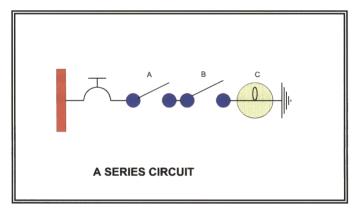


Figure 7.10. The Symbol and Truth Table for an 'AND' Gate.

A simple 'AND' circuit may also be represented by two switches in series used to turn on a light as shown in Figure 7.10. If both switches (inputs) are '1' (on), the light will turn '1' (on). If either switch is '0' (off), the light will be '0' (off).

The 'AND' gate is sometimes called an 'ALL or NOTHING' gate.


7.19 THE 'OR' GATE.

The 'OR' gate is used to represent a situation where any input being '1' (on) will produce a '1' (on) output. To be an 'OR' gate, input No. 1 or input No. 2 or input No. 3, etc, must be '1' to produce a '1' output.

Only if all inputs become '0' will the 'OR' gate produce a '0' output. If any input is a '1', regardless of the other input values the 'OR' gate will produce a '1' output.

A two-input 'OR' gate symbol and corresponding truth table are illustrated in Figure 7.11..

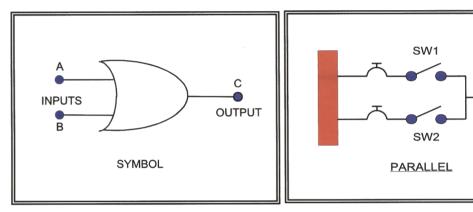A simple 'OR' circuit may be comprised of two switches in parallel controlling one light. If either switch is '1' (on), the light will turn '1' (on).



	INP	STL	OUTPUT
	A	В	C
	0	0	0
	0	1	1
Γ	1	0	1
	1	1	1
		TRUTH	TABLE

Figure 7.11. Representation of the 'OR' Gate.


The OR gate may be called an "ANY or ALL" gate.


7.20 THE 'INVERT' OR 'NOT' GATE.

The 'INVERT' gate is used to reverse the condition of the input signal. The 'INVERT' gate contains only one input and one output, and is most often used in conjunction with other gates.

The 'INVERT' gate is sometimes referred to as a 'NOT' gate. The symbol and truth table for an 'INVERT' gate are shown in Figure 7.12.

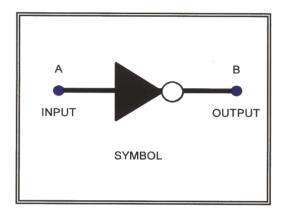An 'INVERT' circuit might be comprised of a switch controlling a normally closed relay which turns on or off a light. As also illustrated in Figure 7.12., if the switch is turned '1' (on), the light is '0' (off).



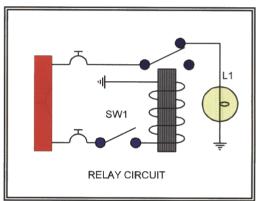



PROCESSAL AND COMPANY AND COMP	Spanning and a spanni			
INPUT	OUTPUT			
A	В			
0	1			
1	0			
TRUTH TABLE				

Figure 7.12. Representation of the 'INVERT' or 'NOT' Gate.

7.21 THE 'NAND' GATE.

The 'NAND' gate is an 'AND' gate with an inverted output. The output of this gate will be '1' if any input is '0'. This is the exact opposite of an 'AND' gate. The representations of a 'NAND' gate are shown in Figure 7.13.

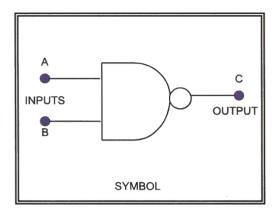

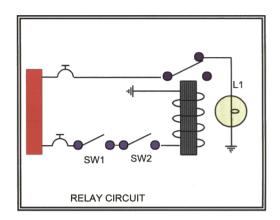


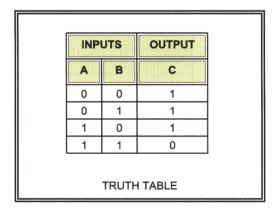



Figure 7.13. The Representations of the 'NAND' Gate.

The 'NAND' gate circuit illustrated in Figure 7.13.shows if either switch is closed there will be no output.

7.22 THE 'NOR' GATE.

The 'NOR' gate is an 'OR' gate with an inverted output. This results in a gate where any input being '1' will create a '0' output. The 'NOR' symbol, the truth table, the electronic circuit and the relay circuit which represent a 'NOR' gate are all illustrated in Figure 7.14.

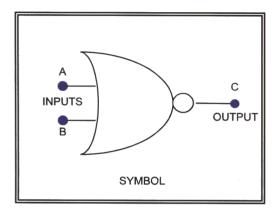

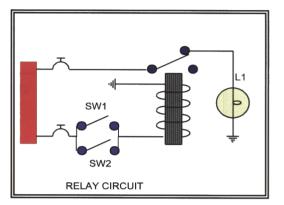

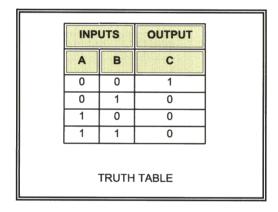



Figure 7.14. Representations of the 'NOR' Gate.


7.23 THE 'EXCLUSIVE OR' GATE.

The EXCLUSIVE OR gate is designed to produce a '1' output whenever its input signals are dissimilar.

An illustration of the representations of the 'EXCLUSIVE OR' gate is shown in Figure 7.15. This gate compares a maximum of two input signals to determine its output.

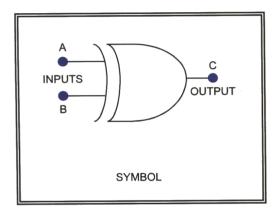As shown in the truth table within Figure 7.15., if the input signals have like values, the output will be '0', if the input signals have unlike values, the output will be '1'



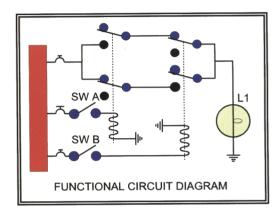


INPUTS		OUTPUT			
Α	В	C			
0	0	0			
0	1	1			
1	0	1			
1 1		0			
TRUTH TABLE					


Figure 7.15. Representations of the 'EXCLUSIVE OR' Gate.

SELF ASSESSMENT QUESTIONS - LOGIC

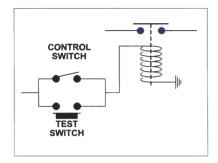
- 1. The logic function of the circuit shown is;
 - a) AND
 - b) OR
 - c) NOR
 - d) NOT




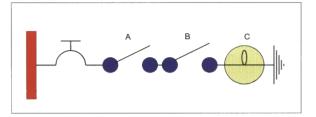- 2. The circuit shown here represents;
 - a) an 'AND' gate.
 - b) a 'NOR' gate.
 - c) an 'OR' gate.
 - d) an 'EXCLUSIVE OR' gate.




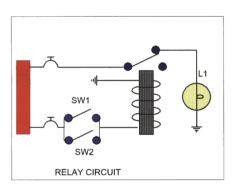3. The diagram is the equivalent of which of the accompanying symbols;-




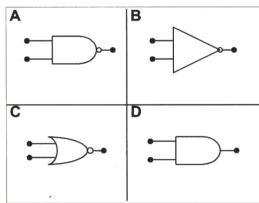

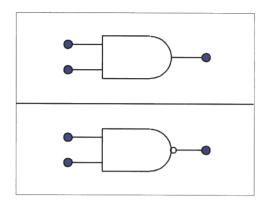
- 4. The gate symbols shown are;
 - a) 'AND' and 'NAND'.
 - b) 'EXCLUSIVE OR' and 'EXCLUSIVE NOR'.
 - c) 'OR' and 'NOR'.
 - d) 'OR' and 'EXCLUSIVE OR'.



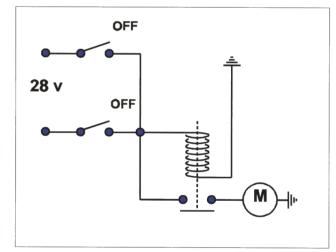
- 5. A gate which requires that all inputs must be HIGH to obtain an output would be;
 - a) a 'NOR' gate.
 - b) an 'OR' gate.
 - c) an 'AND' gate.
 - d) a 'NOT' gate.
- 6. This diagram represents;
 - a) an inverter.
 - b) an 'AND' gate.
 - c) an 'EXCLUSIVE NOR' gate.
 - d) an 'OR' gate.



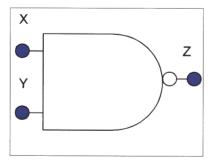
- 7. To obtain logic '0' at output 'Z' there must be;
 - a) logic '1' at 'X' and logic '0' at 'Y'.
 - b) logic '0' at 'X' and logic '1' at 'Y'.
 - c) logic '1' at 'X' and logic '1' at 'Y'.
 - d) logic '0' at 'X' and logic '0' at 'Y'.



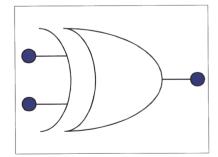
- 8. A transistor ;
 - a) can only be used as an amplifier.
 - b) can be used as a demi-conductor to act as an automatic switch or an amplifier.
 - c) is an inverted silicon controlled rectifier.
 - d) can be used as a semi-conductor to act as an automatic switch or an amplifier.
- 9. A transistor;
 - a) is made up of crystals in the arrangement of emitter, base and collector.
 - b) is made up of crystals in the arrangement of emitter, collector and base.
 - c) is made up of crystals in the arrangement of collector, emitter and base.
 - d) requires a current of ten amps through the base to transmit.
- 10. A gate with only one input and one output;
 - a) cannot be a 'double' gate.
 - b) is a 'NOT' gate.
 - c) can only be a 'semi-gate'.
 - d) cannot be a 'NOT' gate.
- 11. The two most commonly used gates are;
 - a) 'NOT' and 'NOR'.
 - b) 'OR' and 'EXCLUSIVE AND'.
 - c) 'AND' and 'OR'.
 - d) 'AND' and 'NAND'.
- 12. Truth tables illustrate the relationship between;
 - a) inputs and outputs.
 - b) integrated gates for trouble shooting.
 - c) the sequence of operation of the gates.
 - d) electronic and electrical circuits.
- 13. The output expression for this type of gate is;
 - a) 'AND'.
 - b) 'EXCLUSIVE NOR'
 - c) 'EXCLUSIVE OR'.
 - d) 'EXCLUSIVE NOT'.



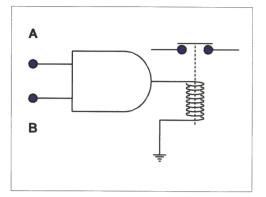- 14. In order to energise the relay shown in this circuit, the logic state at the inputs must be;
 - a) logic '0' at points 'A' and 'B'.
 - b) logic '0' at point 'A' and logic '1' at point 'B'.
 - c) logic '1' at points 'A' and 'B'.
 - d) always identical at points 'A' and 'B'.



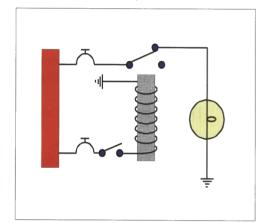- 15. The type of logic gate represented by this diagram is;
 - a) 'OR'
 - b) 'NAND'
 - c) 'AND'
 - d) 'NOT'.



QUE	1	2	3	4	5	6	7	8	9	10
ANS										
REF										

QUE	11	12	13	14	15	16	17	18	19	20
ANS										
REF										

LOGIC SELF ASSESSMENT ANSWERS

QUE	1	2	3	4	5	6	7	8	9	10
ANS	В	A	С	A	С	D	С	D	A	В
REF										
QUE	11	12	13	14	15	16	17	18	19	20
QUE ANS	11 C	12 A	13 C	14 C	15 D	16	17	18	19	20

JOINT AVIATION AUTHORITIES AIRLINE TRANSPORT PILOT'S LICENCE

Theoretical Knowledge Manual

AIRCRAFT GENERAL KNOWLEDGE 2

021 02 05 BASIC RADIO PROPAGATION

Second Edition, First Impression.







SUBJECT 3 BASIC RADIO PROPAGATION

TABLE OF CONTENTS

CHAPTER 01 BASIC PRINCIPLES CHAPTER 02 OSCILLATORS CHAPTER 03 ANTENNAE

CHAPTER 1 - BASIC PRINCIPLES

Contents

	I	Page
1.1	INTRODUCTION	1 - 1
1.2	AC	1 - 1
1.3	RADIO WAVES	1 - 2
1.4	POLARIZATION	1 - 2
1.5	SPEED OF PROPAGATION	1 - 3
1.6	WAVELENGTH	1 - 3
1.7	FREQUENCY UNITS	1 - 3
1.8	USE OF FREQUENCY UNITS	1 - 3
1.9	WAVELENGTH, FREQUENCY, AND SPEED OF PROPAGATION 3.	1 - 3
1.10	FREQUENCY / WAVELENGTH CONVERSIONS	1 - 4
1.11	FREQUENCY SPECTRUM 3.	1 - 5
1.12	PHASE	1 - 5
1.13	PHASE DIFFERENCE	.1 - 6
1.14	ATTENUATION	.1 - 6
1.15	REFRACTION	.1 - 7
1.16	PROPAGATION PATHS	.1 - 7
1.17	DIRECT AND GROUND-REFLECTED WAVES	.1 - 7
1.18	SURFACE WAVE	.1 - 9
1.19	GROUND WAVE. 3.1	- 10
1.20	SKY WAVE	- 10
1.21	THE IONOSPHERE	11
1.22	IONISED LAYERS	11
1.23	D-LAYER. 3.1	11
1.24	E-LAYER. 3.1	- 11
1.25	F-LAYERS. 3.1	- 12
1.26	HF SKY WAVES	- 13
1.27	FADING. 3.1	- 16
1.28	FADE-OUTS	- 16


1.29	HF SKY WAVE RANGES	3.1 - 16
1.30	SKY WAVES - SUMMARY	3.1 - 16
1.31	FREQUENCY / PROPAGATION TABLE	3.1 - 17
1.32	FREAK PROPAGATION	3.1 - 17
1.33	DUCT PROPAGATION	3.1 - 18
1.34	SCATTER PROPAGATION	3.1 - 18
1.35	MODULATION	3.1 - 18
1.36	AMPLITUDE MODULATION (AM)	3.1 - 19
1.37	SIDE FREQUENCIES.	3.1 - 20
1.38	SIDEBANDS AND BANDWIDTH	3.1 - 20
1.39	SINGLE SIDEBAND TRANSMISSIONS	3.1 - 20
1.40	FREQUENCY MODULATION (FM)	3.1 - 21
1.41	AERIAL POLAR DIAGRAMS	3.1 - 21
1.42	CLASSES OF EMISSIONS	3.1 - 23
1.43	FREQUENCY/WAVE LENGTH CONVERSION	3.1 - 24
1.44	DIRECT WAVE	3.1 - 25
1.45	ANSWERS	3.1 - 27
REVIS	ION QUESTIONS	3.1 - 29
OHEGT	TION DADED	2 1 21

1.1 INTRODUCTION.

It is generally agreed that even a partial understanding of radio theory helps in appreciating the limitations of the various radio aids to navigation. These notes aim to introduce the fundamentals as simply as possible with a minimum of mathematics.

1.2 AC.

In the simple circuit depicted in Figure 1.1(a), alternating current flows in the circuit. This simply means that the direction of current flow is being reversed at regular intervals. At one instant the flow is clockwise, the next it is anticlockwise round the circuit. A graph of current against time in this case would appear as in Figure 1.1(b). It can be shown that the curve is a sine curve.

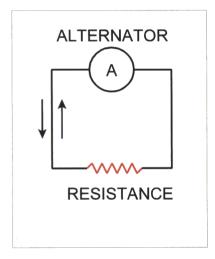

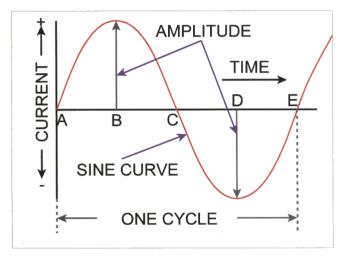


Figure 1.1 (a)

Figure 1.1 (b)

A study of this curve shows that the current starts at zero (point A), increases to a maximum value in one direction (at B), decreases to zero (at C), increases to maximum again in the opposite direction (at D), and then reduces to zero again at point E. This sequence of events is called a **Cycle**, which could be defined as one complete oscillation of the alternating current. The + and - signs on the graph simply indicate the reversing directions of current flow.

It can be seen from the graph in Figure 1.2(b). that at points B and D the instantaneous current flow has a maximum value. This peak value (in either direction) is called the **Amplitude** of the current. Since a similar graph of alternating voltage in the circuit could be plotted, the term amplitude is defined as the peak value of the alternating quantity (current or voltage).

The term **Frequency** is used to state the number of cycles occurring in one second. Frequency is measured in Hertz (Hz). The time for one complete cycle is called the period or periodic time(T). The relationship between frequency and periodic time is such that one is the reciprocal of the other; ie

$$F = \underline{1}$$
 and $T = \underline{1}$

1.3 RADIO WAVES.

If an alternating current of suitably high frequency is fed to a transmitting aerial, the energy is not confined to the metal of the aerial but radiates out into space in the form of electro-magnetic waves (radio waves). This radiation of energy through space comprises alternating electrical and magnetic fields at right angles to each other. The amplitude of each field varies (oscillates) between zero and a maximum value, at the same frequency as the alternating current in the aerial.

1.4 POLARIZATION.

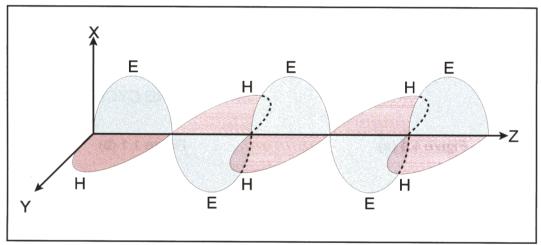


Figure 1.3. Vertical Polarization.

The term polarization is used to describe the direction or plane of oscillation of the electrical field of an electro-magnetic wave. For instance a vertical transmitting aerial produces (mainly) a vertically polarized radio wave, with the electrical field (E) oscillations occurring in the vertical plane and the magnetic field (H) oscillations in the horizontal plane. For **efficient** reception, the receiving aerial should also be vertical. If the transmitting aerial is horizontal, the receiving aerial should also be horizontal.

The electric and magnetic fields oscillate at right angles to each other and both are at right angles to the direction of propagation (or travel) of the radio wave. Figure 1.3. shows the peak values E and H of the electric and magnetic fields of a vertically polarized wave.

1.5 SPEED OF PROPAGATION.

Radio waves travel at the speed of light. The speed is virtually constant and is:-

300,000,000 metres per second,

or

162, 000 nautical miles per second

1.6 WAVELENGTH.

The wavelength of a radio wave can be defined as the distance travelled by the radio signal during the transmission of one cycle. Wavelength is normally expressed in metres unless it is less than one metre, when centimetres or millimetres are used.

1.7 FREQUENCY UNITS.

Frequencies are expressed in Hertz (Hz). One Hertz equals one cycle per second. Radio frequencies are high and for convenience the following units may be used:-

Kilo-Hertz	(kHz)	= 1,000 Hz	$= 10^3 \text{ Hz}$
Mega-Hertz	(MHz)	= 1,000,000 Hz	$= 10^6 \mathrm{Hz}$
Giga-Hertz	(Ghz)		$= 10^9 \mathrm{Hz}$
Tera-Hertz	(THz)		$= 10^{12} \text{ Hz}$

1.8 USE OF FREQUENCY UNITS.

kHz are used, normally, up to 3 000 kHz (3MHz)

MHz are used, normally, between 3 and 3 000 MHz (3 GHz)

GHz may be used from 3 GHz upwards, though it is common to continue to use MHz.

THz are not currently used with radio navigation aids.

Examples:

Droitwich Broadcasting Station

200 kHz

Doppler Navigation Aid

8 800 MHz or 8.8 GHz

1.9 WAVELENGTH, FREQUENCY, AND SPEED OF PROPAGATION.

The relationship between these three quantities is:-

 $c = f \lambda$

Where c = speed of propagation (m/s)

f = frequency in Hz

 λ = wavelength in metres.

It can also be seen that:-

$$f = \frac{c}{\lambda}$$
 $\lambda = \frac{c}{f}$

With these formulae, it is a fairly simple matter to convert between wavelength and frequency. It can be seen from the formulae that wavelength is inversely proportional to frequency; so that if frequency is increased, wavelength will decrease. If the frequency were doubled the wavelength would be halved.

The transmissions listed below exemplify wavelength decreasing as frequency increases.

Facility	Frequency	Wavelength
Droitwich Broadcasting Station Fan Marker	200 kHz 75 MHz	1 500 metres 4 metres
Precision Approach Radar	10 000 MHz	3 cm

1.10 FREQUENCY / WAVELENGTH CONVERSIONS.

Example No.1 What frequency corresponds to a wavelength of 1,500 m?

Frequency Hz =
$$\frac{\text{Speed of Propagation (metres/sec)}}{\text{Wavelength (metres)}}$$

= $\frac{300,000,000}{1,500}$ = 200,000 Hz (or cps) = 200 kHz (Answer)

Example No.2 What is the wavelength of a 300 kHz transmission?

Wavelength (metres) =
$$\frac{\text{Speed of Propagation (metres/sec)}}{\text{Frequency (Hz)}}$$
$$= \frac{300,000,000}{300 \times 1,000}$$
$$= 1,000 \text{ m. (Answer)}$$

1.11 FREQUENCY SPECTRUM.

Frequencies	Frequency Band	Wavelength	Facilities
3-30 kHz	VLF (Very Frequency) Low	100 km - 10 km	Very long range navigation.
30-300 kHz	LF (Low Frequency)	10 km - 1km	Decca, NDB, Loran -C, long/medium wave broadcasting stations (B/S).
300-3,000 kHz	MF (Medium Frequency)	1 km - 100 metres	NDB, B/S Radio Range.
3 - 30 MHz	HF (High Frequency)	100 metres-10 metres	HF R/T
30 - 300 MHz	VHF (Very High Frequency)	10 metres -1 metre	VHF R/T, VDF, VOR, marker beacons, ILS.
300 - 3,000 MHz	UHF (Ultra High Frequency)	1 metre -10 cm	ILS Glidepath, DME, some Surveillance Radar.
3 - 30 Ghz (3,000 - 30,000 MHz)	SHF (Super High Frequency)	10 cm -1 cm	Precision Approach Radar (PAR), some Surveillance Radar, Doppler, Airborne Weather Radar (AWR), Radio Altimeter.
30 - 300 GHz	EHF (Extremely High Frequency)	1 cm -1 mm	Airfield Surface Movement Radar, experimental radar.

1.12 PHASE.

In earlier paragraphs the sinusoidal variations of an alternating current or voltage during one cycle were described. The stage reached in a cycle at a given instant in time is known as the **Phase** of the current or voltage. Phase is expressed in degrees (between 0° and 360°).

This is illustrated in Figure 1.4..

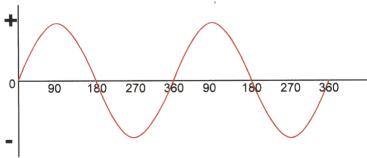


Figure 1.4. Phase.

1.13 PHASE DIFFERENCE.

Two radio waves at the **same frequency** can be 'In Phase' or 'Out of Phase' by any number of degrees from 1° to 359°. It is essential that the two signals are at the same frequency for there to be a fixed phase difference between them. If they were at different frequencies (and therefore different wavelengths) the phase difference would be continually changing.

With some radio aids, including VOR and Decca, the phase difference between two signals is measured in order to establish a position line. Figures 1.5(a)., 1.5(b)., and 1.5(c). depict examples of 'in phase' and 'out of phase' signals.

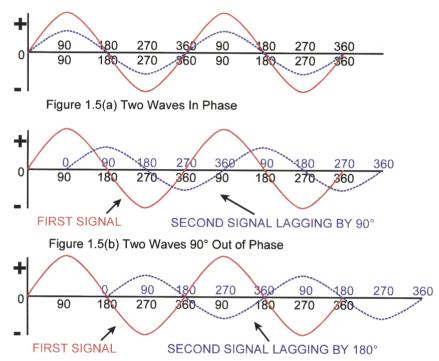


Figure 1.5 (c) Two Waves 180° Out of Phase

1.14 ATTENUATION.

The term **attenuation** means the loss in strength of a radio signal as range from the transmitter increases. The signal strength received is inversely proportional to the distance from the transmitter. A wave becomes attenuated as range increases because:-

- a) The radio energy available is spread over a greater area.
- b) Radio energy is lost to the earth, the atmosphere, and sometimes to the ionised layers above the earth.

One factor on which the operational range of a radio emission depends is the transmitter power. The range obtainable is proportional to the square root of the power; in other words if the range is to be doubled, the transmitter power must be quadrupled.

1.15 REFRACTION.

As a general rule, radio signals travel in straight lines, that is, they follow great circle paths over the surface of the earth. Under certain circumstances, however, the path of a signal may change direction. This change of direction is known as **refraction**. The amount of refraction varies considerably, depending on conditions. Well-known examples of refraction are:-

Coastal Refraction - where there is a change in direction when a signal crosses a coastline.

Atmospheric Refraction - Where changes in direction occur due to variations in temperature, pressure, and humidity - particularly at low altitude.

Ionospheric Refraction - where the wave changes direction as it passes through an ionised layer.

1.16 PROPAGATION PATHS.

The path of a radio wave from a transmitter to a receiver many miles away is not necessarily direct. The following paragraphs describe the various paths a radio signal can follow. In many cases, the signal may be reaching the receiver by more than one path at the same time, and because of the different path lengths there will be phase differences between the signals. Such phase differences affect the resultant signal strength.

For instance, if two waves from the same transmitter travel by different paths and arrive 180° out of phase, as in Figure 1.5(c)., they will cancel each other if their amplitudes are the same. The resultant signal strength will be zero, so no signal will be received. Changes in phase difference will cause changes in signal strength so producing the effect known as 'fading'.

1.17 DIRECT AND GROUND-REFLECTED WAVES.

A signal which travels in a straight line between transmitter and receiver is called the **direct wave**. In addition to this, there is normally a signal arriving at the receiver after reflection at the earth's surface. This is the **ground-reflected wave**. These two waves are jointly known as the **Space Wave** and are depicted in Figure 1.6(a). (In this and other diagrams, the abbreviation Tx is used for transmitter and Rx for Receiver.)

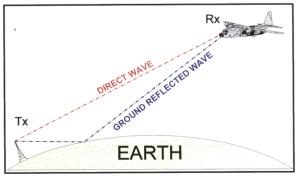


Figure 1.6(a). Space Wave.

Since the direct and reflected waves follow different paths they may arrive at the receiver with large phase differences. The situation is further complicated by a change in phase which occurs at the point of reflection of the ground-reflected wave. The net result is that, for instance, an aircraft flying towards a ground station may suffer fading or temporary loss of VHF communications with that station. The range at which this occurs depends on ground aerial height above the surface, aircraft altitude, and frequency.

The curvature of the earth limits the use of the direct wave. It can be seen from Figure 1.6(b). that the aircraft 'below the horizon' cannot use the direct wave for communications.

The lowest direct wave is just tangential to the surface and is known as the 'horizon ray'. It will be appreciated that direct wave communications for the aircraft in Figure 1.6(b). could be restored by either raising the height of the ground aerial or increasing the aircraft's altitude.



Figure 1.6(b). Line of Sight.

A formula used for calculating the maximum range of direct wave reception is:-

Range (nm) = 1.25 (
$$\sqrt{h_1}$$
 + $\sqrt{h_2}$)
where h_1 = height of ground aerial (feet AMSL)
 h_2 = aircraft altitude (feet AMSL)

This formula allows for a small amount of refraction in the lower layers of the atmosphere, which gives a slightly better range than would be obtained if the direct wave followed a perfectly straight path without any downward refraction. Under normal conditions, the space wave provides the only propagation path for frequencies **above** about 30 MHz.

Therefore, except on fairly rare occasions, communications in the VHF and higher bands suffer from **line of sight** transmission with range limited by the curvature of the earth and any high ground which interrupts the line of sight. Note that the range limitation imposed by Line of sight transmission is useful when there is a shortage of available frequencies.

For instance, with VHF R/T, except in freak conditions, the curvature of the earth gives protection from mutual interference between stations using a common frequency provided they are well-separated geographically.

1.18 SURFACE WAVE.

If the space wave were the only means of propagation, communications could only be 'line of sight'. However, the phenomenon of **diffraction** can produce a **surface wave**, a signal which follows the curvature of the earth as depicted in Figure 1.7.

Diffraction, which occurs for all types of wave motion, allows the wave to pass round an obstacle. With the surface wave, the obstacle is the earth and the amount of diffraction depends on the wavelength in relation to the radius of the earth. With longer wavelengths (lower frequencies) the diffraction effect becomes more pronounced with consequently improved surface wave range.

The type of surface also influences the range - for two reasons:

- a) it affects the amount of downward 'bending' of the wave.
- b) different surfaces absorb different amounts of radio energy from the wave, so affecting the rate of attenuation. The latter is always greater over land than over sea so surface wave range is better over sea than over land.

Frequency is also important, the **lower frequencies suffering less attenuation** along the surface and therefore giving better surface wave range.

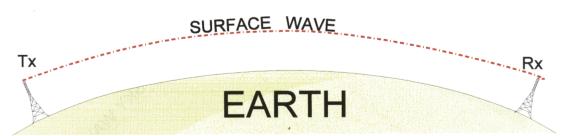


Figure 1.7. Surface Wave.

Surface wave propagation is complex, but the following general rules can be stated:-

- a) Surface wave range is greatest at very low frequencies (most diffraction and least attenuation).
- b) At frequencies above about 30 MHz, surface wave range is only a few miles (very little diffraction but rapid attenuation).
- c) At very low frequencies, surface wave range is great, and is nearly as great over land as over sea, but as frequency is increased the range over land (particularly dry land) decreases far more rapidly than over sea.

1.19 GROUND WAVE.

The term **ground wave** is used to describe the combination of direct wave, ground-reflected wave, and surface wave. Not all these are necessarily present together. For instance, below the horizon the ground wave consists of the surface wave alone - provided the frequency is low enough (below about 30 MHz).

1.20 SKY WAVE.

Yet another mode of propagation is by sky waves. These are waves which have been reflected or refracted down from **ionised layers** above the earth and are sometimes known as ionospheric waves. More details of sky wave propagation are given in the following paragraphs.

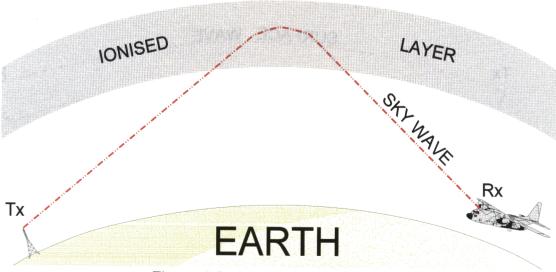


Figure 1.8. Ionospheric Refraction.

1.21 THE IONOSPHERE.

Ultra-violet light from the sun can cause electrons to become separated from their parent atoms of the gases in the atmosphere. The atoms are left with resultant positive charges and are then known as ions. The intensity of this ionisation depends on the strength of the ultra-violet radiation and the density of the air. The part of the atmosphere in which this process occurs is called the ionosphere, extending from about 50 km to as high as 500 km above the earth's surface. The ionospere is therefore situated above the stratosphere (which lies above the troposphere).

Several definite ionised layers exist within it. When a radio wave enters such a layer, refraction occurs causing the wave to be bent away from its straight path. The amount of refraction depends on the frequency, the angle at which the wave enters the layer and the intensity of ionisation. Under certain circumstances the wave may be bent so much that it is returned to earth as a **sky wave** as illustrated in Figure 1.8.

1.22 IONISED LAYERS.

During daytime hours there are four main ionisation layers designated D, E, F_1 and F_2 in ascending order of height. At night, when the sun's radiation is absent, ionisation still persists but is less intense, and fewer layers are found. Since the strength of the sun's radiation varies with latitude, the structure of the ionosphere varies widely over the surface of the earth.

Another factor affecting the layers is the state of the sun, since sunspots affect the amount of ultra-violet radiation. Figures 1.9(a)., 1.9(b)., and 1.9(c). show the approximate vertical distribution of the layers over the British Isles by day and night in summer and winter.

1.23 **D-LAYER.**

This layer is only significant during daylight hours, dispersing soon after sunset. It is the lowest layer and its intensity of ionisation is not great. VLF waves are reflected from the base of the layer. LF and MF waves enter the layer and are severely attenuated, without being appreciably refracted. Higher frequency signals pass through the layer with less attenuation. The practical effect on LF and MF transmissions is that daytime up-going waves are absorbed by the D-layer, so that LF/MF sky waves which would otherwise be refracted back to earth from the higher layers are very weak or completely absent by day.


1.24 E-LAYER.

This layer, which used to be known as the Kennelly-Heaviside layer, is strongly ionised by day and remains weakly ionised by night. It produces strong sky waves in the LF and MF bands by night, but in daytime the D-layer causes so much attenuation, as mentioned in Paragraph 1.23., that sky waves are too weak to be usable in these bands by day.

Usable HF sky waves may be produced by the E-layer by night and day. VHF signals pass through the E-layer with insufficient refraction to produce sky waves except under freak conditions (described in later notes). Ionospheric refraction is negligible with UHF, SHF and EHF signals, so sky waves do not occur in these bands.

1.25 F-LAYERS.

At night there is a single F-layer (originally known as the Appleton layer) above the E-layer, but in daytime the F divides into two - the F_1 and F_2 layers. The F-layers are the highest and most intensely ionised layers. Strong sky waves are produced in the LF, MF, and HF bands at night but, as in the case of the E-layer, only the HF band has usable F-layer sky waves by day. As with the E-layer, signals in the VHF and higher bands escape through the F-layer into space with, normally, no sky waves produced.

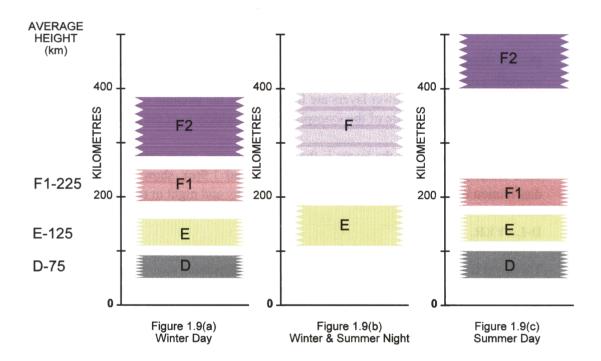

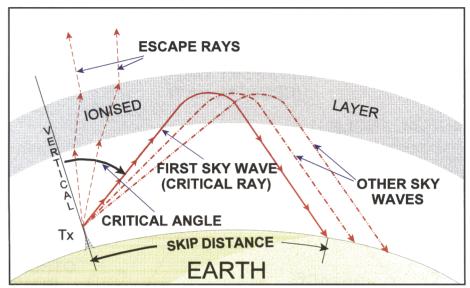


Figure 1.10. Critical Angle (HF Band).

1.26 HF SKY WAVES.

Sky wave propagation occurs in the HF band (3-30 MHz). However there are many variable factors which decide whether or not there is a propagation path open between transmitter and receiver for long range radio-telephony.

For a given frequency, and state of the ionosphere, the amount of refractive 'bending' of the wave will depend on the angle at which the wave penetrates the layer. From Figure 1.10. it can be seen that waves travelling nearly vertically may escape through a layer (they may be returned to earth from a higher, more intensely ionised layer).

For waves ascending with an increased angle with the vertical the amount of bending is greater, and when the angle with the vertical is increased to the **critical angle**, the path is bent enough for the wave to return to earth as the 'first sky wave'. Waves making an angle with the vertical greater than the critical angle will also produce sky waves, coming down to earth at greater ranges than that of the first sky wave. The range from the transmitter of the first sky wave for a given frequency and set of conditions is called the **skip distance**.

Note that the surface wave from a HF transmitter may become completely attenuated at a shorter range than that at which the first sky wave returns to earth. This leaves an area in which neither ground nor sky waves are received and which is known as **dead space**. Figure 1.11. illustrates this phenomenon.

Critical angle depends largely on frequency. The higher the frequency, the greater the critical angle. Therefore, if skip distance is to be reduced, a lower frequency has to be used. This is most significant when choosing the optimum frequencies for HF communications and ensuring that the skip distance is less than the range of the distant receiver.

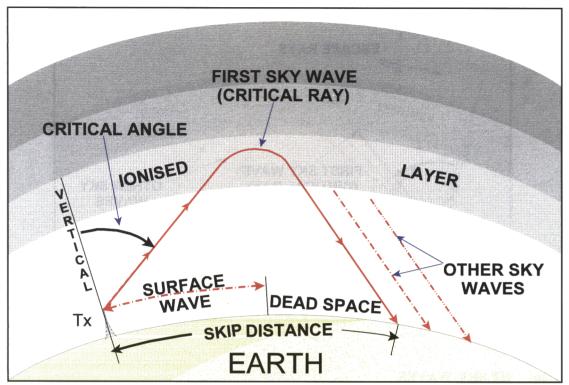


Figure 1.11. Dead Space and Skip Distance.

As frequency is reduced then, the critical angle decreases and skip distance becomes shorter. The frequency at which the critical angle reaches zero is called the **critical frequency**. This is the highest frequency which will give vertical reflections. With any higher frequency a wave travelling vertically would escape through the layer.

At and below the critical frequency the intensity of ionisation in the layer is great enough to produce vertical reflections. Measurements of critical frequency for the E and F layers are made in various parts of the world and these, together with past records, are used to predict the optimum HF R/T working frequencies.

It should be noted that for frequencies above about 30 MHz, waves generally escape through the layers into space - regardless of the angle the wave makes with the vertical. Thus sky waves are relatively rare in the VHF and higher frequency bands.

For good long-range HF R/T reception a frequency must be chosen which will not suffer too much attenuation. If a relatively high frequency is used, for example 20 MHz, most of the energy will pass through the E-layer and be reflected from the more intensely ionised F-layer. (The higher the frequency, the greater the degree of ionisation required to give reflections.)

This has advantages. A single reflection from the F-layer can give about the same range as a double reflection from the E-layer, as shown in Figure 1.12. The F-layer reflection will be stronger because it has only one change in direction (with associated energy-loss) instead of three with the double E-layer reflection.

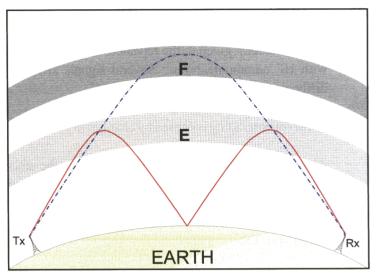


Figure 1.12. Single and Double Reflections.

Furthermore, the signal will not be confined below the E-layer, in a region where denser atmosphere and daytime D-layer cause more attenuation.

It is worth noting that as frequency is reduced and attenuation of the E-layer reflections increases, a limit is reached called the 'Lowest Usable High Frequency'. Below this frequency the attenuation is too great for the signal to be usable. Yet another reason for using the higher frequencies is that natural radio noise (static) is worst at low frequencies, becoming much less significant as the VHF band is approached.

Thus for least attenuation (and so the highest received signal strength for a given transmitter power) a frequency is chosen which is as high as possible without exceeding the **MUF** (**Maximum Usable Frequency**) for the path between the transmitter and distant receiver. The MUF is that frequency (for the prevailing conditions) which produces a skip zone extending just short of the distant receiver. Any higher frequency would give a higher critical angle and a greater skip distance extending beyond the receiver which would then lose that sky wave contact with the transmitter.

MUF at night is much less than by day because the intensity of ionisation in the layers is less so that lower frequencies have to be used to produce the same amount of refractive bending and give the same critical angle and skip distance as by day. However, the signal attenuation in the ionosphere is also much less at night so the lower frequency needed is still usable. **Hence the night frequency for a given path is about half the day frequency.** It can be seen that shorter distances can be 'worked' at night than by day while still using a single reflection from the F-layer.

Note that the MUF not only varies with path length and between day and night, but also with season, meteor trails, sunspot state, and sudden ionospheric disturbances produced by eruptions on the sun. Because of the variations of MUF, HF transmitting stations have to use frequencies varying widely between about 2 and 20 MHz.

1.27 FADING.

This is the term given to the repeated variations in received signal strength which are common with HF communications. Several signals arriving by different paths with varying phase differences cause 'interference' fading.

Polarization fading is caused by changes in polarization of the wave during refraction in a layer.

Absorption fading is caused by variations in the amount of attenuation, while 'skip fading' is caused by changes in the ionisation of the layer varying the MUF and so the skip distance so that the receiver may alternately lie inside and outside the skip zone.

1.28 FADE-OUTS.

Complete loss of HF communications sometimes take place and may last for many hours. This is caused by eruptions on the sun which produce a high level of radio noise, increased attenuation in the lower levels, and a reduction in the reflecting efficiency of the F-layer.

1.29 HF SKY WAVE RANGES.

It must be remembered that sky waves will not be received within the skip distance - probably several hundred miles from the transmitter. The theoretical **maximum** range obtainable by means of a single reflection from the E-layer is about 1 300 nm; from the F-layer about 2 500 nm. This theoretical maximum range is achieved with the transmitted signal leaving the earth's surface tangentially.

Ranges of 8 000 nm or more may be achieved by means of multiple reflections - mainly from the F-layer - the signal being alternately refracted down from the layer and reflected up again fro the earth's surface until it becomes too weak to use.

1.30 SKY WAVES - SUMMARY.

Sky waves are sometimes useful, sometimes a nuisance. They provide long-range communications in the HF band by day and night. In the LF and MF bands, sky waves greatly increase the effective range of Loran without serious reduction in accuracy. On the other hand, ADF errors are immensely increased at night due to the reception of sky waves (which are absorbed by the D-layer by day). LF / MF sky waves also seriously increase the amount of mutual interference between NDBs and broadcasting stations at night.

It should be remembered that sky waves are rare in the VHF, UHF, SHF, and EHF bands and performance of the aids in these bands is much the same at night as by day. The main factors which determine whether sky waves will be received at a given point remote from a transmitter are:

- a) Frequency band in use (sky waves are rare in the VHF and higher frequency bands).
- b) Range from transmitter. Sky waves suffer attenuation which varies with the state of the ionosphere. Noise level also varies. Maximum range is unlikely to exceed 8 000 nm.
- c) Frequency mainly in the HF band, where it affects skip distance.
- d) Power of transmitter, type of emission (see later notes), and sensitivity of the receiver.
- e) State of the ionosphere which varies with time of day, season of the year, and state of the sun and affects the amount of refraction, attenuation, and radio noise level.

1.31 FREQUENCY / PROPAGATION TABLE.

The following table summarises the main features of the various frequency bands.

Frequency Band	Type of Propagation
VLF (3-30 kHz)	Ground and sky waves
LF (30-300 kHz)	Ground waves by day, sky and ground waves at night
MF (300-3 000 kHz)	As for LF band
HF (3-30 MHz)	Mainly sky waves - day and night
VHF, UHF, SHF, (30-30 000 MHz)	Space wave (line of sight transmission) except for (see Paragraph 1.32.) Freak propagation

1.32 FREAK PROPAGATION.

It has been stated that for frequencies above about 30 MHz, transmission is normally 'line of sight' so that propagation is by means of the space wave. Under certain conditions of freak or 'anomalous' propagation, however, ranges much greater than line of sight ranges can be achieved by means of **duct propagation** and **scatter propagation**.

1.33 DUCT PROPAGATION.

This effect, also called 'super-refraction, is associated with a temperature inversion and a rapid decrease in humidity with height. Such meteorological conditions are most often found at the surface over land in high pressure conditions at night and in the early morning. A warm air mass over a cold sea can also produce the effect. It can also occur at higher levels.

The way in which radio signals can be 'trapped' in a duct of cold air is shown in Figure 1.13.. This process sometimes permits reception of signals at the surface hundreds of miles beyond the horizon. The effect is most common in the SHF and UHF bands, but is also encountered in the VHF band if the duct is sufficiently deep (say, 500 ft). Duct propagation can cause annoying interference between control towers using the same R/T frequency, and false range indications on ground radar screens.

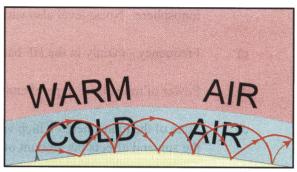


Figure 1.13 Duct Propagation.

1.34 SCATTER PROPAGATION.


The E-layer sometimes contains areas of very high ionisation density which can produce weak sky waves (known as 'Sporadic-E' reflections) in the VHF band. The effect is unpredictable and the sky waves are scattered at random in the forward direction from the transmitter. With specially designed aerials, scatter propagation can sometimes be used to provide intermittent extended range VHF R/T but it is not a reliable means of communication.

Scatter propagation can cause mutual interference between VHF radio aids sharing a frequency and normally protected from interference by line of sight transmission. Television programmes also suffer from interference due to this effect.

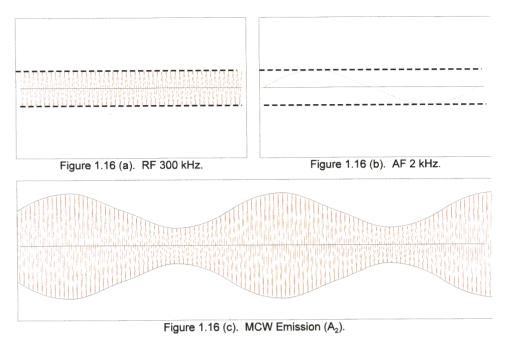1.35 MODULATION.

Intelligence in the form of speech, music, or single audio frequencies cannot be transmitted direct through space in the form of electro-magnetic waves, because the audio frequencies involved are too low for efficient transmission. To overcome this difficulty the audio frequency (from, say, a microphone) is combined with the radio frequency carrier wave at the transmitter. This process is called Modulation.

The resultant waveform (Modulated Carrier Wave or MCW) is transmitted through space. The radio frequency (RF) carrier wave can be considered to be 'carrying' the audio frequency (AF). The receiver separates the audio frequency from the carrier frequency, feeding the amplified audio frequency to the earphones or loudspeaker. Two main types of modulation used are 'Amplitude' and 'Frequency' modulation. Pulse modulation is also commonly used.



1.36 AMPLITUDE MODULATION (AM)

Figure 1.16(a). shows a constant-amplitude radio frequency (RF) carrier wave of say, $300 \, \text{kHz}$. Figure 1.16(b). depicts a constant-amplitude audio frequency (AF) of, say, $2 \, \text{kHz}$ which is the 'intelligence' required to be transmitted. The latter frequency, keyed in morse, could provide the identification letters for an NDB. Figure 1.16(c). illustrates the carrier wave modulated by the audio wave; this resultant waveform (MCW) is known as an A_2 emission, whether the signal is keyed or not.

It can be seen that the carrier wave amplitude is varied at a rate depending on the frequency of the audio wave. The amount of variation of the carrier wave amplitude depends on the amplitude of the audio wave. It should be noted that these and other diagrams are not to scale; for instance, with the frequencies chosen for Figures 1.16., there should be 150 cycles of the carrier wave drawn for each cycle of the audio wave. Further study of Figure 1.16(c). shows that the peaks of the carrier wave trace out the shape of the audio wave. This is indicated by the dotted line called the carrier wave envelope. The amplitude of this envelope is a measure of the strength (or 'loudness') of the sound transmitted. The extent to which the carrier is modulated is called the **depth of modulation**.

Depth of Modulation = Signal amplitude X 100% Carrier amplitude

1.37 SIDE FREQUENCIES.

The modulated signal depicted in figure 16(c) is the resultant of three frequencies. These are:-

- a) The carrier frequency (300 kHz)
- b) The carrier **plus** the audio frequency (300 + 2 = 302 kHz)
- c) The carrier **minus** the audio frequency (300 2 = 298 kHz)

The frequencies b) 302 kHz and c) 298 kHz are known as the Side Frequencies.

1.38 SIDEBANDS AND BANDWIDTH.

The spread of side frequencies above and below the carrier frequency are known respectively as the upper and lower sidebands. The total spread of frequencies in the modulated emission is known as the Bandwidth of the signal. In the case illustrated in Figure 1.16(c)., the bandwidth is 4 kHz (from 298 to 302 kHz). If the modulating audio frequency were reduced to 1 kHz, the bandwidth would be only 2 kHz.

A voice (or music) transmission consists of many different audio frequencies, up to at least 5 kHz, impressed on the carrier wave. Consequently many side frequencies exist in the modulated signal, which may have a bandwidth of at least 10 kHz. Such a signal is classified as an A3E emission; an example is VHF R/T.

1.39 SINGLE SIDEBAND TRANSMISSIONS.

The side frequencies of 298 kHz and 302 kHz in the example above both perform the same function, they transmit the 'intelligence'. One of these can be suppressed at the transmitter. For example, if the upper side frequency of 302 kHz is suppressed, the frequencies transmitted would be the 300 kHz carrier and the lower side frequency of 298 kHz.

Such a Single Sideband emission has certain advantages:-

- a) Narrower bandwidth occupying less room in the frequency band.
- b) The available transmitting power is concentrated in two frequencies instead of three.

The narrower bandwidth of the emission allows a narrower bandwidth (more selective) receiver to be used. (An alternative terminology is that a receiver with a narrower 'pass band' can be used.) The narrow pass band receiver allows a smaller band of frequencies to pass to the earphones - so cutting down the amount of radio 'noise' and increasing the effective range.

A further development is the suppression of the carrier frequency in addition to one of the side frequencies. This gives an even more efficient signal - a 'suppressed-carrier single sideband' emission. Such a transmission requires a modified receiver which substitutes the carrier frequency (which was suppressed at the transmitter), in order to extract the 'intelligence'. Single sideband emissions (SSB) are much used with modern HF R/T transmitter / receivers giving very long range sky wave voice communications by making the best use of the available sky wave propagation paths.

1.40 FREQUENCY MODULATION (FM).

In this method of modulating a carrier wave, the amplitude remains unaltered but the carrier frequency is made to vary about a mean value at a rate depending on the frequency of the modulating audio wave. Figure 1.17. illustrates.

The amount of frequency deviation above and below the normal carrier frequency depends on the amplitude of the modulating signal. The rate of frequency deviation depends upon the frequency of the modulating signal.

FM emissions have a greater bandwidth than corresponding AM emissions because the spread of side frequencies is greater and they are more numerous. Consequently FM is not used in the congested LF and MF bands where bandwidths have to be restricted.

The main advantage of FM systems is that they are relatively noise-free, since noise frequencies modulate the amplitude rather than the frequency of the carrier wave. Applications include BBC VHF sound broadcasting, VOR, Radio Altimeters and some airborne Doppler sensors.

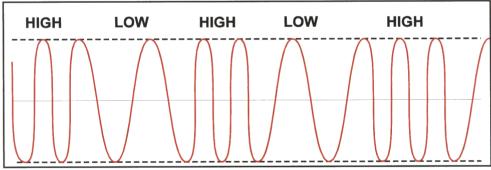


Figure 1.17.

1.41 AERIAL POLAR DIAGRAMS.

Whilst it is not necessary to know precisely how an aerial succeeds in emitting electro-magnetic radiation, it is useful to have some general knowledge of the distribution of radio energy about a transmitting aerial.

This distribution is commonly depicted by means of a polar diagram, basically a line joining points of equal signal strength. For a receiving aerial of similar design, the same polar diagram would apply - this time showing the reception pattern.

Consider a single vertical aerial transmitting a signal of constant power. In theory at least, a receiver carried round a horizontal circle with the transmitting aerial at its centre would receive a constant strength signal from the transmitting aerial. The horizontal polar diagram (radiation pattern) for a single vertical transmitting aerial is therefore a circle drawn with the transmitting aerial at its centre as in Figure 1.18.

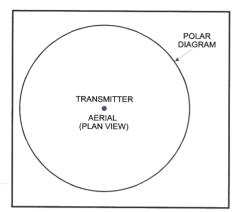


Figure 1.18. Horizontal Radiation Pattern (Single Vertical Aerial)

The radius of the circle is not important in itself because the circle is simply a line joining points receiving equal signal strength. Any radius could be chosen. Note that the vertical radiation pattern is more complicated and will not be dealt with at this stage.

The polar diagram in Figure 1.18. can also be used to show the reception pattern of a single vertical aerial, the latter being at the centre of the circle. A transmitter (with constant power output) could be moved in the horizontal plane round the receiving aerial and providing the transmitter followed a circular path, the receiving aerial would pick up a constant signal strength. So the polar diagram for a receiving aerial is a line joining the positions of a constant output transmitter which produce a constant signal strength at the receiver.

Aerial polar diagrams vary in shape depending on the complexity of the aerial system. A well-known combination of a single vertical receiving aerial and a vertical loop aerial produces a Cardioid (heart-shaped) reception pattern which is mentioned in the section on ADF.

A more complex system of aerials is employed by VOR transmitters to produce the rotating Limacon radiation pattern described in the section on VOR. Narrow 'beams' or 'lobes' of radiation can be produced by aerials of suitable design for use by such installations as ILS and PAR. Figure 1.19. illustrates some different radiation patterns produced by directional aerials which should be compared with the omni-directional pattern illustrated in Figure 1.18..

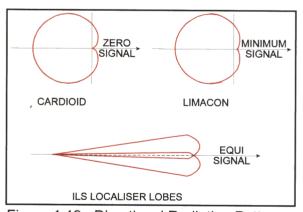


Figure 1.19. Directional Radiation Patterns.

1.42 CLASSES OF EMISSIONS

First Symbol (Type of modulation of main CW)

	T T		- 1	\sim	
N	linm	odulat	മവ	('ar	riei
14	Cimi	ouuiai	-u	Car	1101

- A Amplitude Modulated Double Sideband
- J Single Sideband, Suppressed Carrier
- P Unmodulated Pulses

ALSO

- H Single sideband
- **F** Frequency modulation
- **G** Phase modulation
- **K** Pulse modulated in amplitude

Second Symbol (Nature of signals modulating main CW)

- 0 No Modulation
- 1 Single channel, containing information, but unmodulated (keyed)
- 2 Single channel, containing information but modulated
- 3 Single channel, containing analogue information
- 7 Two or more channels containing information (digital)
- 8 Two or more channels, containing analogue information
- 9 Composite system (1, 2 or 7 above with 3 or 8 above)
- X Cases not otherwise covered

Third Symbol (Type of information to be transmitted)

- N No information transmitted
- A Telegraphy for aural reception
- E Telephony including sound broadcasting
- W Combination of above

ALSO

- **B** Telegraphy for automatic reception
- C Facsimile
- **D** Data transmission, telemetry
- F Television
- X Cases not otherwise covered

The Most Common Designations Are:

(NDB) NON A1A NDB NON A2A (HF COMMS) J3E (ILS) A8W (VOR) A9W (DME) PON (VHF) COMMS A3E (MLS) NOX G1D

1.43 FREQUENCY/WAVE LENGTH CONVERSION

Convert the following frequencies to wavelengths:

- a) 2300khz
- b) 403.5khz
- c) 71.4khz
- d) 6670khz
- e) 45Mhz
- f) 115Mhz
- g) 300Mhz
- h) 600Mhz
- i) 243Mhz
- j) 10Ghz

Convert the following λ to frequencies and state the navigation/communication aid using the facility:

- k) 3520m
- 1) 400m
- m) 2.62m
- n) 2.47m
- o) 89.5cm
- p) 3.41cm

- q) 28.3cm
- r) 3km
- s) 6.98cm
- t) 0.02m

1.44 DIRECT WAVE

Calculate the theoretical maximum range in nautical miles and kilometers of transmissions from a VHF station which is at mean sea level; an aircraft is at the altitude stated in the following:

- 1. 2500ft
- 2. 8100ft
- 3. 19000ft
- 4. 31000ft
- 5. 64000ft

Calculate the theoretical maximum range in nautical miles at which a VOR can be received by an aircraft:

VOR ELEVATION		AIRCRAFT ELEVATION	
6.	400ft	3600ft	
7.	1600ft	10000ft	
8.	325ft	3600ft	
9.	1500ft	20000ft	
10.	1370ft	22500ft	

Calculate the theoretical minimum altitude at which an aircraft must fly in order to receive a DME transmission using the following:

DME ELEVATION		AIRCRAFT RANGE
11.	MSL	75nm
12.	900ft	150nm
13.	6400ft	400nm

1.45 ANSWERS

a) Frequency/Wavelength conversion:

Ques	Answer	Ques	Answer	
1.	130.5m	11.	85.2 khz	Decca
2.	743m	12.	750 khz	NDB
3.	4200m	13.	114.4 Mhz	VOR
4.	45m	14.	121.5 Mkhz	VHF R/T (International Distress)
5.	6.67m	15.	335 Mhz	ILS Glidepath
6.	2.61m	16.	8800 Mhz	Doppler
7.	1m	17.	1060 Mhz	DME
8.	50cm	18.	100 khz	Loran C
9.	1.235m	19.	4300 Mhz	Radio Altemeter
10.	3cm	20.	15 Ghz	ASMI

b) Direct Wave

Ques	Answer	Ques	Answer
1.	15.75 km	8.	97.5 nm
2.	208.5 km	9.	225 nm
3.	319 km	10.	234 nm
4.	407.5 km	11.	3,600 ft
5.	585.5 km	12.	8,100 ft
6.	160 nm	13.	57,600 ft
7.	175 nm		

RADIO PROPAGATION REVISION QUESTIONS

- 1. Draw a diagram to show two cycles of an electromagnetic wave and illustrate the following terms:
 - a) Cycle
 - b) Wavelength
 - c) Amplitude
- 2. What is the speed of radio waves in m/sec and nm/sec?
- 3. State the formulae that are used to indicate the relationships of frequency, wavelength and speed of radio waves.
- 4. Convert:
 - a) a wavelength of 3.2 cm to a frequency and nominate its navigation aid.
 - b) a frequency of 15 Ghz to a wavelength and nominate its navigation aid.
 - c) a wavelength of 4m to a frequency and nominate its navigation aid.
 - d) a frequency of 15 Mhz to a wavelength and nominate its navigation aid.
- 5. Nominate the navigation aid and frequency band, by name and numerical limits, for the following frequencies:
 - a) 10.2 khz
 - b) 404.5 khz
 - c) 110.25 Mhz
 - d) 4.3 Ghz
- 6. Define the meaning of phase and draw a diagram which shows two radio waves of different amplitudes 135° out of phase.
- 7. Explain the terms "Horizontally" and " Vertically Polarised" with reference to the effecient transmission and reception of radio waves.
- 8. What is the theoretical maximum range in nautrical miles at which an aircraft at 10000 ft would receive a VHF transmission from mean sea level?
- 9. Explain the following terms in relation to the propagation of radio emissions
 - a) Attenuation
 - b) Refraction
 - c) Diffraction
- 10. List the factors which cause radio waves to be refracted as they enter the ionosphere.


- 11. With reference to HF communications make a sketch to show:
 - a) Skip distance
 - b) Dead space
 - c) Critical angle
 - d) The theoretical maximum range from a single hop
- 12. Why, for a given reception range, is the daytime HF frequency markedly different to the nighttime frequency; what is the approximate relationship?
- 13. State, in each of the following cases, two frequency bands in which you would expect:
 - a) the use of large transmitting aerials
 - b) considerable static interference
 - c) negligible static interference
 - d) maximum attenuation in precipitation
 - e) reception at ranges greater than 300 nm (exclude HF skywaves)
- 14. Describe the two types of "Freak Propagation".
- 15. With reference to MODULATION:
 - a) Why is it necessary to modulate a radio transmission?
 - b) Name the three main methods of modulation and draw diagrams to illustrate their differences.
 - c) Which type of modulation is restricted to the higher frequency bands and why is this so
- 16. With reference to POLAR DIAGRAMS:
 - a) What is a Polar diagram?
 - b) The simple directional LOOP polar diagram has one major disadvantage. What is this and how is it resolved?

SELF ASSESSMENT QUESTION PAPER

- 1. Phase comparison is only possible between two signals with the same:
 - a) Amplitude
 - b) Frequency
 - c) Amplitude and frequency
 - d) Plane of polarisation
- 2. The advantages of single sideband over double sideband communications systems are:
 - a) Bandwidth halved/power output many times greater
 - b) Bandwidth halved/signal to noise ratio greater/more power may be transmitted
 - c) Bandwidth reduced by 2/3 better signal to noise ratio greater
 - d) Bandwidth reduced by 1/3 power output reduced
- 3. A signal with a wavelength of 7360 metres lies in the:
 - a) VLF band
 - b) LF band
 - c) MF band
 - d) HF band
- 4 A frequency at with skywaves are unlikely to occur by day or night is:
 - a) LF
 - b) MF
 - c) HF
 - d) VHF
- 5. Which situation will give the greatest surface wave range?

	<u>Surface</u>	Frequency
a)	Sea	110.0 MHZ
b)	Desert	500 kHz
c)	Mountains	1.5 MHz
d)	Sea	500 KHz

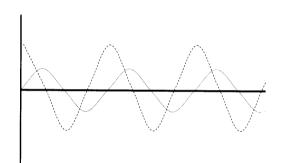- 6. A frequency which corresponds to a wavelength of 12 cm is:
 - a) 2500 KHz
 - b) 360 MHz
 - c) 2500 MHz
 - d) 3600 MHz
- 7. A maritime reconnaissance aircraft using primary pulsed air to surface radar first detects a large vessel on this radar at a range of 110 NM. Considering only line of sight limitations of the system the aircraft altitude must be approximately:
 - a) 230 ft
 - b) 790 ft
 - c) 2300 ft
 - d) 7700 ft
- 8. The diagram below shows two radio waves with:
 - a) The same frequency and amplitude, one 90° out of phase with the other
 - b) The same frequency, one being 270° out of phase with the other and having twice its amplitude
 - c) Different frequencies and amplitudes, and a phase difference of 90°
 - d) The same frequency, one being 270° out of phase with the other and having half its amplitude



9. You are heading west over the mid Atlantic at dusk. Which combination of frequencies would be most suitable for HF communications with stations ahead and behind?

	Ahead	Behind
a)	9 MHz	9 MHz
b)	9 MHz	3 MHz
c)	3 MHz	9 MHz
d)	9 Khz	3 KHz

10. Coasting out over the Irish Atlantic coast at dawn, pick suitable HF frequencies for communication with stations ahead and behind the aircraft:

	Ahead	Behind
a)	3 KHz	9 KHz
b)	9 MHz	3 MHz
c)	3 MHz	9 MHz
d)	9 MHz	9 MHz

- 11. The wavelength corresponding to a frequency of 108.95 MHz is:
 - a) 0.275 m
 - b) 275 m
 - c) 27.5 m
 - d) 2.75 m
- 12. A horizontally polarised wave is emitted from a.....antenna with thefield in theplane and the....field at 90° to it.

The correct line to complete the above statement is:

a)	horizontal	electrical	vertical	magnetic
b)	vertical	electrical	vertical	magnetic
c)	horizontal	magnetic	vertical	electrical
d)	vertical	magnetic	vertical	electrical

- 13. The optimum frequency of an HF signal is one which:
 - a) Puts the receiver just within the surface wave coverage
 - b) Puts the receiver just within the minimum skip distance
 - c) Puts the receiver just outside the minimum skip distance
 - d) Allows a skywave to return to the surface
- 14. As the frequency of a signal entering the ionosphere increases, the amount of refraction suffered by the signal will:
 - a) Increase
 - b) Decrease
 - c) Increase by day, decrease by night
 - d) Decrease by day, increase by night

- 15. A transmitter polar diagram is a line joining:
 - a) Points bounding the limits of reception
 - b) Points at which the signal to noise ratio will be 3:1
 - c) Points at which the signal to noise ratio will be 5:1
 - d) Points at which the signal strength will be equal
- 16. As the frequency of a transmitter is increased the range of the surface wave will:
 - a) Increase
 - b) Decrease
 - c) Remain the same by day but increase by night
 - d) Increase over the sea only
- 17. The type of modulation described as A3E is used in:
 - a) ILS equipment
 - b) VHF communications
 - c) HF single side band communications
 - d) Doppler VOR
- 18. As the frequency of an HF transmission is increased the dead space will:
 - a) Decrease
 - b) Increase due only to the increase of the minimum skip distance
 - c) Increase due only to the decreased surface wave coverage
 - d) Increase due to both the increasing minimum skip distance and to decreasing surface wave range
- 19. Atmospheric ducting is most likely to occur close to the surface of the earth when:
 - a) There is a marked inversion and no change in humidity with height
 - b) There is a marked inversion and a marked increase in humidity with height
 - c) There is a marked inversion and a marked decrease in humidity with height
 - d) Over the sea
- 20. The wavelength corresponding to a frequency of 9875 MHz is:
 - a) 0.303 m
 - b) 0.303 cm
 - c) 3.03 cm
 - d) 30.3 cm

21. A radio aid has a wavelength of 31 cm. The frequency of transmission and the band in which it operates are:


	Frequency	Band
a)	967.7 KHz	UHF
b)	967.7 MHz	UHF
c)	9.677 Ghz	SHF
d)	96.77 MHz	VHF

22. Study the diagram below which shows two radio signals:

The	S	ignal	w i	t h	t h e
		amplitude	has	a	phase
differen	ce	of	.from	the	other
signal.					

The line which correctly completes the above statement is:

a)	Smaller	325°
b)	Larger	225°
c)	Smaller	045°
d)	Larger	135°

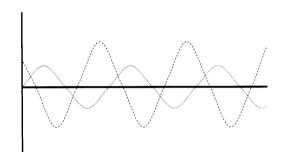

- VLF surface waves achieve a greater range than LF surface waves because:
 - a) VLF diffraction is greater and attenuation is less
 - b) VLF diffraction and attenuation are less
 - c) VLF diffraction is less and attenuation is greater
 - d) VLF diffraction and attenuation are greater
- 24. J3E is the emission designator for:
 - a) VHF comms
 - b) Doppler VOR
 - c) Decca
 - d) HF comms

25. The maximum theoretical range at which an aircraft at FL225 can receive signals from a VOR situated at 1600 ft AMSL is:


- a) 194 NM
- b) The DOC limit
- c) 237.5 NM
- d) 68.75 NM
- 26. A horizontally polarised wave is emitted from:
 - a) Horizontal antenna with the electrical field in the vertical plane and the magnetic field in the horizontal plane
 - b) Vertical antenna with the electrical field in the vertical plane and the magnetic field in the horizontal plane
 - c) Horizontal antenna rotating about a horizontal axis with magnetic and electrical fields in alternating horizontal and vertical planes
 - d) Horizontal antenna with the electrical field in the horizontal plane and the magnetic field in the vertical plane
- 27. As frequency increases:
 - a) Wavelength decreases and antenna size increases
 - b) Wavelength decreases and power requirements increase
 - c) Wavelength increases and antenna size decreases
 - d) Wavelength decreases and antenna size decreases
- 28. Loran operates at 100 KHz the wavelength and band are:

a)	3000cm	LF
b)	3000mm	VLF
c)	3 Km	LF
d)	3 NM	LF

29. A radio aid has a wavelength of 18.75 cm the frequency and band are:

a)	16 MHz	UHF
b)	16 Ghz	SHF
c)	1.6 Ghz	UHF
d)	16 KHz	SHF

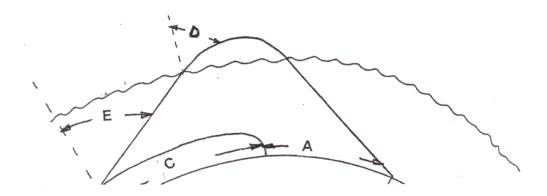- 30. Frequency modulation techniques are not used in the LF/MF/HF bands because:
 - a) The power requirements would be too high
 - b) Naturally occurring static would swamp the signal
 - c) The large bandwidth required is not available in these congested bands
 - d) Frequency modulation had not been invented when frequencies in these bands were allocated to users
- 31. What is the average height of the F layer of the ionosphere:
 - a) 75 km
 - b) 225 km
 - c) 275 km
 - d) 500 km
- 32. Look at this diagram. The correct labelling for Critical Angle, Dead Space and Skip Distance will be:



	critical angle	dead space	skip distance
a)	A	· C	D
b)	A	В	C
c)	D	A	В
d)	E	A	В


ANSWER SHEET

QUESTION	ANSWER	QUESTION	ANSWER
01		21	
02		22	
03		23	
04		24	
05		25	
06		26	
07		27	
08	>	28	
09		29	
10		30	
11		31	
12		32	
13		33	
14		34	
15		35	
16		36	
17		37	
18		38	
19		39	
20		40	

RADIO THEORY


REVISION QUESTION ANSWERS (P 3.1 - 29)

1.

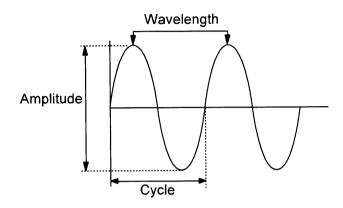

- 2. 300 x 10⁶ m/s and 162000nm/sec
- 3. $c = f \lambda$
- 4. a) 9375 Mhz AWR
 - b) 2 cm ASMI
 - c) 75 Mhz Fan marker
 - d) 20 m HF radio
- 5. a) omega 3 30 khz
 - b) NDB MF band 300Khz 30 Mhz c) VOR VHF 30Mhz - 300 Mhz
 - d) Rad Alt SHF 3 30 Ghz

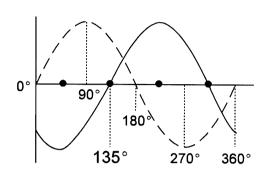6. Phase is a rotational relationship (measured in degrees) between two sine waves



The reference wave always commences at the graph intercept (dotted line) and this point is 0° of phase rotation. The phase points are now marked along the **reference** sine wave $0^{\circ} 90^{\circ} 180^{\circ} 270^{\circ}$ etc. The variable sine wave passes through zero volts going positive 135° out of phase with the reference sine wave. It **must** be the same frequency, the amplitude is unimportant.

- 7. A horizontally polarised system uses horizontal Transmitter and Receiver antennas. The "E" waves are horizontal and the "H" (magnetic) waves are vertical.

 A vertically polarised system has vertical antennas Vertical "E" and Horizontal "H"
- 8. Providing no intervening high ground

$$R_{MAX}$$
 (nm) = 1.25 x ($\sqrt{H_1}$ (ft) + $\sqrt{H_2}$ (ft))

$$R_{MAX}$$
 (nm) = 1.25 x ($\sqrt{0} + \sqrt{10,000}$)

$$R_{MAX}$$
 (nm) = 1.25 x 100

$$R_{MAX}$$
 (nm) = 125 nm

9. **Attenuation** occurs as soon as the radio waves leave the antenna, it is the process of making smaller.

Refraction occurs because of changes in velocity when a radio wave passes from one medium to another. ie. From land to sea, or from atmosphere to ionosphere.

Diffraction is the process of bending of a radio wave to stay in contact with earth's surface. Diffraction varies inversely with frequency.

- 10. Radio waves refraction in ionosphere
 - i) Frequency and therefore wavelength


Frequency increases, refraction decreases

Only a narrow band 2 - 25 Khz suffer the optimum refraction. Frequencies below this suffer excessive ionospheric attenuation. Frequencies above this pass straight through the ionosphere because they are not refracted enough.

ii) Refraction varies with the state of the ionosphere -

which varies a) diurnally)
b) seasonally) Predictable variations
c) with latitude)
d) with short term solar disturbances (SIDS)


11.

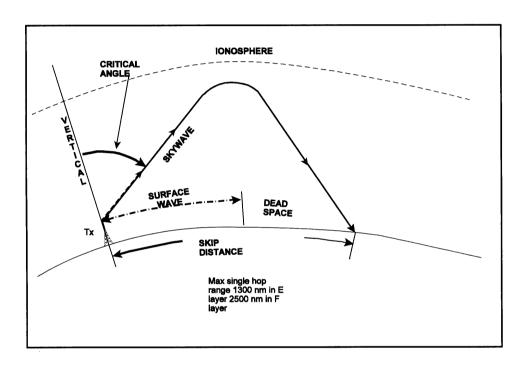


12. At night the base of the ionosphere is higher and the ionosphere is generally less strongly ionised. Therefore night refraction occurs at a markedly higher level so the night frequency needs to be reduced to approximately half the day frequency value. This reduces the critical angle and reduces the skip distance.

- 13. a) Decca Loran LF band
 - b) LF/MF
 - c) VHF upwards
 - d) UHF/SHF/EHF (nothing currently in syllabus for EHF)
 - e) Loran and Decca LF


14. a) <u>Ducting at VHF and above</u>

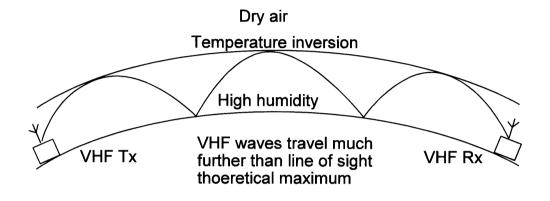


14. b) <u>Sporadic "E"</u>

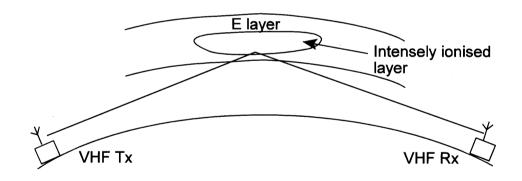

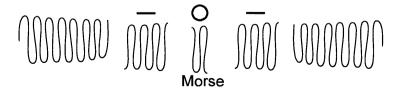
- 15. a) To superimpose intelligence on a carrier frequency
 - b) (i) Keying



b) (ii) Amplitude AM

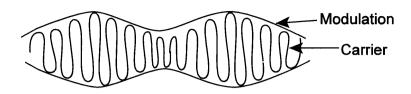

b)(iii) Frequency Mod (FM)

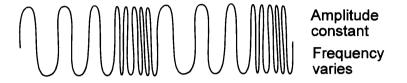


b)(iv) Pulse modulation




c) FM is limited to VHF and above because it requires a wide bandwidth which is not available in congested lower frequency bands.

16. A polar diagram is line joining points where signal strength is equal.

Loop Polar diagram

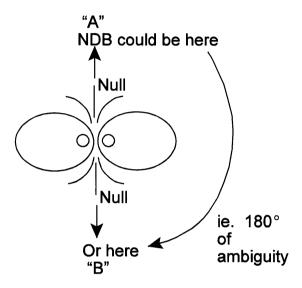

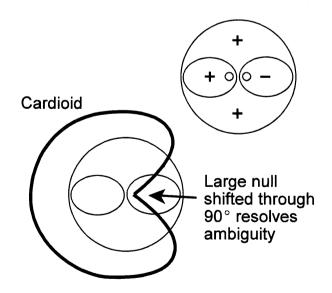This 180° ambiguity is resolved by combining the loop PD with the sense PD and forming a cardioid PD.



RADIO THEORY ANSWER SHEET

SELF ASSESSMENT QUESTIONS page 3.1 - 31 to 3.1 - 37.

No	A	В	С	D	REF	No	A	В	С	D	REF
1		X				21		X			
2		X				22		X			
3		X				23	X				
4				X		24				X	
5				X		25		X			
6			X		,	26				X	
7				X		27				X	
8		X				28			X		
9		X				29			X		
10			X			30			X		
11				X		31		X			
12			X			32				X	
13			X			33					
14		X				34					
15				X		35					
16		X				36					
17		X				37					
18				X		38					
19			X			39					
20			X			40					

CHAPTER TWO - OSCILLATORS

Contents

		Page
2.1	PURPOSE	3.2 - 1
2.2	PRINCIPLE OF OPERATION	3.2 - 1
2.3	TYPES OF OSCILLATORS	3.2 - 2
2.4	RESONANT FREQUENCY	3.2 - 2
2.5	L.C. OSCILLATOR.	3.2 - 4
2.6	PIEZO-ELECTRIC EFFECT.	3.2 - 4
2.7	QUARTZ CRYSTAL CONTROLLED OSCILLATOR	3.2 - 5
2.8	BANDWIDTH AND SELECTIVITY	3.2 - 5
2.9	CATHODE RAY TUBE	3.2 - 6
2.10	CRT COMPONENTS	3.2 - 6
2.11	MICROWAVE OSCILLATORS	3.2 - 7
2.12	KLYSTRON	3.2 - 8
2.13	MAGNETRON	3.2 - 9
SELF .	ASSESSMENT QUESTIONS	.2 - 11

2.1 PURPOSE

An oscillator is an electronic circuit designed to produce an AC sinewave. The frequency of this wave ranges from relatively low, a few hundred Herz, to frequencies in the V/UHF band. Specialist oscillators can produce frequencies to the S/EHF band.

Oscillators are used in radio **transmitter** systems to produce the **carrier wave** that will carry information from transmitter to receiver.

Oscillators are used in the radio **receiver** systems to generate a signal which when mixed with the received signal will produce an **intermediate frequency** which is lower that the received signal and much easier to amplify and process. This is the **super-heterodyne principle.**

2.2 PRINCIPLE OF OPERATION

An oscillator has no input signal but manages to produce an AC oscillating output signal from just a DC supply. It does this by using positive feedback. All oscillators consist of three basic parts:

- a) a frequency determining unit
- b) an amplifier
- c) a positive feedback unit

The principle of operation is shown in figures in Figures 2.1 and 2.2.

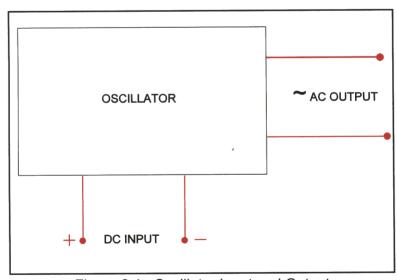


Figure 2.1. Oscillator Input and Output

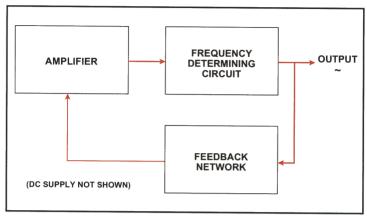


Figure 2.2. Principle of an Oscillator

2.3 TYPES OF OSCILLATORS

Radio systems use sinusoidal oscillators that produce an output in the form of sine waves. The frequency determining unit may be one of the following types:

LC (inductance -capacitance)

RC (resistance - capacitance)

Crystal

The LC and crystal oscillators will be discussed in these notes.

2.4 RESONANT FREQUENCY

Inductive reactance, X_L varies directly with frequency whereas capacitive reactance, X_C varies inversely with frequency. If we display X_C against frequency on the same graph as X_L against frequency, there is a point corresponding to a certain frequency where $X_L = X_C$.

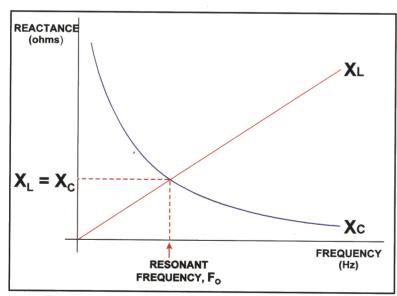


Figure 2.3. X_L and X_C plotted against frequency

The frequency where $X_L = X_C$ is called the resonant frequency (F_0) .

At this point:
$$2\pi FL = \frac{1}{2\pi FC}$$

Solving for **f** we get
$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

At the resonant frequency alone $X_L = X_C$ and because of the relationship of the currents, they effectively cancel each other. So at the resonant frequency in a parallel LC circuit the current flow increases dramatically as all opposition to current flow has been cancelled.

If an inductor of $5\mu H$ was placed in parallel with a capacitor of $2.5\mu F$ the resonant frequency would be:

$$F_0 = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(5x10^{-6})x(2.5x10^{-6})}} = 45016Hz \text{ or } 45\text{khz}$$

Now let us connect the above LC circuit into a complete oscillator circuit.

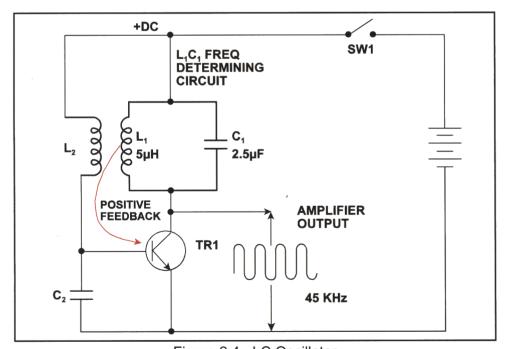


Figure 2.4. LC Oscillator

2.5 L.C. OSCILLATOR.

In the circuit on previous page we have a complete oscillator. This is known as a tuned-collector oscillator. The **frequency determining circuit** is formed by the parallel connected L1 and C1 (sometimes called a **tank circuit**).

The amplifier is Transistor TR1 and its job us to make up for losses in the circuit.

Positive feedback is provided by transformer coupling between L1 and L2 to the base of TR1. This positive feedback keeps the circuit oscillating, rather like whipping a top. Left to its own devices a spinning top will soon stop spinning unless energy is applied to it in the correct direction. Energy applied in the wrong direction will stop the spinning i.e. negative feedback.

When the switch **SW 1** is closed the transistor conducts and **shock excites** the L C circuit into oscillation. A portion of the oscillations are coupled via L1 and L2 to the base maintaining the oscillations (positive feedback). The output taken from the collector of TR1 is a sine wave of **45 Khz.**

If C1 or L1 were replaced by components of different value the output frequency would change. If C1 was replaced with a variable capacitor we would have a means of easily changing the output frequency of the oscillator.

2.6 PIEZO-ELECTRIC EFFECT.

A piezo electric crystal is a material that produces an emf if it is subjected to mechanical stress. The emf reverses polarity if the stress is reversed. Conversely the application of a potential difference across the crystal causes a stress in the material according to the polarity of the crystal voltage.

When a quartz crystal has a voltage applied across it, it will vibrate and produce a small electrical AC signal at a frequency that is dependent upon its thickness (Resonant Frequency).

Using quartz crystals as the frequency determining device in oscillators produce extremely **precise stable frequencies**. They are particularly used for producing frequencies at VHF and above.

2.7 QUARTZ CRYSTAL CONTROLLED OSCILLATOR

The crystal acts as both the frequency determining circuit as well as providing the positive feedback

Whereas the output frequency of a LC oscillator may drift with temperature variations as the device warms up, a crystal controlled oscillator is extremely stable. The disadvantage is that we cannot easily change the frequency as we could in a LC oscillator. Modern developments have overcome this minor drawback.

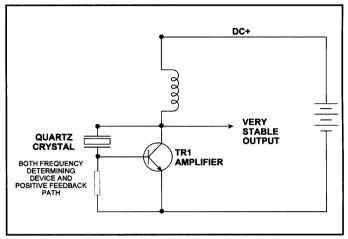


Figure 2.5 Crystal Controlled Oscillator

2.8 BANDWIDTH AND SELECTIVITY

The figures above show the frequency response of two LC tuned circuits with the same resonant frequency, f_0 Frequencies f_1 and f_2 occur at 0.707 Vp which is known as the half power or -3dB points. They give us the bandwidth for the circuit, which is f_2 - f_1 . It can be seen that circuit (B) has a larger bandwidth than circuit (A).

Selectivity is the ability of a tuned in a receiver to differentiate between adjacent stations. It can be seen that a circuit with a narrow bandwidth will have a higher selectivity.

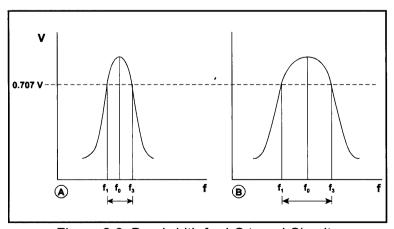


Figure 2.6 Bandwidth for LC tuned Circuits

2.9 CATHODE RAY TUBE

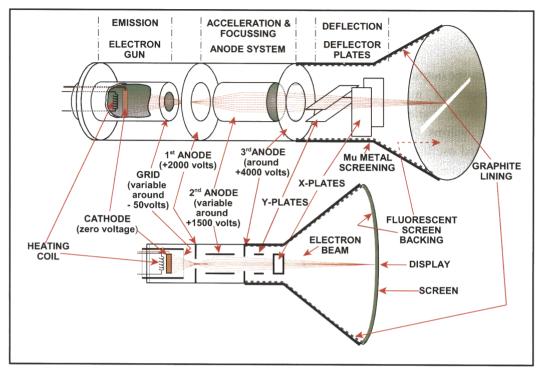


Figure 2.7 An Electrostatic Cathode ray Tube.

- a) **Description**. A Cathode Ray Tube (CRT) is an evacuated glass tube in which a controllable beam of electrons is produced and directed on to a screen to give a visible display. The tube may be of the electrostatic or the electromagnetic type.
- b) **Applications.** CRT's are used as displays in **radar** systems to give a circular presentation on plan position indicator (PPI) or a rectangular display when used in computerised radar systems. The **television** screen is also part of a CRT.

2.10 CRT COMPONENTS

a) The Electron Gun. This is made up of the heater cathode and the grid. The cathode consists of a small cylinder inside which is a low voltage heater. One end of the cylinder is covered in a barium salt; when heated this emits electrons. The grid is a metal cylinder surrounding the cathode and is always more negatively charged than the cathode. Thus the electrons emanating from the cathode are repelled from the grid walls and form a concentrated narrow beam.

The **negative** potential of the **grid can be varied** to control the number of electrons passing through it to give **brilliance control**. To increase the brilliance the negativity is decreased. If the grid is made too negative the flow of electrons ceases and the beam is cut-off.

b) Anode System. From Figure 2.7. it can be seen that the anode system accelerates the electron beam along the tube, because it is highly **positive** in respect to the **cathode**. It also controls the **focus** by adjusting the potential of the second anode.

- c) **Deflection System.** The electrostatic system uses **deflection plates** inside the tube whereas the electromagnetic system uses **coils** wrapped round the outside of the tube. In the electrostatic system, varying potential on the plates causes the electron beam to deflect horizontally and vertically to 'paint' a picture on the screen by moving the electron 'spotlight' across the screen.
- d) Flourescent Screen. The inside of the screen is coated with a flourescent substance which glows when it is bombarded by the electron beam. The colour and persistence of the glow depend upon the substance used. For colour displays three electron beams are used to produce the full range of colours from the three primary colours of **Red**, **Green and Blue**. Three secondary colours are produced by mixing the primary colours as follows:

```
Red + Green = Yellow (or amber),
Red + Blue = Magenta and
Green + Blue = Cyan.
```

2.11 MICROWAVE OSCILLATORS

Microwave is the general term used to describe radio frequencies higher than 1 Ghz i.e. when the wavelengths can be measured in cms or mms. At such frequencies conventional circuits using transistors become unusable due to radiation losses and increased resistance arising from skin effect.

Klystrons and **Magnetrons** are two of the devices that can be used for microwave oscillators. They have frequency determining circuits built into the device and work on a different principle to conventional oscillators; they use **resonant cavities**.

The shape of the resonant cavity can be rectangular, spherical or cylindrical. The internal diameter of the cavity which should be half wavelength, determines its resonant frequency. Due to skin effect the currents flow only on the inner surfaces of the cavity. The outer surfaces can therefore be earthed without affecting the cavity operation.

2.12 KLYSTRON

The Klystron is a low power oscillator which comprises:

- a) a resonant cavity
- b) an electron gun

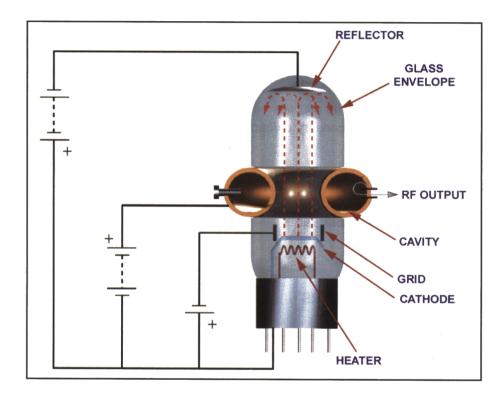


Figure 2.8 Klystron Oscillator

- c) a reflector electrode
- d) an output coupling.

An arrangement for a klystron oscillator is shown at figure 2.8.

Electrons generated at the cathode are roughly focussed into a beam by the negative cylindrical grid and the positive cavity acting as an anode. Positive feedback is provided by the electrons which pass through the lips of the cavity and are then reflected back by the negative reflector. The net result is that an oscillation is set up inside the cavity. The frequency is dependent upon the cavity dimensions which can be altered by an adjustable screw.

The resulting currents in the cavity walls can be fed to the output terminal via a coupling loop. Klystrons are used as low power oscillators in radar receivers.

2.13 MAGNETRON

For **higher power** outputs a magnetron is used in microwave oscillators. The magnetron is constructed by making a number of cavities in a solid block of copper. Each cavity oscillates to the same frequency as the others. There several versions of cavities used with the most easily recognisable cavity being the hole and slot type.

The component parts of a magnetron include the anode, the cathode the output coupling and also a powerful magnet. The cavity block is placed inside the poles of the magnet as shown in figure 2.9.

Electrons emitted by the cathode travel in complicated circular orbits and may return to the cathode. Oscillations are set up in the cavities and a coupling to one of the cavities provides the means of extracting the radio energy via co-axial feed connected to a waveguide.

Magnetrons are used as high power oscillators in Radar transmitters.

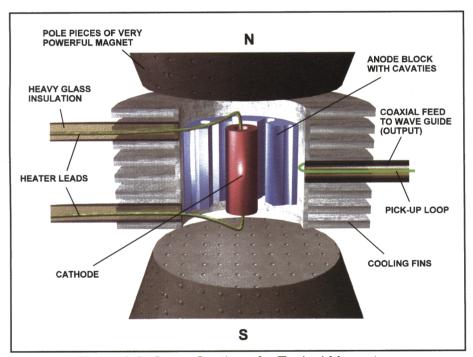


Figure 2.9 Cross-Section of a Typical Magnetron

RADIO THEORY OSCILLATORS

SELF ASSESSMENT QUESTIONS

OSCILLATORS

- 1. The purpose of a basic Oscillator is to:
 - a. amplify a signal
 - b. attenuate a signal
 - c. produce a sine wave from a DC input
 - d. increase the frequency of a sine wave
- 2. A basic oscillator consists of
 - 1. amplifier
 - 2. positive feedback path
 - 3. negative feedback path
 - 4. frequency determining circuit
 - 5. DC supply
 - 6. AC supply
 - a. 1, 3, 4, 5.
 - b. 1, 2, 4, 5.
 - c. 1, 3, 4, 6.
 - d. 1, 2, 3.
- 3. An electrical resonant circuit is constructed from:
 - a. resistors and inductors in series
 - b. inductors and resistors in series or parallel
 - c. inductors and resistors always in parallel
 - d. capacitor and inductor which may be in parallel or series
- 4. When a parallel inductive capacitive circuit is operating at its resonant frequency:
 - a. capacitive reactance is greater than inductive reactance
 - b. inductive reactance is greater than capacitive reactance
 - c. inductive reactance equals capacitive reactance and a large circulating current exists
 - d. inductive reactance equals capacitive reactance and zero current flows in the circuit

5. Capacitive reactance:

- a. decreases as frequency increases
- b. increases as frequency increases
- c. remains constant with changes in frequency
- d. remains constant up to approximately 30MHz and then decreases with increasing frequency

6. Inductive reactance:

- a. decreases as frequency increases
- b. increases as frequency increases
- c. remains constant with changes in frequency
- d. effectively falls to zero at VHF and above

7. In a LC circuit the frequency where XL = XC is called:

- a. Impedance (Z)
- b. Cancellation point
- c. Oscillation frequency (F_0)
- d. Resonant frequency (F_0)

Look at the circuit at annex A and answer the following 3 questions

- 8. Which components form the resonant circuit and control the frequency of operation:
 - 1. C1
 - 2. L1
 - 3. TR1
 - 4. L2
 - 5. C2
 - a. 1 and 2 only
 - b. 1, 2, 3, 5.
 - c. 2, 3, 4, 5.
 - d. 3 only


9. The NPN transistor TR1 is necessary to:

- a. form the positive feedback path to maintain oscillations
- b. act as the frequency controlling device
- c. act as an amplifier and make up for losses in the circuit
- d. form the negative feedback path to maintain oscillations


- 10. Positive feedback in the circuit:
 - a. is provided by transistor TR1
 - b. is provided by transformer coupling between L1 and L2
 - c. is not necessary, the oscillations are maintained by negative feedback
 - d. is determined by the ratio of C1 to L1
- 11. In the circuit at Annex A it is necessary to make the output frequency variable. This could be achieved by:
 - a. replacing C1 with a variable capacitor
 - b. placing a variable resistor in the emitter of TR1
 - c. increasing the turns ratio of L1 L2
 - d. making the gain of transistor TR1 variable
- 12. The Piezo electric effect is:
 - a. the resonation when XL = XC
 - b. the generation of sine waves by an oscillator
 - c. a quartz crystal vibrating at a frequency dependent on its thickness when an EMF is applied to it
 - d. a quartz crystal vibrating at a frequency dependent on the size of the EMF applied to
- 13. Look at the circuit at Annex B. This shows:
 - a. an audio frequency amplifier
 - b. a radio frequency amplifier
 - c. a crystal controlled oscillator
 - d. a LC controlled oscillator
- 14. The advantages of a crystal controlled oscillator over a LC controlled oscillator include:
 - 1. cheapness of construction
 - 2. precise stable frequency output
 - 3. very narrow bandwidth
 - 4. frequency can easily be changed
 - a. 2 and 3 only
 - b. 1, 2, and 3
 - c. 1, 3, and 4
 - d. there are no particular advantages

- 15. The output frequency of a magnetron depends on:
 - a. the voltage applied to the cathode
 - b. the voltage applied to the anode
 - c. the size of the cavities
 - d. the material from which the cavities are constructed
- 16. To produce frequencies in the SHF (microwave) band which of the following could be used:
 - 1. LC oscillator
 - 2. Crystal oscillator
 - 3. Magnetron
 - 4. Klystron
 - a. 1 and 2 only
 - b. 2, 3, and 4
 - c. 3 and 4 only
 - d. 3 only
- 17. Oscillations in a magnetron are maintained by:
 - a. electrons under the influence of a magnetic field energising the cavities
 - b. electrons under the influence of an electrostatic field creating negative feedback to the cavities
 - c. electromagnetic coupling between anode and cathode
 - d. electromagnetic coupling between heater and cathode
- 18. The high power pulse of a ground radar system is most likely to be produced by:
 - a. crystal oscillator
 - b. klystron
 - c. klystron followed by a power amplifier
 - d. magnetron

ANNEX A

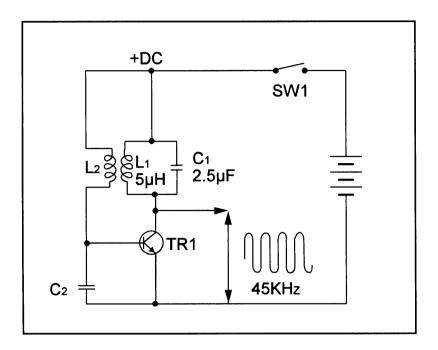

ANNEX B

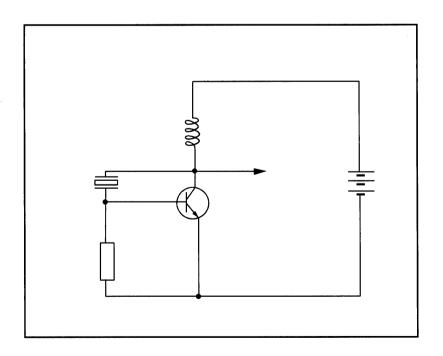

OSCILLATORS SAQ. ANSWER SHEET.

No	A	В	С	D	REF
1			X		
2		X			
3				X	
4			X		
5	X				
6		X			
7				X	
8	X				
9			X		
10		X			
11	X				
12			X		
13			X		
14	X				
15			X		
16			X		
17	X				
18				X	

CHAPTER THREE - ANTENNAE

Contents

		Page
3.1	INTRODUCTION	3.3 - 1
3.2	POLARISATION.	3.3 - 1
3.3	RADIATION PATTERN OR POLAR DIAGRAM	3.3 - 2
3.4	HALF WAVE DIPOLE ANTENNA	3.3 - 3
3.5	DIRECTIONAL ANTENNAE	3.3 - 3
3.6	ANTENNA DIMENSIONS.	3.3 - 4
3.7	ANTENNA FEEDING CABLES (FEEDERS)	3.3 - 4
3.8	ANTENNA TYPES.	3.3 - 6
	SELF ASSESSMENT OUESTIONS	3.3 - 9

3.1 INTRODUCTION.

If a wire is fed with an alternating current, some of the power from it will be radiated into space. A similar wire parallel to and remote from the first will intercept some of the radiated power and as a consequence an alternating current of the same frequency will be induced into it. This is the basis of the transmission and reception of radio waves.

The above involves a transfer of energy from one point to another through free space by means of an **electromagnetic wave** (EM Wave). This wave consists of **two** oscillating fields mutually perpendicular to each other and to the direction of propagation. The **Electric (E)** field will be parallel to the wire from which the wave was emitted while the **Magnetic (H)** field will be at right angles. A snapshot of such a wave is shown in Figure 3.1 where the distance between successive peaks is called the wavelength (λ) .

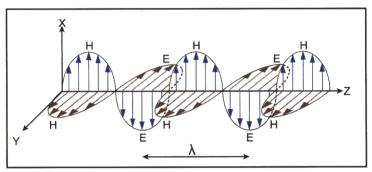


Figure 3.1. An Electromagnetic Wave

3.2 POLARISATION.

An electromagnetic wave launched from an antenna may be **vertically** or **horizontally polarised**.

Vertical Polarisation: This requires a vertical antenna which launches a vertical electric field and a horizontal magnetic field. Figure 3.2 shows a vertically polarised transmission.

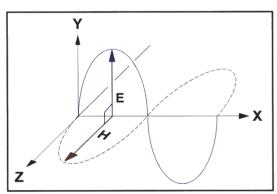


Figure 3.2. Vertically Polarised Transmission

Horizontal Polarisation: This requires a horizontal antenna which launches a horizontal electric field and a vertical magnetic field. Figure 3.3 shows a horizontally polarised transmission.

Note that the Electric field is always in the same plane as the antenna and the transmit and receive antennas must be in the same plane.

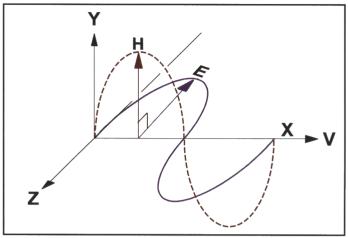


Figure 3.3 Horizontally Polarised Transmission

3.3 RADIATION PATTERN OR POLAR DIAGRAM.

By far, the most important characteristic of an antenna is its radiation pattern or **Polar Diagram**. In the case of a transmitter antenna, the pattern is a graphical plot of the power or field strength radiated in different angular directions. **Or, more simply, a transmitter polar diagram is a line joining points of equal power**.

A wide variety of polar patterns are possible, such as the **omnidirectional** pattern in which energy is radiated equally in all directions. The **pencil beam** pattern in which energy is concentrated mainly in one direction. The **cosecant squared** pattern where the radiated energy takes the shape of a fan. Figure 3.4. shows an omnidirectional transmitter polar diagram when radiation takes place from a single piece of wire.

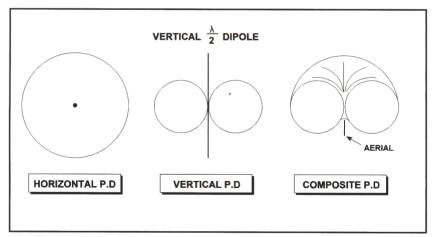


Figure 3.4. Omni Directional Transmitter Polar Diagram

3.4 HALF WAVE DIPOLE ANTENNA

A well known and efficient radiator is the half-wave dipole antenna. It consists of two quarter-wavelength (of the frequency being transmitted) radiators and is centre fed. Figure 3.5. shows the current and voltage distribution and relationship in the half wave dipole. Notice the voltage and current waves are 90° out of phase.

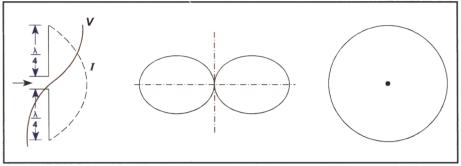


Figure 3.5. Half Wave Dipole

3.5 DIRECTIONAL ANTENNAE

A simple half wave dipole radiates omnidirectionally as shown above. If additional, un-fed elements are placed near to the dipole it is possible to concentrate the energy into one direction. The smaller elements placed in front of the dipole (in the direction of propagation) are called **directors**. The larger element placed behind the dipole is called a **reflector**. Together directors and reflectors are referred to as **parasitic elements**. Figure 3.6. shows a dipole, folded and fed with a signal, a reflector and three directors. It produces the beam pattern shown and is often called a **yagi array**.

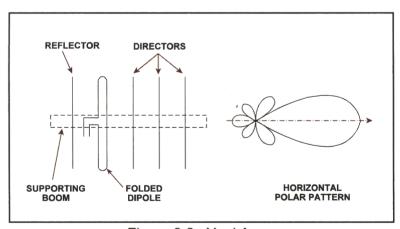


Figure 3.6. Yagi Array

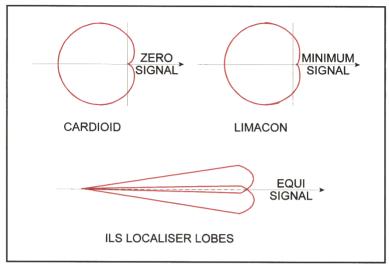


Figure 1.19. Directional Radiation Patterns.

3.6 ANTENNA DIMENSIONS.

A radiating wire, which is what an antenna is, is most efficient when it's length is equal to half a wave length of the frequency being transmitted. In practice it is not possible to exactly achieve this because of the prohibitively large size of the antenna at lower frequencies.

It is possible however, to increase an antenna's natural wavelength by the addition of inductance (L) or capacitance (C) or a combination of both (LC) in series with the radiating dipole. An antenna to which inductance, capacitance or a combination of both have been added is called a **Loaded Antenna**.

When an antenna is required to transmit a wide band of frequencies such as an aircraft HF Communications antenna, it may be necessary to "tune" the antenna after changing frequencies. This involves changing the amounts of L, C, or both in the antenna feeding circuit.

3.7 ANTENNA FEEDING CABLES (FEEDERS)

Antennae are designed to transfer energy in the form of electromagnetic waves from the element to free space efficiently. However, the antenna is likely to be remote from the transmitter where the electromagnetic wave originates. If a simplé piece of wire connected the transmitter to the antenna it would undoubtedly act as an antenna and radiate electromagnetic energy within the aircraft. (**Radiation Losses**). This would result in loss of power radiated to free space and also interference with other radio systems within the aircraft. To prevent these problems specialised feeders are required especially at higher frequencies.

a) **Coaxial Cables.** Here the signal is fed along the inner conductor and the outer conductor (called the screen) is earthed. This stops the signal escaping (Radiation Loss) before it reaches the antenna and also protects it from unwanted electromagnetic fields within the aircraft. Figure 3.7. shows coaxial cable.

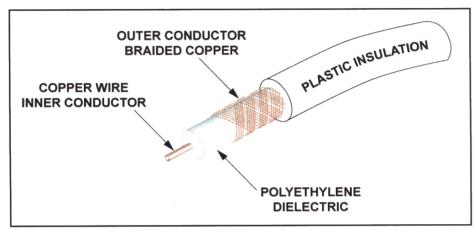


Figure 3.7. Coaxial Cable

- b) Waveguide: Coaxial cable becomes unusable at high power levels above about 1 Ghz. Radar systems use hollow, rectangular metal tubes to convey the electromagnetic energy from the transmitter to the antenna and also the received signals from the antenna to the receiver. The energy is actually propagated within the tube much as it would be in free space. The enclosure of the energy within the tube means that Radiation Loss is almost zero and also the phenomenon of Skin effect is minimised.
- c) **Skin Effect:** This phenomena occurs at the higher frequencies (VHF upwards) where high frequency currents tend to be confined to a thin layer (skin) of the conductor. Remembering that the resistance of a conductor is proportional to it's resistivity ρ, multiplied by it's length l, and divided by it's cross sectional area A.

Resistance is equal to $\underline{\rho}\underline{l}$

It can be seen that skin effect causing current to flow only in the skin area has effectively reduced the cross sectional area of the conductor (A) and this will cause the resistance to increase with subsequent attenuation of the signal.

To reduce skin effect some conductors are hollow, like miniature waveguide. Another way of combatting skin effect is to use multi-stranded wire, each strand being separately insulated. Such wire is known as "Litz" or "Endraht" wire.

3.8 ANTENNA TYPES.

a) Simple Antennae.

Over the years a wide variety of antenna designs have evolved and broadly speaking they can be divided into single radiators and multiple radiators. The monopole and dipole antennae have been used extensively in the past and are still used individually or as components of more complex arrays such as the Yagi array.

More recently, the **Helix** and **Spiral** antennae shown in Figure 3.9 have evolved and found a particular use in satellite communications because of their **broadband** properties. (Their ability to transmit and receive a wide band of frequencies without retuning).

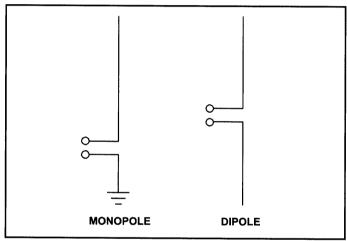


Figure 3.8. Single Element Antennae

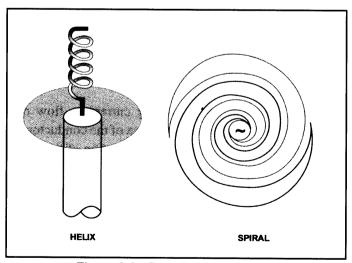


Figure 3.9. Broadband Antennae

b) Radar Antennae

The microwave horn, parabolic reflector and slotted planar array shown in Figure 3.10. are popular antennae which are used extensively in radar and satellite systems. Microwave horns are very often used as feeds for large parabolic reflectors.

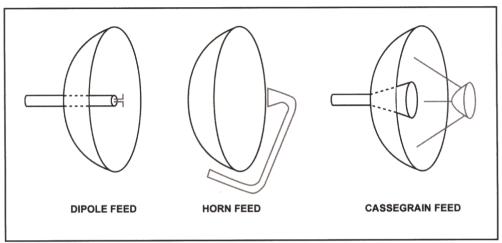


Figure 3.10. Radar Antennae

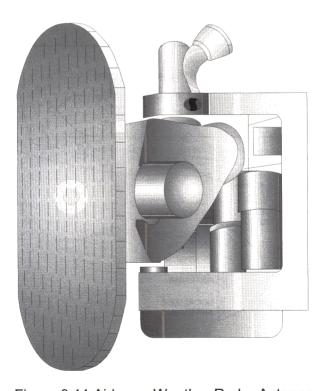


Figure 3.11 Airborne Weather Radar Antenna

c) Aircraft antennae.

Aerials in an aircraft appear in the form of wires, whips, probes, rods, blades, monopoles, dipoles or cavities. They can be external or internal. Figures 3.12. and 3.13. show some of the antenna on two different aircraft.

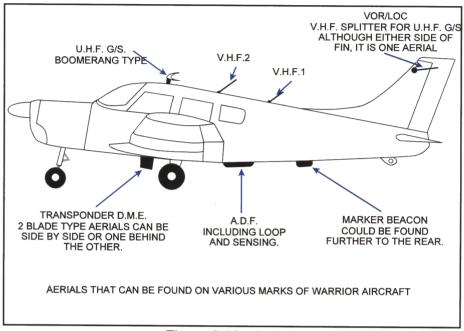


Figure 3.12. Aerials

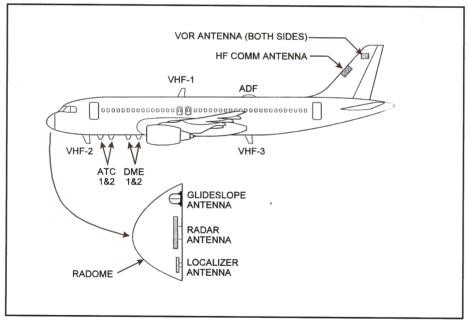



Figure 3.13. Antenna installations on modern airliners often include localizer and glidescope antennae inside the radome and flush mount VOR and HF comm antennae in the vertical fin.

SELF ASSESSMENT QUESTIONS

ANTENNAS AND FEEDERS

- 1. The relationship between current and voltage in a dipole or monopole antenna is:
 - a. they are out of phase by 90°
 - b. they are in phase
 - c. they are in phase on a monopole and out of phase in a dipole
 - d. they are out of phase by 180°
- 2. An antenna polar diagram is:
 - a. a line joining points bounding the limits of reception
 - b. a line joining points where the signal to noise ratio will be 3:1
 - c. a line joining points where the signal to noise ratio will be 5:1
 - d. a line joining points at which the signal strength is equal
- 3. A simple dipole may be made directional by:
 - 1. placing a reflector behind it
 - 2. placing directors behind it
 - 3. placing directors in front of it
 - 4. placing reflectors in front of it
 - a. 1 and 2 only
 - b. 1, 2, 3.
 - c. 1 and 3 only
 - d. 2 and 4 only
- 4. With reference to antennas, parasitic elements are:
 - a. unfed elements which make the radiation pattern directional
 - b. unfed elements which make the antenna radiation pattern omnidirectional
 - c. dipole or folded dipole radiating elements
 - d. parabolic reflectors placed behind the antenna

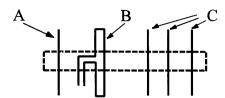- 5. In the diagram shown here the parts A, B, and C are respectively:
 - a. dipole, reflector and directors
 - b. parasitic element, reflector and director
 - c. reflector, dipole and directors
 - d. directors, reflector and fed element



6. What is a loaded antenna:

- a. a highly directional antenna
- b. a parabolic dish antenna
- c. an antenna which has had its natural wavelength increased by adding inductance and capacitance or a combination of both
- d. an antenna which has had its natural wavelength increased by adding directors and a reflector
- 7. Loaded antenna come in the following forms:
 - 1. inductive (L)
 - 2. resistive (R)
 - 3. capacitive (C)
 - 4. inductive capacitive (LC)
 - 5. resistive capacitive (RC)
 - a. 1, 2, 3, 4, and 5.
 - b. 4 and 5 only
 - c. 1, 3, and 4.
 - d. 1, 3, and 5.

8. Skin Effect:

- 1. causes insulation to breakdown
- 2. causes to current to flow only in the outer layer of the conductor
- 3. effectively reduces the resistance of the conductor
- 4. effectively increases the resistance of the conductor
- 5. may be overcome by using waveguides
- a. 1, 2, 3, 5.
- b. 2, 3, and 5.
- c. 2, 4, and 5.
- d. 1, 4, and 5.

- 9. Skin effect is most likely to occur:
 - a. at high power levels up to VHF
 - b. at the higher frequencies ie VHF and above
 - c. in radar systems fed by rectangular waveguides
 - d. in moist, humid conditions when insulation may breakdown
- 10. To overcome skin effect:
 - a. frequencies are reduced below VHF
 - b. power levels are reduced
 - c. use hollow conductors, multi stranded conductors or waveguide
 - d. use conductors with a large cross sectional area thus reducing resistance
- 11. "Litz" or "Endraht" conductors are:
 - 1. multi stranded wire
 - 2. separately insulated wire
 - 3. waveguide
 - 4. used to reduce skin effect
 - 5. used for the transmission of high voltages
 - a. 4 and 5 only
 - b. 1, 2, and 5
 - c. 1, 2, and 4
 - d. 1, 2, 3, 4, and 5
- 12. Radio beams may be "bent" or deflected by:
 - 1. Terrain and buildings
 - 2. antenna scan rates
 - 3. different power levels
 - 4. weather
 - 5. coastal refraction
 - 6. ionospheric refraction
 - a. 1, 2, 5, and 6
 - b. 1, 4, 5, and 6
 - c. 1, 2, 3, 4, 5, and 6
 - d. 1, 2, 3, and 4

- 13. The glide slope antenna radiates:
 - a. lobe transmissions on a UHF carrier which are amplitude modulated
 - b. lobe transmissions on a VHF carrier which are amplitude modulated
 - c. a scanning beam on a UHF carrier which is frequency modulated
 - d. a scanning beam on a SHF carrier with the designator A8W
- 14. The localiser transmitter radiates:
 - a. a scanning azimuth beam in the VHF band with 150 Hz and 90 Hz amplitude modulations
 - b. two lobes on a single VHF carrier with amplitude modulations of 90 and 150 Hz
 - c. two lobes on paired VHF carriers with amplitude modulations of 90 and 150 Hz
 - d. two lobes on a UHF carrier with amplitude modulations of 90 and 150 Hz
- 15. With reference to the ILS localiser, false course and reverse indications may be received:
 - a. never
 - b. anytime when outside the published coverage area
 - c. at up to 17 nm range when within $\pm -35^{\circ}$ of the approach course line
 - d. at up to 25 nm range when within $\pm 10^{\circ}$ of the approach course line
- 16. The lowest false glide slope associated with a 3° ILS is:
 - a. 2°
 - b. 3°
 - c. 6°
 - d. 12°
- 17. The ILS markers transmit:
 - a. lobes at 75 MHZ vertically upwards
 - b. a fan beam vertically upwards at 75 kHz modulated with amplitude modulated tones
 - c. a fan beam vertically upwards at 75 MHz modulated with amplitude modulated tones
 - d. lobes amplitude with tones vertically upwards
- 18. Fan markers use:
 - a. centimetric wavelengths
 - b. millimetric wavelengths
 - c. metric wavelengths
 - d. hectometric or kilometric wavelengths

19. MLS equipment uses:

- a. centimetric wavelengths
- b. millimetric wavelengths
- c. metric wavelengths
- d. hectometric or kilometric wavelengths

20. ADF uses:

- a. hectometric or kilometric wavelengths
- b. metric wavelengths
- c. millimetric wavelengths
- d. centimetric wavelengths

21. For a frequency of 121.95 Mhz what is the wavelength:

- a. 2.46 cm
- b. 2.46 mm
- c. 2.46 Km
- d. 2.46 m

No	A	В	С	D	REF
1	X				
2				X	
3			X		
4	X				. 4 . 1 .
5			X		Arg 198
6			X		
7			X		
8		,	X		
9		X			
10			X		
11			X		
12		X			
13	X				
14		X			
15		X			
16			X		
17			X		
18			X		
19	X				
20	X				
21				X	

Aviation Products From Jeppesen

TechStar

• Over 25 Aviation Calculations • 55 Conversions Available • 6 Independent Memory Registers

• Enter Values In Any Order, Or Change Them At Any Time • Pilot Friendly Use • Work On One Problem While Another On-Screen Calculation Is Being Completed • Weight And Balance Calculations Include Weight Shift Formulas • Three-Year Warranty • Batteries Included • Approved For Use On FAA Knowledge Examinations

Order Code - TECH





SOFTWARE-ONLY PACKAGE

The Software-only Package includes: FlitePro Software CD-ROM

- FliteSchool instrument course CD-ROM Installation handbook
- 10 ATC scenarios 200 selected Jeppesen SIMCharts approach plates Jeppesen worldwide database

Order Code - FLTPRO

Maneuvers Training on CD-ROM

Each CD-ROM is organized into a flexible, easy-to-use format. The design format allows you to choose what topics you would like to review and in what order you would like to study them in. Combine the Private Pilot Manual with the Maneuvers CD-ROM Course for the most exciting way to learn to fly. Order the complete Private Pilot Manuevers Multimedia Course or order individual topics. Includes a Student Tracking Disk for keeping track of your progress through the course and five CD-ROMs covering the following topics:

GFDCD1 Ground Operations CD-ROM

GFDCD2 Basic Maneuvers CD-ROM

GFDCD3 Airport Operations CD-ROM

GFDCD4 Emergency Landing Procedures / Flight Maneuvers CD-ROM

GFDCD5 Ground Reference Maneuvers CD-ROM

GFDPMA Private Pilot Maneuvers Software Course (5 CDs)

JS202500 Private Pilot Maneuvers Software Course

(5 CD-ROM's and Private Pilot Manual)

Chart Series

Professionally designed and produced, the FlighTime Chart Series Videos and DVD cover Jeppesen enroute charts and approach charts, as well as SIDs and STARs.

CHTS3V Videos

JS200300 DVD

Approach Charts includes a detailed introduction of Jeppesen's approach charts, featuring the Briefing StripTM format. RNAV and GPS procedures are also covered. Order Code - CAPPV

Enroute Charts features Jeppesen four-color enroute charts and

is based primarily on US-LO series charts. Order Code - CENRV

Departures and Arrivals presents the unique characteristics of SID and STAR charts. Order Code - CSIDV







To see our full range of products, please request the Jeppesen Catalog or visit our website: www.jeppesen.com

Aviation Products From Jeppesen

JOG-15/JOG-30 Chart Organizers

Transparent pockets are ideal for holding trip charts, flight plans, aircraft checklists, etc. Index tabs and spiral binding make it easy to access the chart you want.

Order Code - JOG-15 (15 Pockets)

Order Code - JOG-30 (30 Pockets)





Airline Flight Case

Designed by the pilots of Swiss Airline Crossair, this rugged, black leather Pilot's Case incorporates longer carrying handles rather than the briefcase-type grip. End flaps keep rain and dust out and serve to protect your valuable paperwork. Room for 4 Jeppesen binders. (Size: 46 x 29 x 19 cm) Order Code - FC-AIR

Three-Ring Trifold Kneeboard

Great for approach charts! Includes 3 approach chart pockets, pen/pencil or penlight holder and a metal

clipboard. Comes with FREE flight planning chart. Measures 10" x 20" open.

TRKNEE Kneeboard/Clipboard

TRCLIP Clipboard only with Leg Strap



Metal CSG (E6-B)

Solves low and high speed problems. Non-glare finish. Complete with instruction manual and carrying case. Order Code - CSG-AL



PN-1 Navigation Plotter

Allows easy identification of WAC and Sectional chart scales. Calibrated in statute and nautical

miles. (Size: 12¼"x4") Order Code - PN-1



Now Includes VFR Chart Set!

JAR FCL Student Pilot Route Manual

The Joint Aviation Authority (JAA) has requested Jeppesen provide the definitive Student Route Manual for the JAA Airline Transport Rating exams. In order to comply with the JAA syllabus, this manual is not revised. Student pilots will

need the manual during the JAA ATPL exams and can familiarize themselves with the material in advance by ordering a personal copy.

Order Code - STPRM

Order Code - STPRMVFR (Add VFR Supplement to existing manual)



Professional European Pilot Logbook

Complies with JAR 1.080 regulations for logging flight time in Europe. Handles 10 years of data. (Size: 17.1 cm x 28.6 cm) Order Code - JAALOG

For more information please contact your local Dealer or Jeppesen directly:



Frankfurter Strasse 233, 63263 Germany • Phone: +49 61 02 50 82 50 FAX: +49 61 02 50 82 82 • E-mail: fra-services@jeppesen.com www.jeppesen.com